

Thermal protection

Safety interlocks

Solid copper heat sink

Control circuit electronics


Cooling water flow switch

Test points

Convenient accessibility

Al Penney
VO1NO

Power Supplies

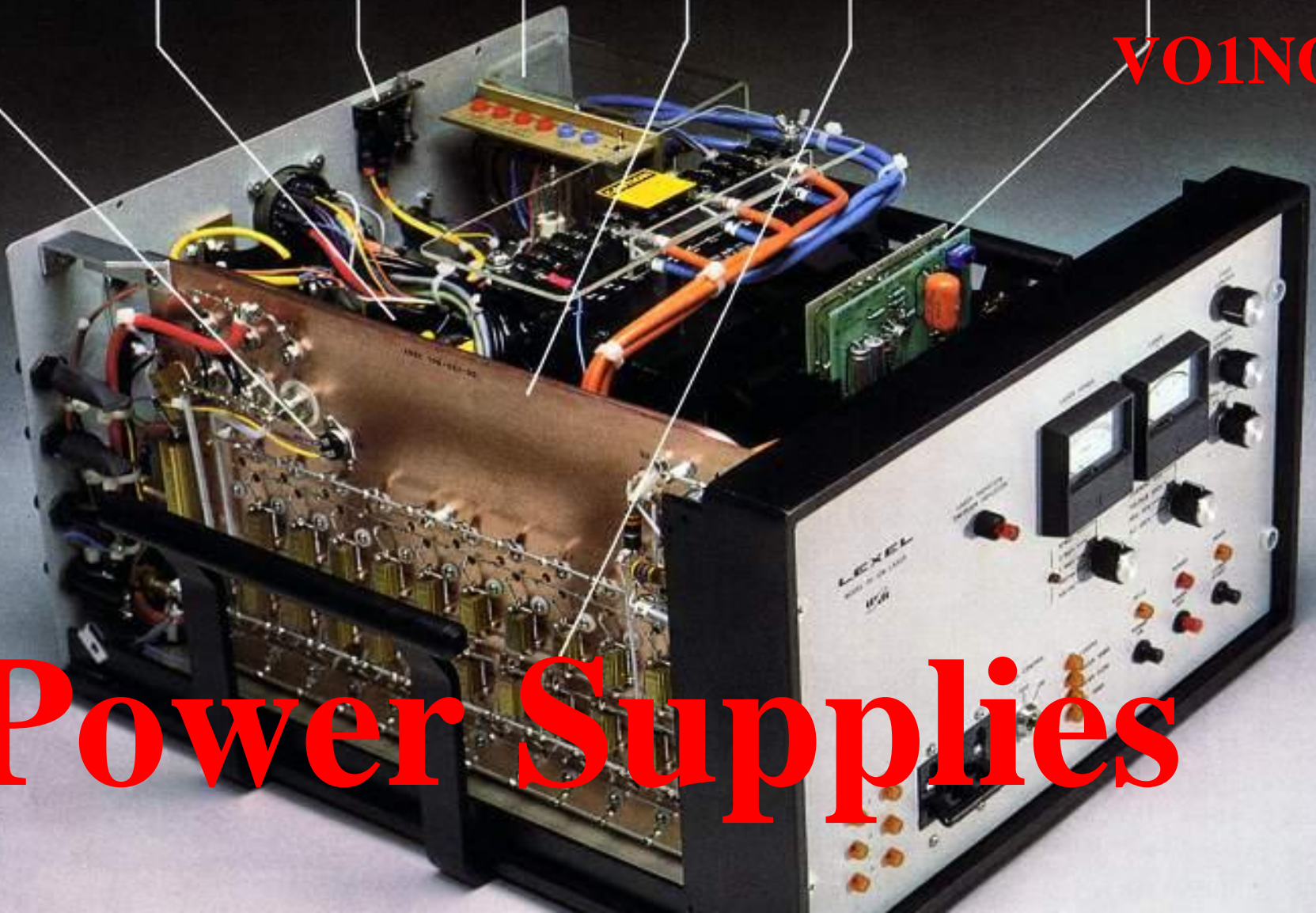

Power Requirements

- Most Amateur Radio gear today requires **13.8 volts DC (Direct Current)**.
- Wall outlets provide **120 volts AC (Alternating Current)** however.
- **To convert AC to DC at the proper voltage, we use Power Supplies.**


Typical Power Requirements

- TS-870S HF Transceiver 20.5 amps
- FT-7800R Dual Band FM Txcvr 8.5 amps
- FT-100 HF/VHF/UHF Transceiver 22.0 amps
- IC-7600 HF/6M Transceiver 23.0 amps

Power Supply Requirements

- **Voltage** must be **raised or lowered** to the desired value.
- **Voltage** must be changed from **AC to DC**.
- The DC that is produced will contain a lot of **ripple**, and must be **filtered**.
- The DC voltage must be **regulated** so that it **remains fairly constant**.

Power Supply Block Diagram




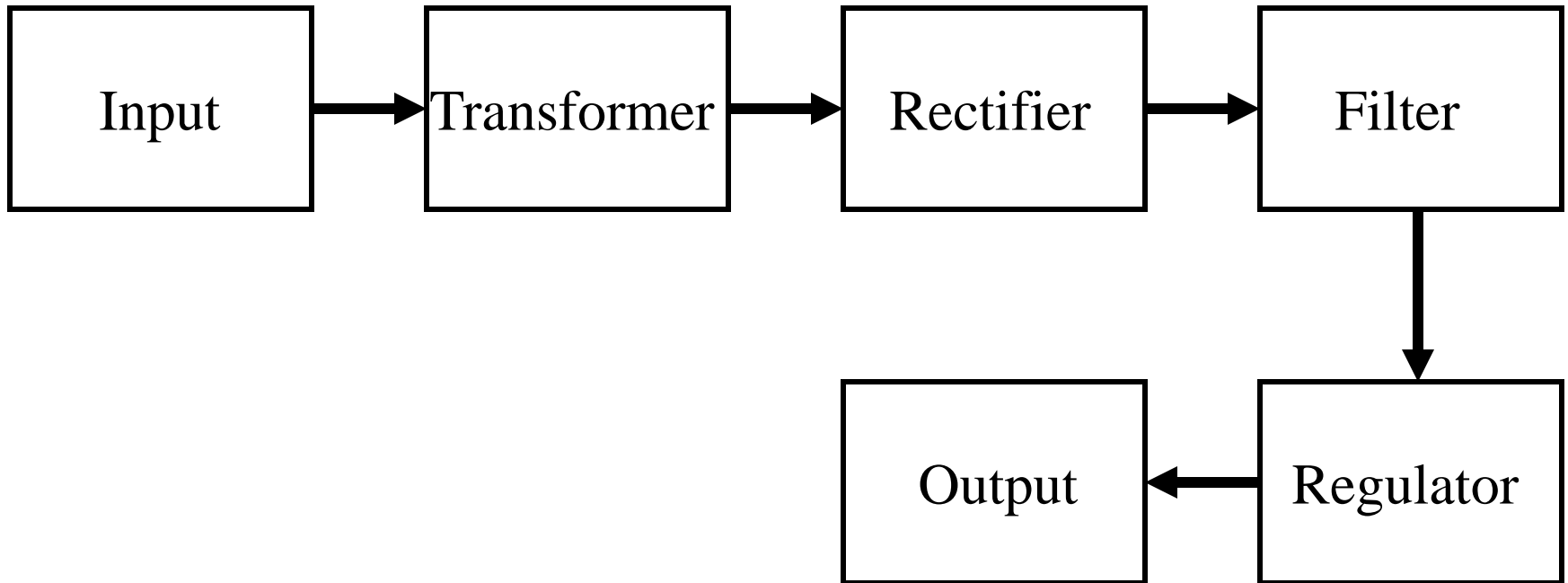


Changing the Voltage

- A transformer is used to step the voltage up or down.
- The ratio of turns in the primary and secondary windings determine the amount of voltage change:

$$\frac{\text{Primary Voltage}}{\text{Secondary Voltage}} = \frac{\text{\# Turns Primary winding}}{\text{\# Turns Secondary winding}}$$

Transformers

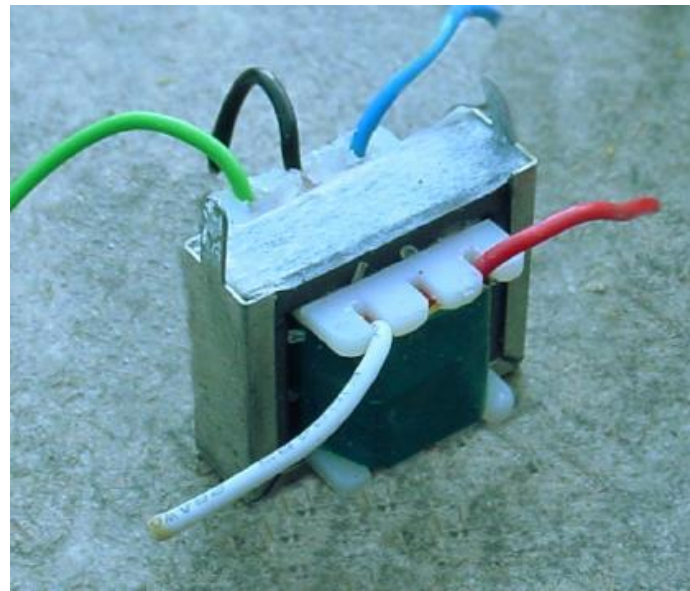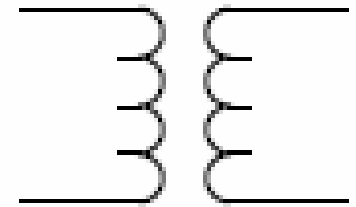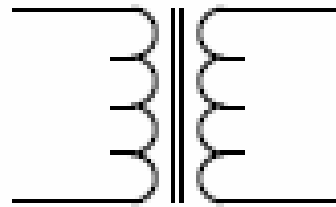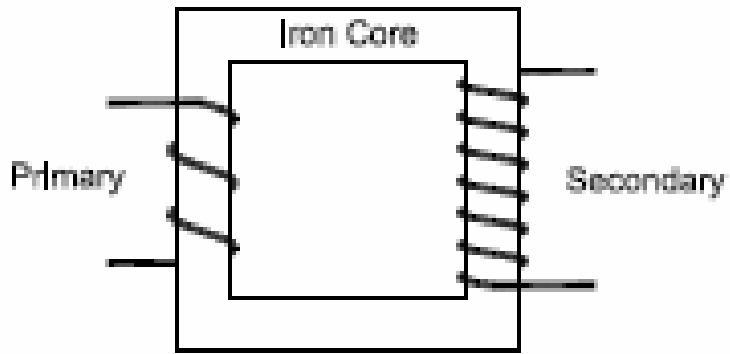

Example

- *Input voltage is 120 VAC. You require an output voltage of 13.8 VAC. The Primary winding has 240 turns. How many turns does the Secondary winding need?*

Example (2)

$$\frac{\text{Primary Voltage}}{\text{Secondary Voltage}} = \frac{\text{\# Turns Primary winding}}{\text{\# Turns Secondary winding}}$$

Example (3)

$$\frac{\text{Primary Voltage}}{\text{Secondary Voltage}} = \frac{\# \text{ Turns Primary winding}}{\# \text{ Turns Secondary winding}}$$

- $120 / 13.8 = 240 / T_{\text{sec}}$

- $T_{\text{sec}} =$

Example (4)

$$\frac{\text{Primary Voltage}}{\text{Secondary Voltage}} = \frac{\# \text{ Turns Primary winding}}{\# \text{ Turns Secondary winding}}$$

- $120 / 13.8 = 240 / T_{\text{sec}}$
- $T_{\text{sec}} = 240 \times 13.8 / 120$

Example (5)

$$\frac{\text{Primary Voltage}}{\text{Secondary Voltage}} = \frac{\# \text{ Turns Primary winding}}{\# \text{ Turns Secondary winding}}$$

- $120 / 13.8 = 240 / T_{\text{sec}}$

- $T_{\text{sec}} = 240 \times 13.8 / 120$

- $T_{\text{sec}} =$

Example (6)

$$\frac{\text{Primary Voltage}}{\text{Secondary Voltage}} = \frac{\# \text{ Turns Primary winding}}{\# \text{ Turns Secondary winding}}$$

- $120 / 13.8 = 240 / T_{\text{sec}}$
- $T_{\text{sec}} = 240 \times 13.8 / 120$
- $T_{\text{sec}} = 27.6$ turns, rounded to 28 turns

Power Rating of the Transformer

- Determined by the **size of the core** and the **diameter of the wire**.
- Power rating usually **stamped on the side** of the transformer, and is **expressed in Volt-Amperes** (abbreviated **VA**).
- **Power = Voltage x Current**
- Calculate power requirements of the equipment using the power supply and compare it with the Power rating of the transformer.

Power Rating Example

- *Radio draws 20 amps at 13.8 VDC.*
- *Transformer rated at 250 VA.*
- *Is the transformer big enough for the job?*

Power Rating Example (2)

- Power = Voltage x Current
- Power =

Power Rating Example (3)

- Power = Voltage x Current
- Power = 13.8 VDC x 20 Amps =

Power Rating Example (4)

- Power = Voltage x Current
- Power = 13.8 VDC x 20 Amps = 276 Watts

Power Rating Example (5)

- Power = Voltage x Current
- Power = 13.8 VDC x 20 Amps = 276 Watts
- Transformer is rated at 250 VA, so....


Power Rating Example (6)

- Power = Voltage x Current
- Power = 13.8 VDC x 20 Amps = 276 Watts
- Transformer is rated at 250 VA, so....
- The transformer is **NOT** big enough for the task!


Isolation

- The **load** attached to the transformer is **not physically connected** to the **primary**, as the windings are insulated.
- Much consumer equipment is powered without transformers to keep costs down.
- As a result the **chassis is directly connected** to one side of the **AC line**, and must therefore be enclosed in an insulated cabinet for safety reasons.
- Amateur gear **must be capable of interconnection**, and so such construction is unacceptable for us.
- **Fuse** in the AC line **provides additional safety.**


Isolation Transformer

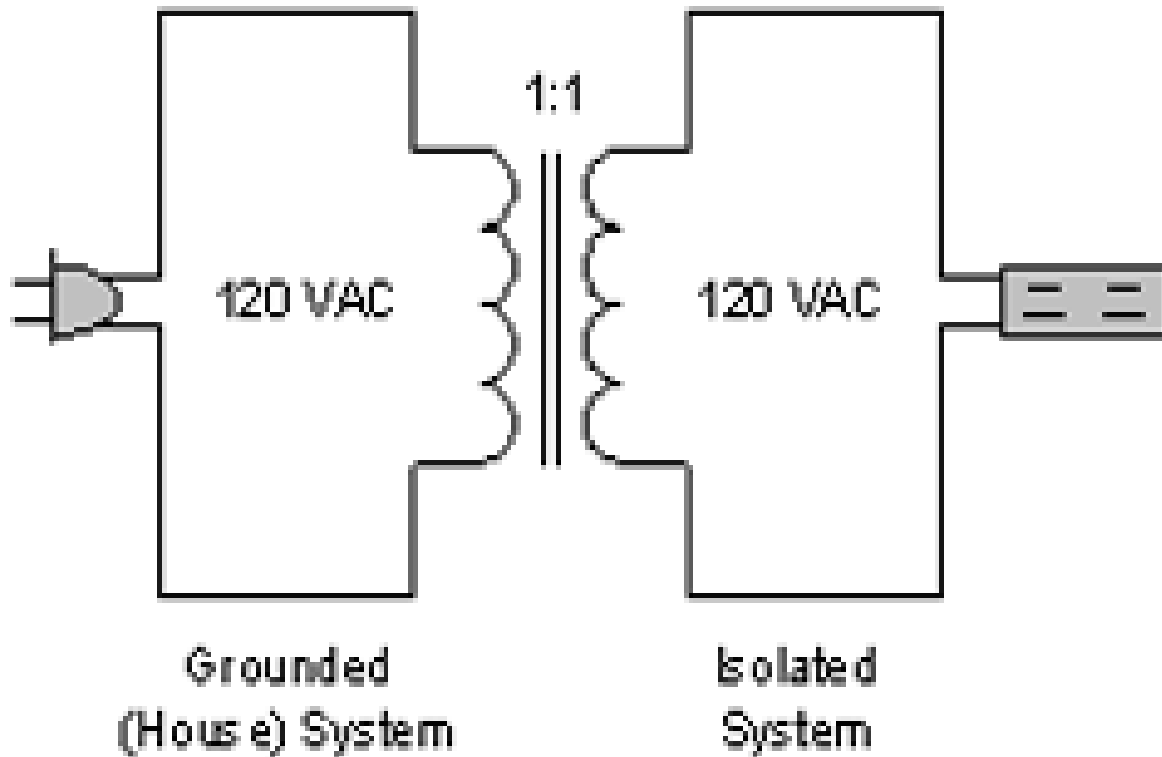

Without Isolation Transformer

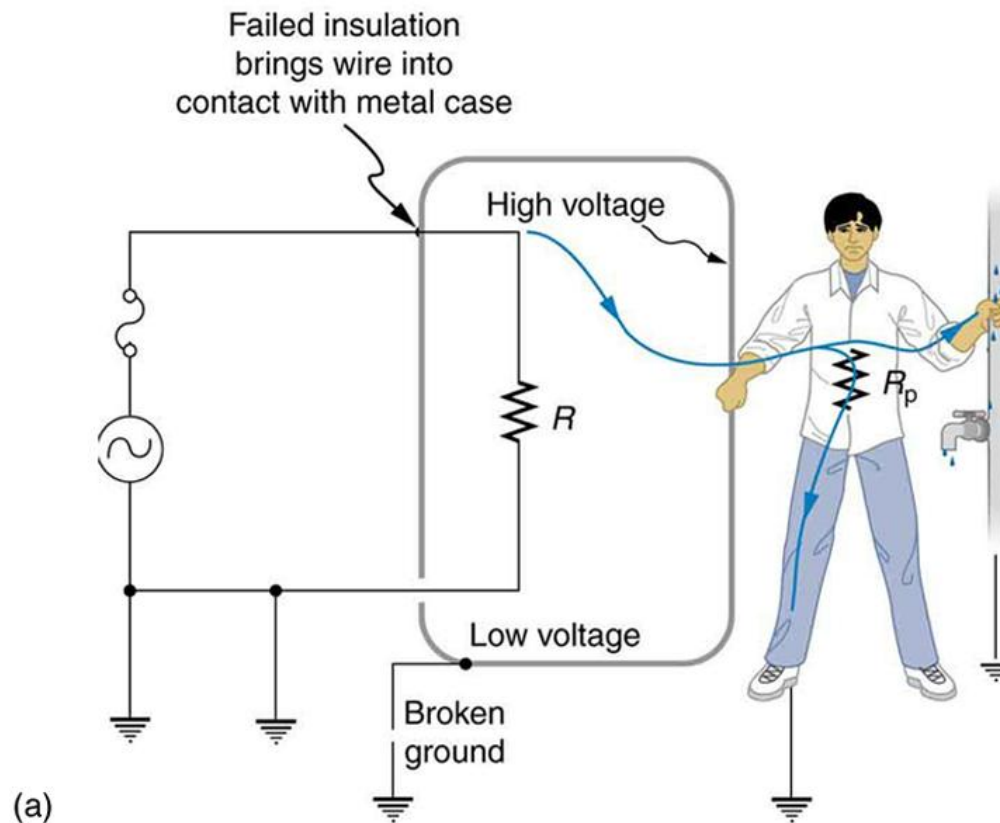



With Isolation Transformer

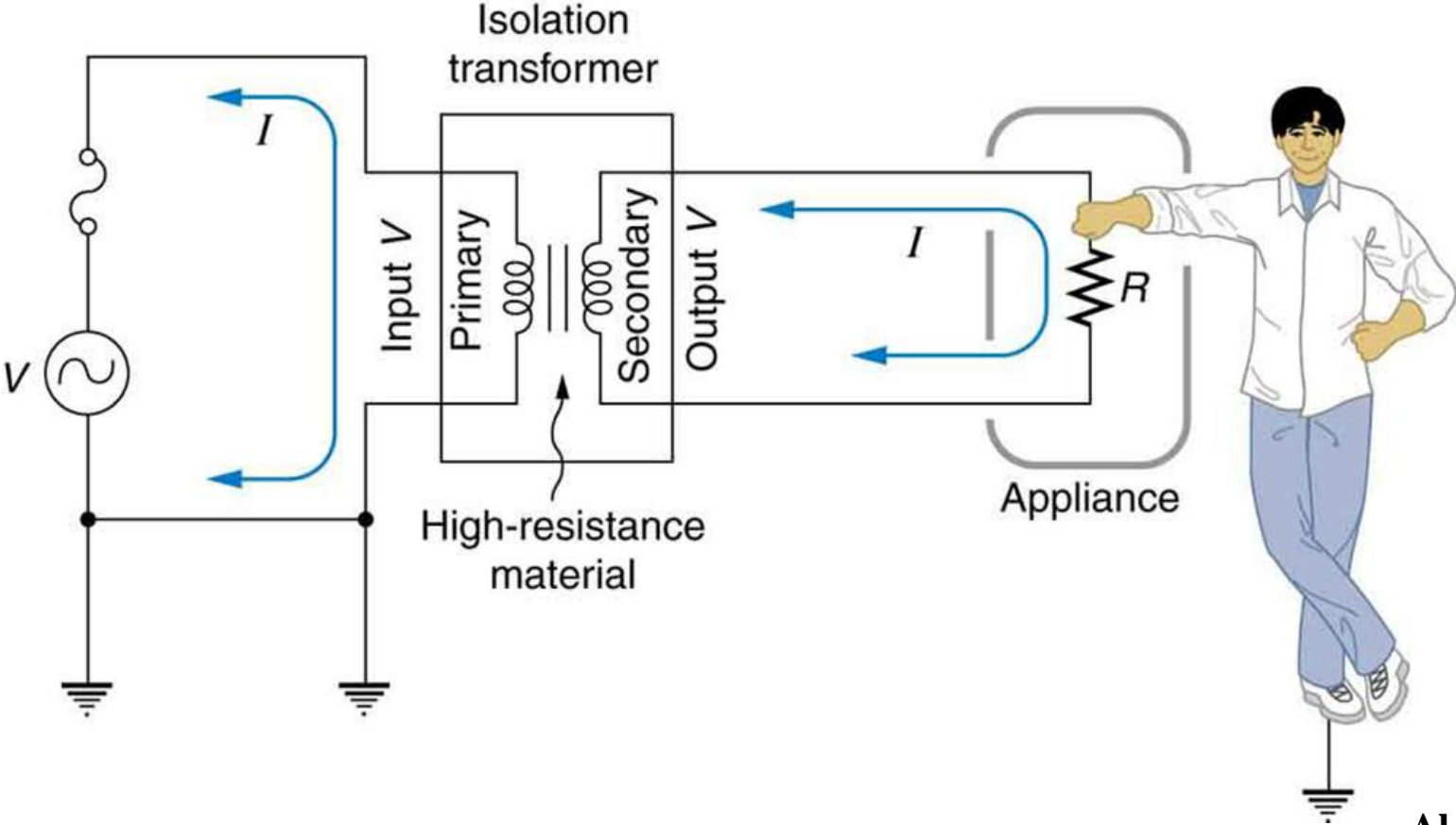

Rectification

- The process by which **AC is converted to DC** is called **Rectification**.
- Broadly classified as either:
 - **Half Wave:** rectify only the positive or negative half of each AC cycle; or
 - **Full Wave:** rectify both halves of the AC cycle.



Half Wave Rectification

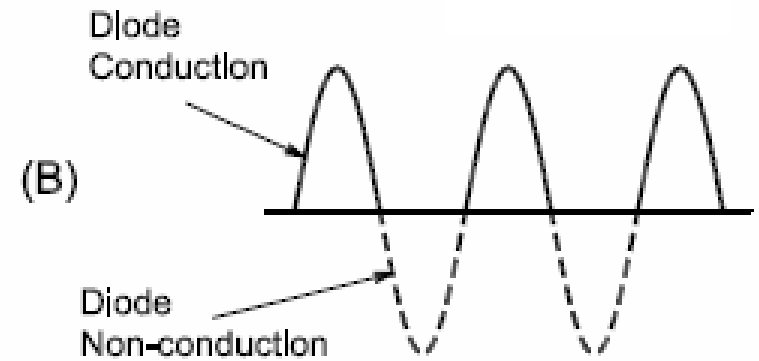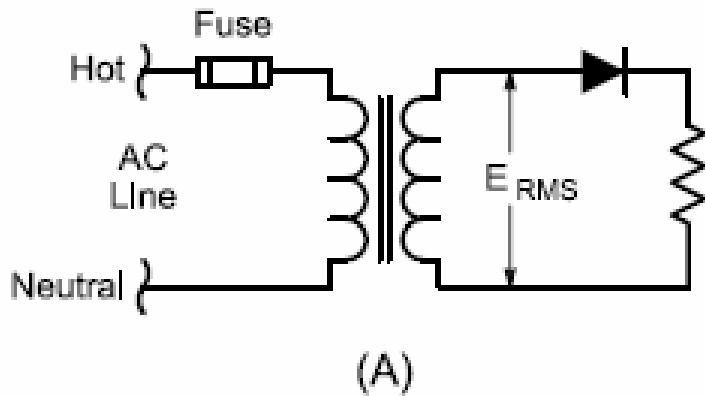

Half Wave Rectification

- Half Wave rectification only **passes half** of the energy thru to the output.
- Resulting DC is very **rough** and needs **heavy filtering**.
- If current requirements are small however, it provides a simple and low-cost solution.

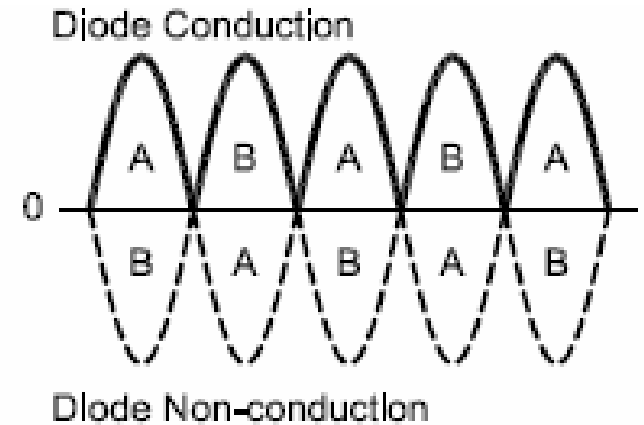
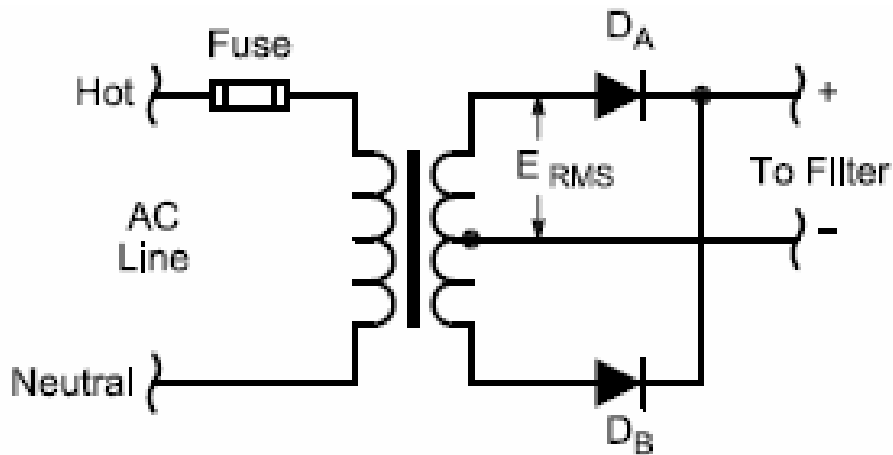
Full Wave Rectification Center-Tap Transformer



Full Wave Rectification Center-Tap Transformer

- **Passes all the energy** thru to the output.
- This method **requires a center tap** however.
- The diodes work alternately, handling the full current load but only for half the time.
- Essentially this is **two half wave rectifiers** operating on **opposite polarities of the AC cycle**.
- An advantage of this method is that the resulting DC **ripple frequency** is 120 Hz (twice 60 Hz), making it **easier to filter**.

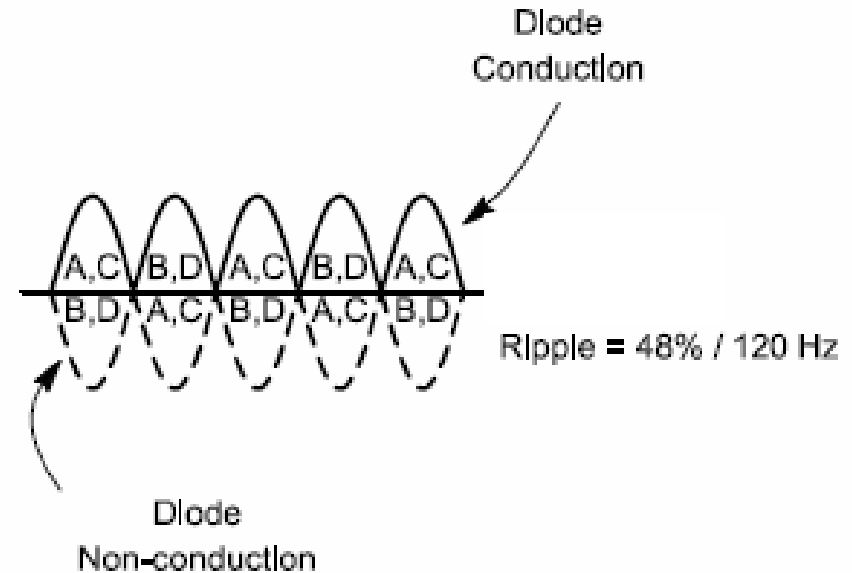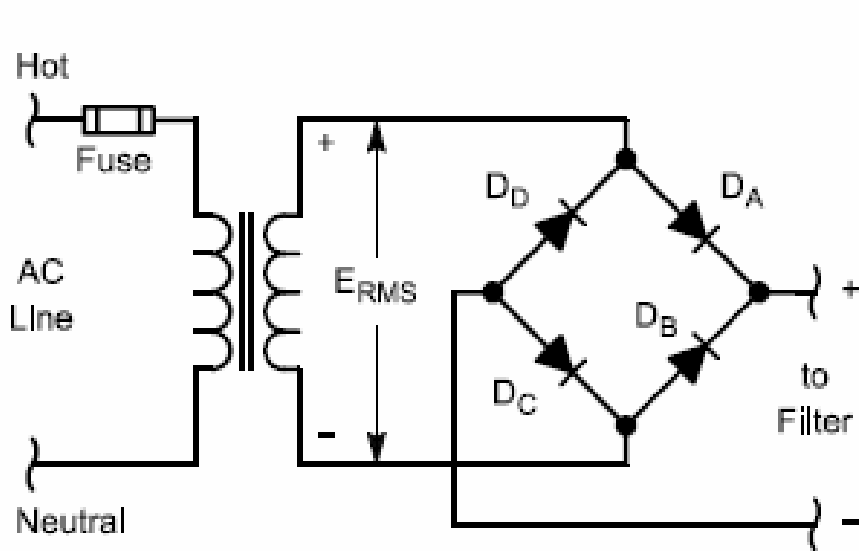Full Wave Rectification Without a Center Tap Transformer



Full Wave Rectification Without a Center Tap Transformer


- This method **eliminates** the requirement for a **center tap transformer**.
- It uses a **Full Wave Bridge Rectifier**.
- Note the polarity of the diodes – two will conduct and two will not conduct on each half-cycle.

Filtering the DC

- Straight out of the rectifier stage, the **DC pulsates**, causing severe hum on transmitted and received signals, as well as a host of other problems.
- This **fluctuating DC** must be “smoothed out” by a **filter**.
- The most effective way to do this is by **using a capacitor** across the output of the power supply.

Simple Full Wave Power Supply


6VDC 300mA Rated AC Adaptor (Wall Wart)

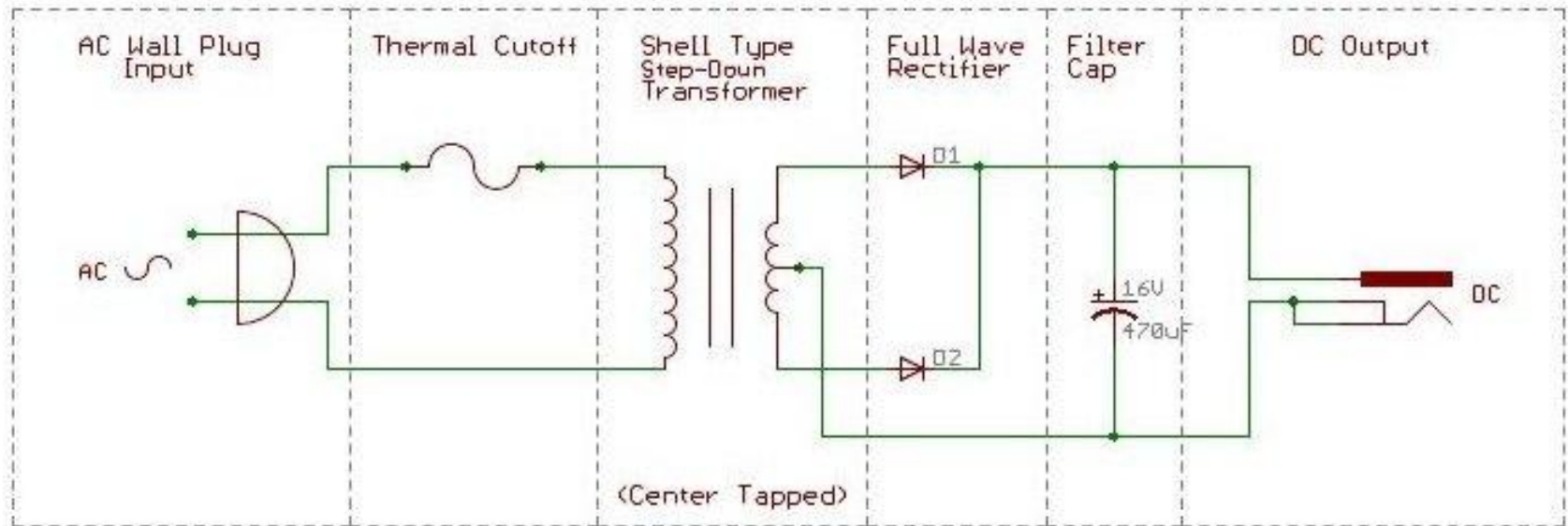

Voltage Output

Straight from
Rectifier stage

Input from Rectifier

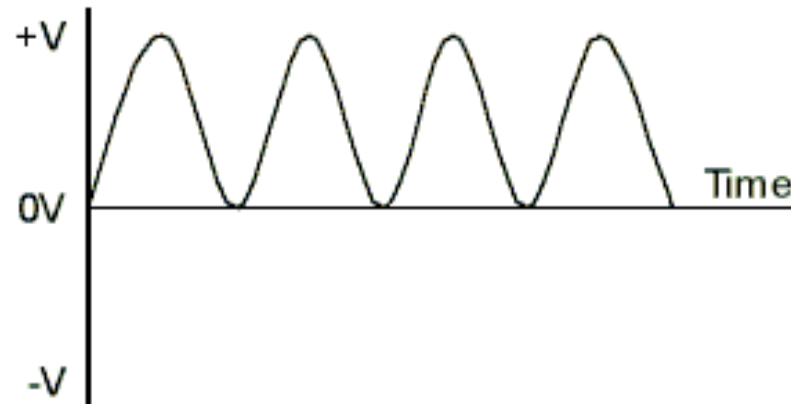

After filtering by
the Capacitor

Smoothed Output


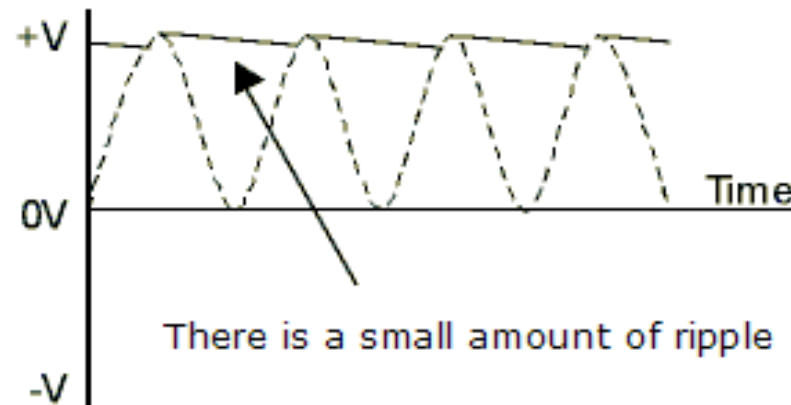
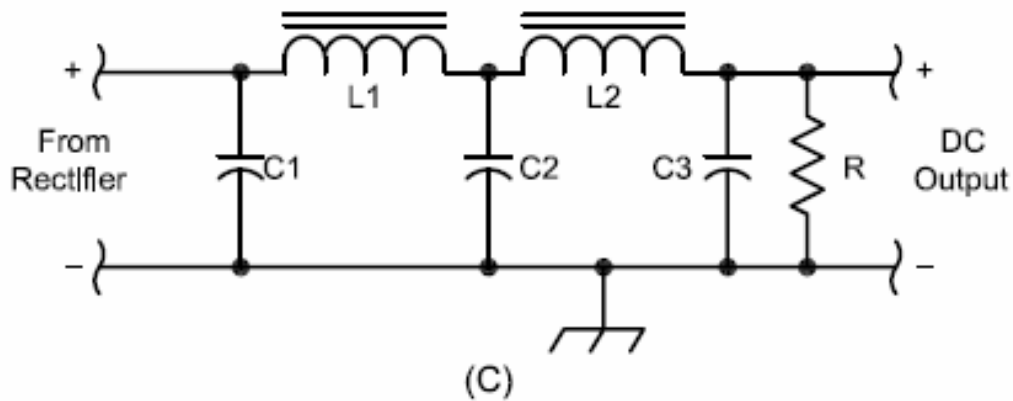
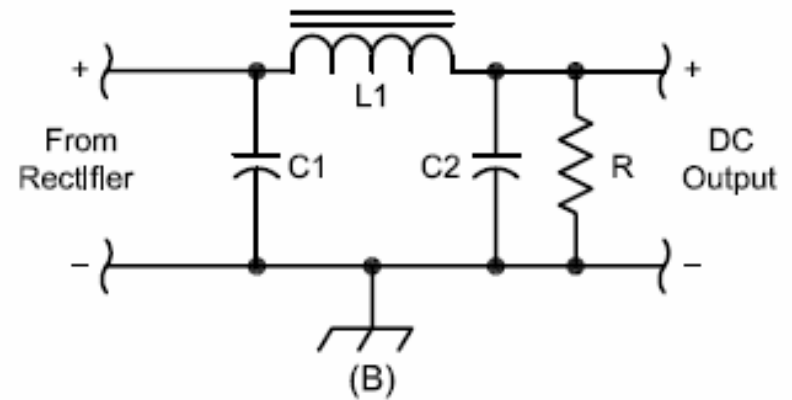


Figure 2: Smoothing

Filtering

- The **capacitor stores energy** when the pulsating DC is high, and **delivers it to the load** when the DC voltage falls.
- Ensure that the capacitor has a working voltage of at least **1.5 times** that of the power supply.
- “**AC hum**” is a sign that the filter capacitor is failing.
- A “**bleeder resistor**” should be placed across the terminals of the capacitor to safely discharge it when the supply is turned off.
- When extra filtering is required, additional capacitors and inductors are used.

Filtering

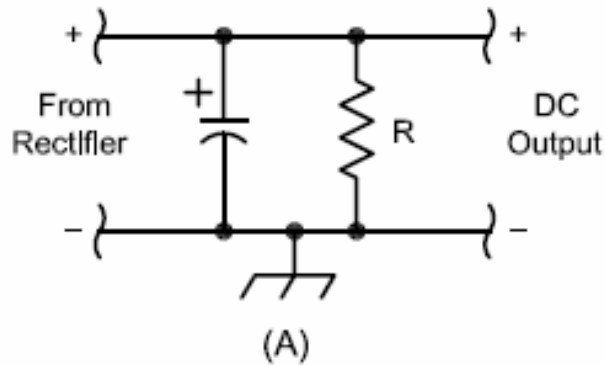


Regulating Voltage and Current

- The **output voltage** will tend to **drop** when a **load is applied**.
- A **regulator circuit** will ensure that the **voltage stays constant** when a heavy demand is placed on the supply.
- It works by acting as an **electronically variable resistor** between the filter and the output. As DC output voltage rises, resistance increases, and vice versa.
- Do not try to exceed the maximum output of the power supply!

Zener Diodes

- A **Zener Diode** is a type of diode that permits current in the forward direction like a normal diode, but **also in the reverse direction** if the voltage is larger than the breakdown voltage known as the "**Zener voltage**".
- Important components of voltage regulation circuits.
- When **connected in parallel** with a variable voltage source so that it is **reverse biased**, a Zener diode **conducts** when the voltage reaches the diode's **reverse breakdown voltage**. From that point on, the relatively low impedance of the diode keeps the **voltage across the diode at that value**.

Zener Diodes

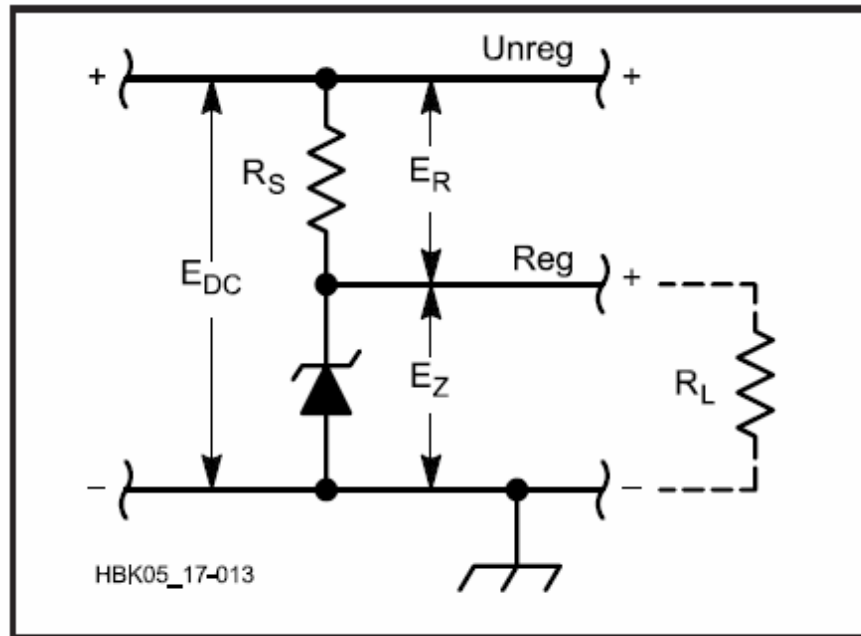

Zener-diode voltage regulation. The voltage from a negative supply may be regulated by reversing the power-supply connections and the diode polarity.

Chirp


- A **poorly regulated power supply** can cause the transmitter **frequency to vary** as the radio is keyed.
- When this happens with a CW signal, the resulting frequency change is called a **chirp**.
- Check the **regulation of your power supply** if you receive a report of chirp.

Monitoring the Output

- Good commercial power supplies include a **voltmeter** and **ammeter** to monitor voltage and current.
- Homebrew power supplies should also incorporate voltmeters and ammeters.

Monitoring the Output

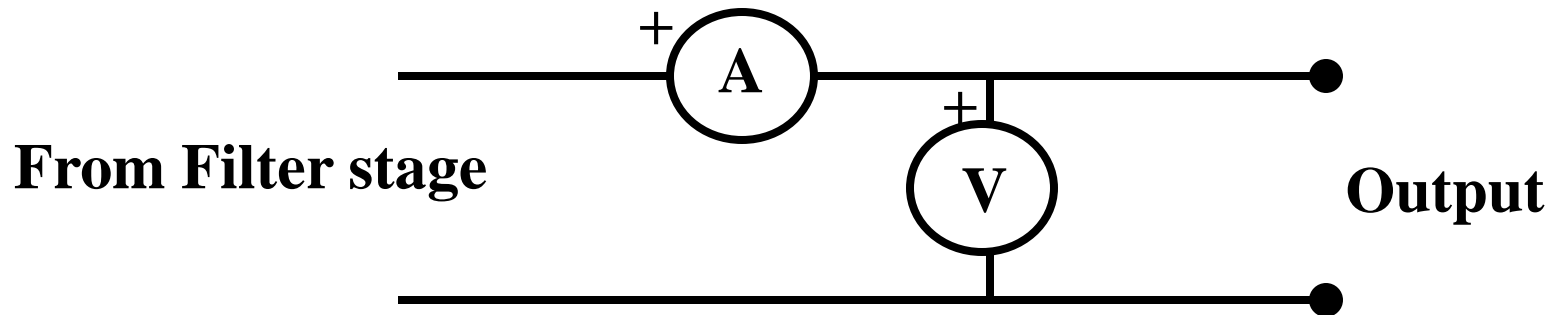- **Voltmeters** are connected **in parallel** with (ie: across) the output of the power supply. Ensure that the meter's polarity is correct.
- **Ammeters** are usually placed **in series** with the positive output terminal, but can also be placed in the negative return line.



Switching Power Supplies

- **Switching Power Supplies switch a power transistor between saturation (full on) and cutoff (completely off) with a variable duty cycle whose average is the desired output voltage.**
- **Switching rate is in the range of tens to hundreds of kHz, which can cause electronic “noise” on receivers.**
- **Advantage is that they are much lighter and smaller than conventional power supplies, but they are more complex.**
- **In widespread use nowadays.**

Questions?

TF4RX01JB
COMMUNICATION
ACCESSORIES CO.
94 0654 00

TF4RX01JB
COMMUNICATION
ACCESSORIES CO.



WWW.DG2KBC.DE

Al Penney
2004/ 8/ 6 4:28pm
VO1NO