

Advanced Course: Ch. 4 Amplifiers

de VE1FA, 2019

Objectives

- define audio + radio frequency signal amplification
- how small signals are amplified
- linearity
- classes of amps, and where they are used
- active devices used in amplifiers:
tubes + transistors/integrated circuits

Amplifier- a circuit containing a DC power-consuming active device which increases the voltage (E), current (I), or power (W) of a DC or AC audio or RF signal.

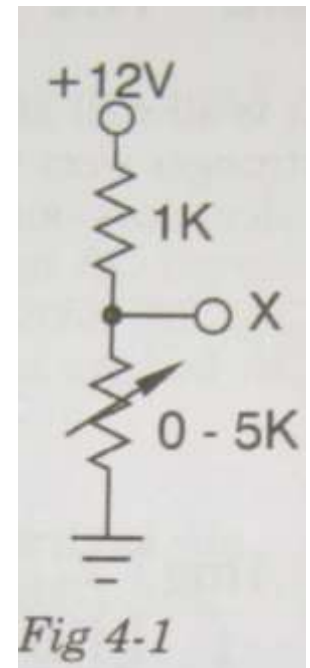



Fig 4-1

-one of the most important functional units in electronics

Active device: a power-consuming device that amplifies or modulates a flow of electrons


Transistors

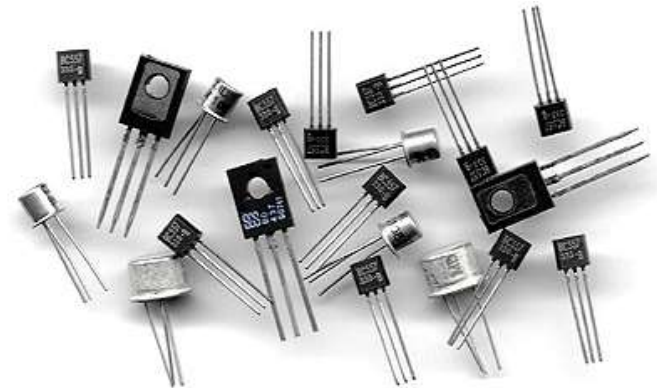- a. Bipolar: NPN and PNP
- b. Field effect: JFET and MOSFET
- c. Integrated circuits = integrated transistor/diode circuits



3. Vacuum tubes, or valves

- a. Triodes
- b. Tetrodes
- c. Pentodes

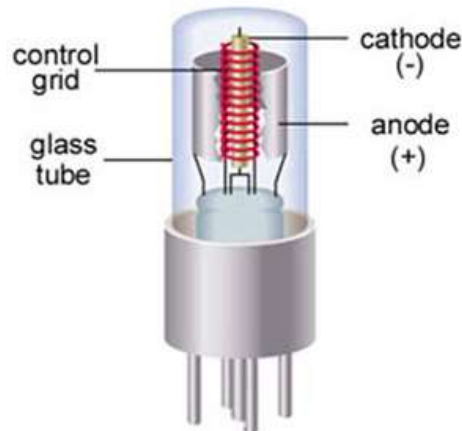

Transistor (NPN, Si) amplifier: calculating currents


$$I = E/R$$

Collector $I = E/RL = 5.0/1000 = 5.0\text{mA}$

Base $I = E/RB = 9.3/93000 = 0.1\text{mA}$ (DC bias)

Emitter $I = IC + IB = 5.1\text{ mA}$

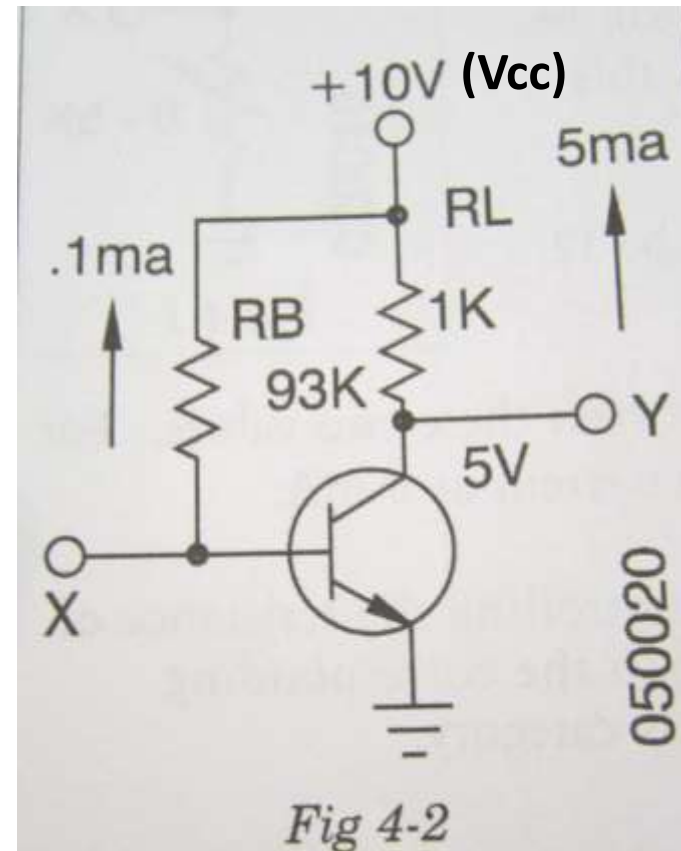$hFE = \text{beta } (\beta) = IC/IB = 5.0\text{ mA}/0.1\text{ mA} = 50$



X (base) to ground PN junction drop: 0.7 VDC


-input signal inserted between X and ground

-output (amplified) signal appears between Y and ground

This is a common emitter amplifier


What does each component do?

What do the abbreviations stand for?

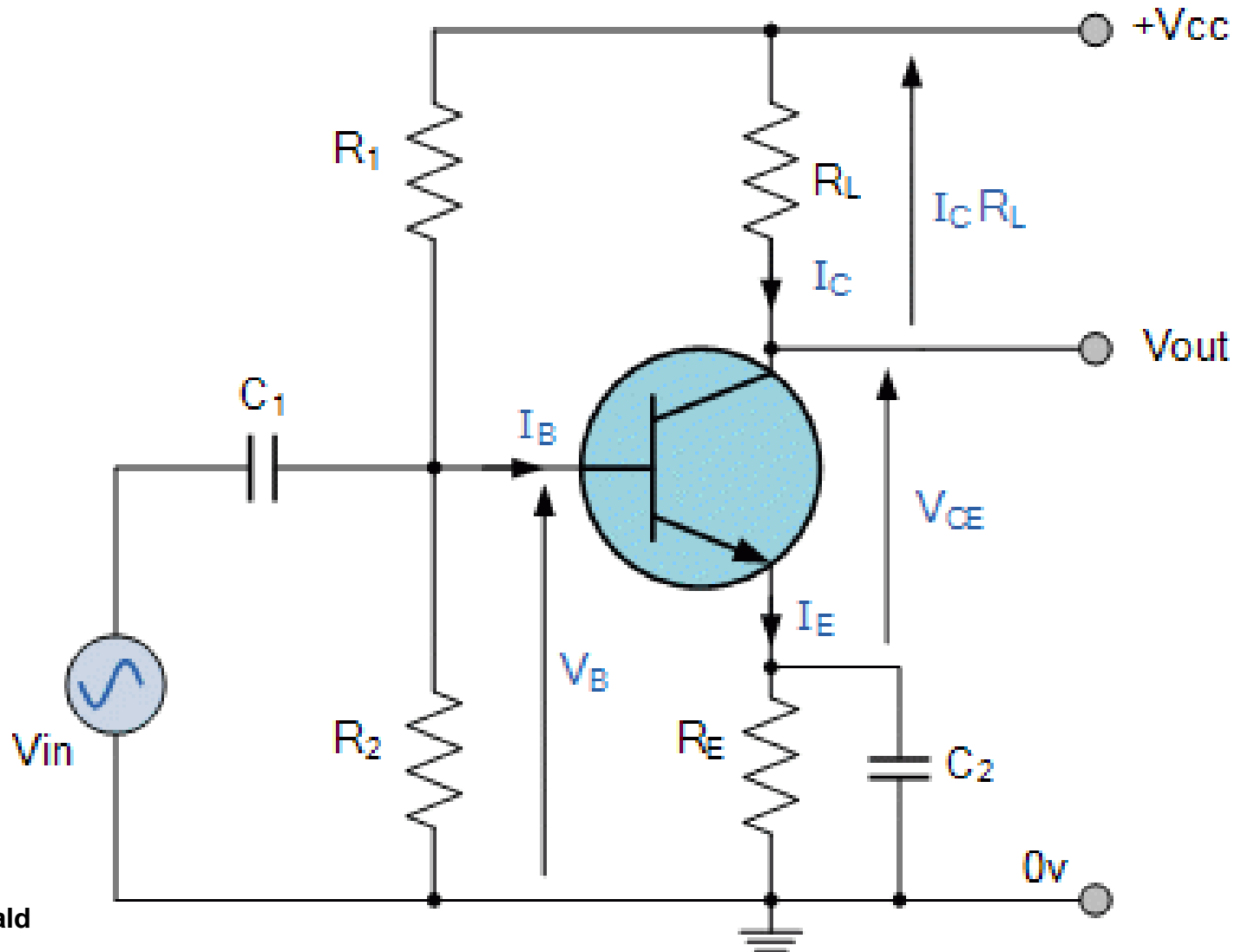

Transistor behavior must be understood to design an amp

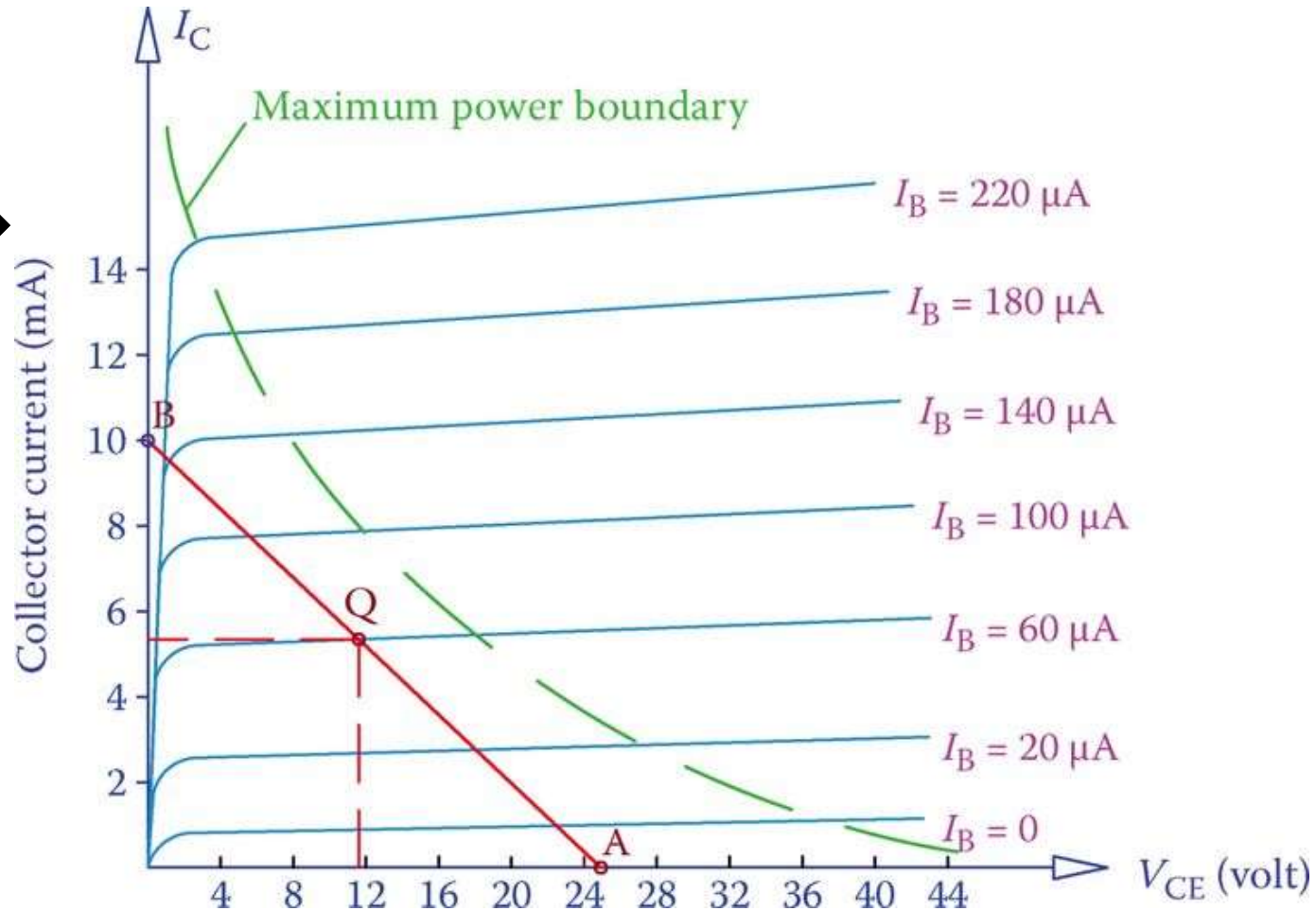Family of
“characteristic
curves” →
e.g.: 2N2222



I_C nearly independent of V_{CE} ,
 I_C nearly totally dependent on I_B

Q: good operating or bias point for “Class A” linear amp

Characteristic curve of a particular transistor type showing “class A amplification”, also called the “linear transfer characteristic”


* Output signal can be in current (IC) or voltage (VCE)

A → B = DC load line

Input sig: 60 uA p-p

Output sig: 2000-7700 uA p-p
or 2.00-9.34 V p-p

If $R_L = 1.2\text{ k}\Omega$

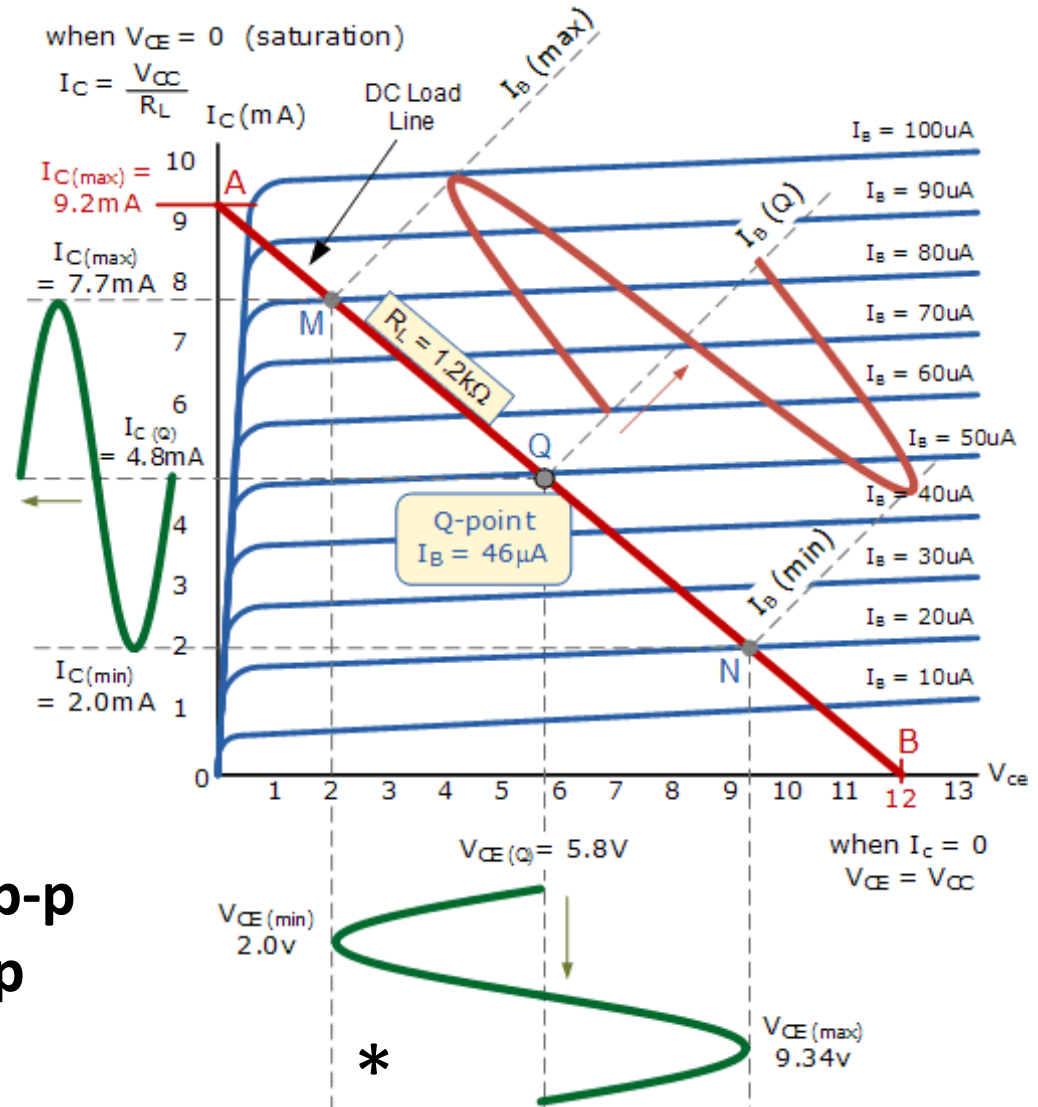

Class AB bias on push-pull amplifier (showing one of two transistors)


Bias poises transistor **ABOVE** the cutoff point, where gain is linear with input signal

-dead zone (producing crossover distortion) is avoided

-moving bias to middle of DC load line would give Class A operation

-moving bias down to $I_C = 0$ (the cutoff point) would produce Class B bias

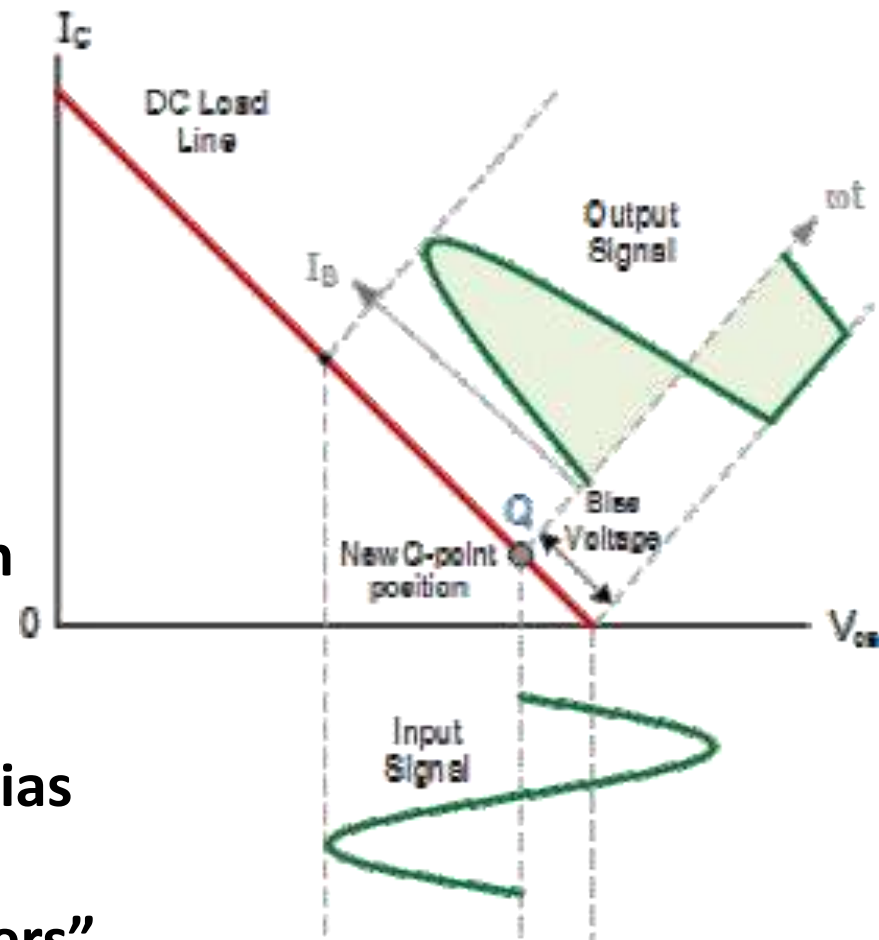-SSB (transceivers and “linear amplifiers” are biased AB



One electrode is always common to both input and output circuits in an amplifier.

This applies to FET, bipolar transistors and tubes.

Common Element	Emitter	Collector	Base
Input Element	Base	Base	Emitter
Output Element	Collector	Emitter	Collector
Voltage Gain	High (200 - 1000)	Low (< 1)	Medium (25 - 50)
Current Gain	High (25 - 300)	High (25 - 300)	Low (< 1)
Input Impedance	Medium	Very High	Low
Output Impedance	Medium	Low/Very Low	High
Phase Reversal	Yes	No	No
Power	High	Low	Medium


Fig 4-5

**Usual
configuration**


**Emitter/Cathode/
Source follower**

**Grounded base
Grounded grid**

4.3 Classification Of Amplifiers

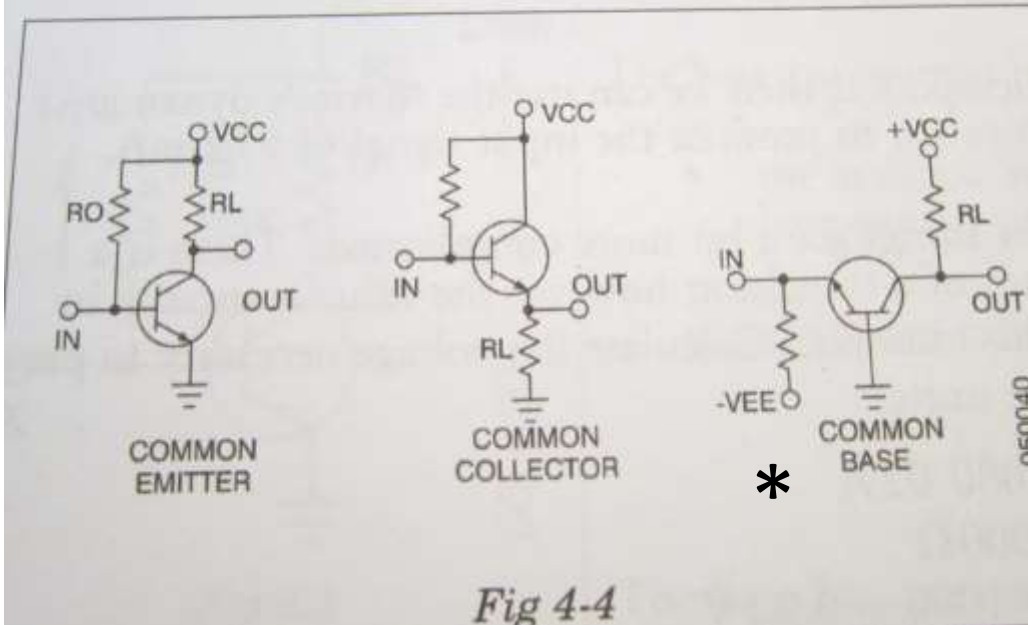

* Usually ground

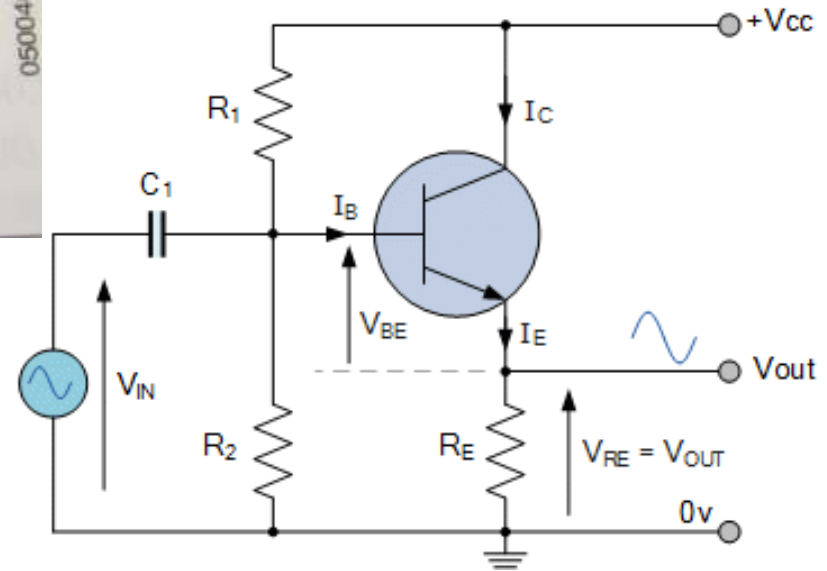


Common collector/emitter follower

- High Z to low Z converter
- V gain = 1 or less
- I and P gains: often quite high

Where you set the static bias on a tube or transistor determines the amp's CLASS of OPERATION Very important for amplifier's:

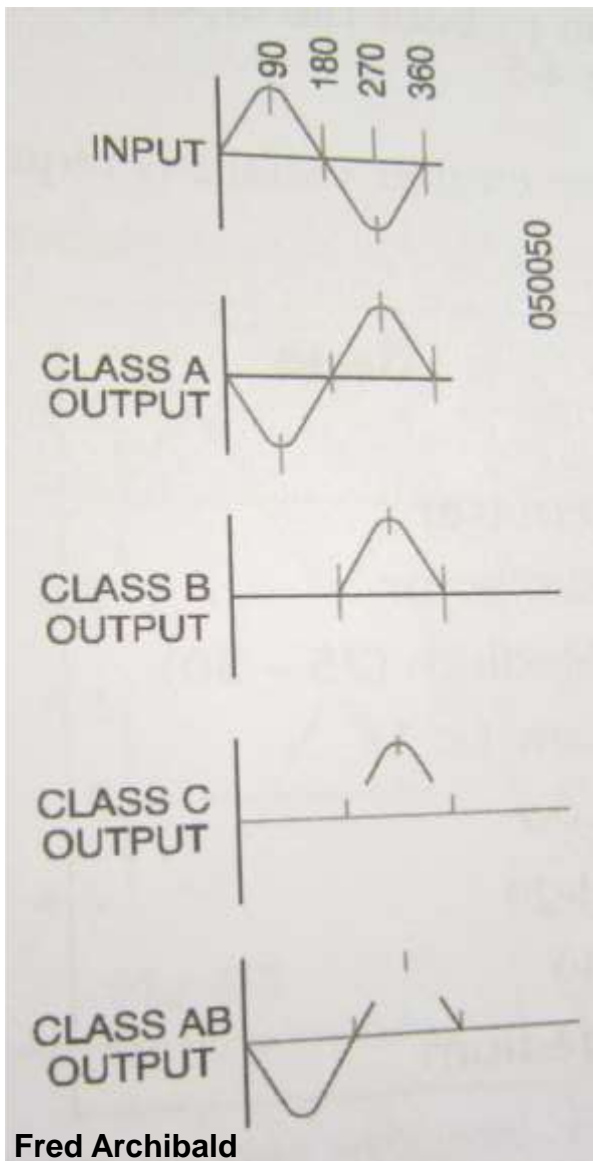- efficiency
- distortion
- harmonic content



	A	AB	B	C
Current Angle	360°	> 180° but < 360°	180°	< 180°
Distortion	Low	Medium	High	Extreme
Efficiency	Low	Better than A; worse than B	Moderate	High
Use	Audio	Audio Power	Audio Power/RF	RF Power


Fig 4-7
Class D + E ! F, G, H

* Wrong! Class AB almost always used for SSB

Above is outdated:

Now : classes D, E, F, G, H of operation

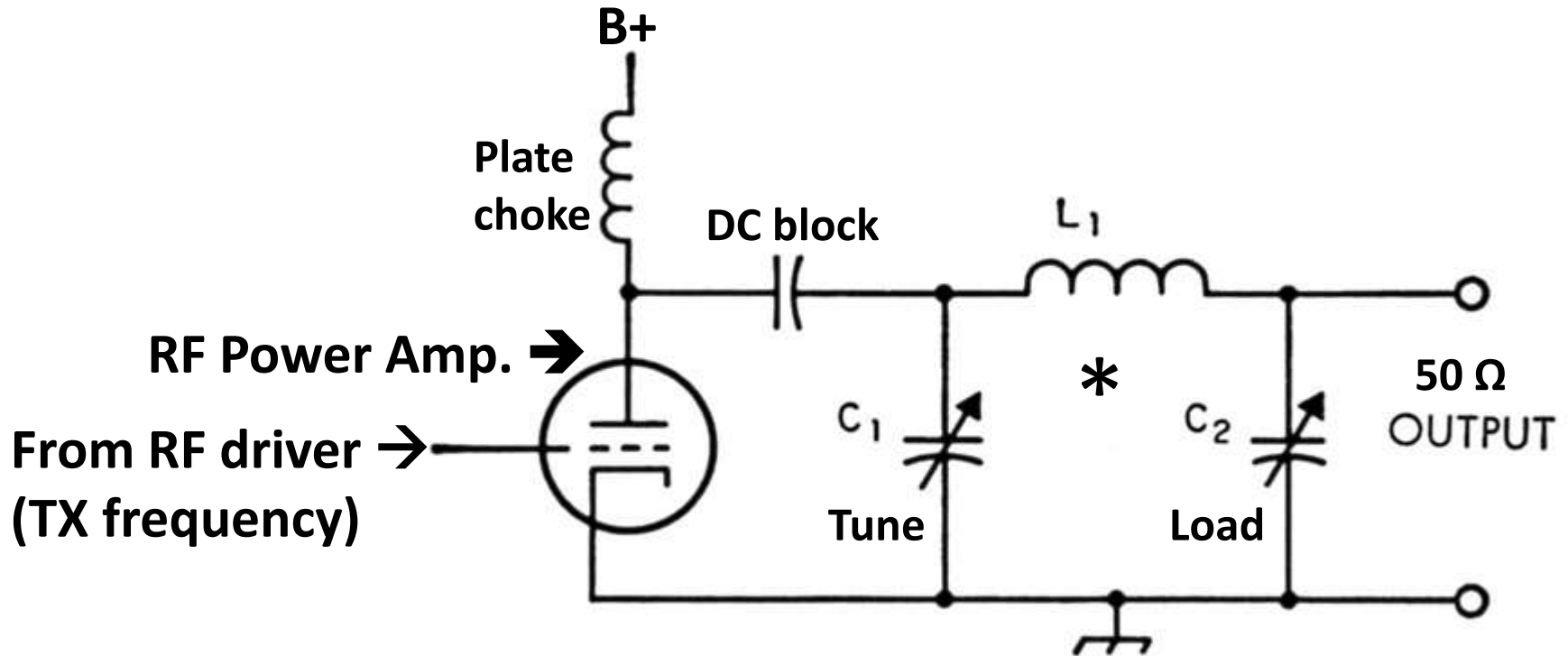Why bias class C can give a fairly clean RF output





* $C_1 + L_1 + C_2 = \text{flywheel} + \text{filter} = \text{"Pi" output or "tank" circuit}$

AM, FM, and CW usually biased class C for high efficiency

Class B push-pull amplifier

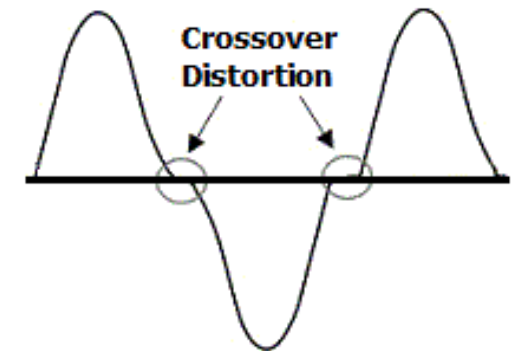
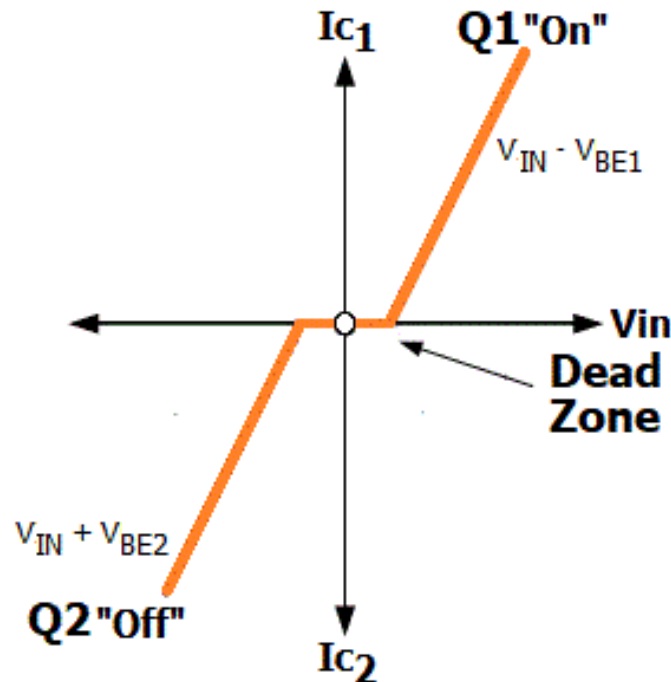
-usually has crossover distortion, due to non-linear response of tubes/transistors near cutoff



Output Waveform

Linear amp: needs = or > 180° amp conduction **Class B biasing**


Mild crossover distortion (below)

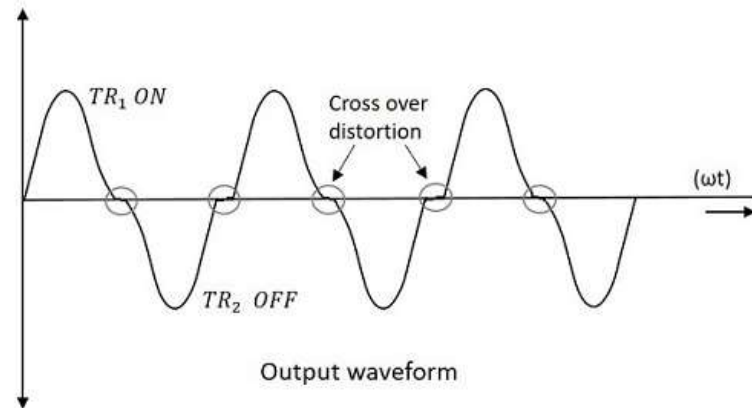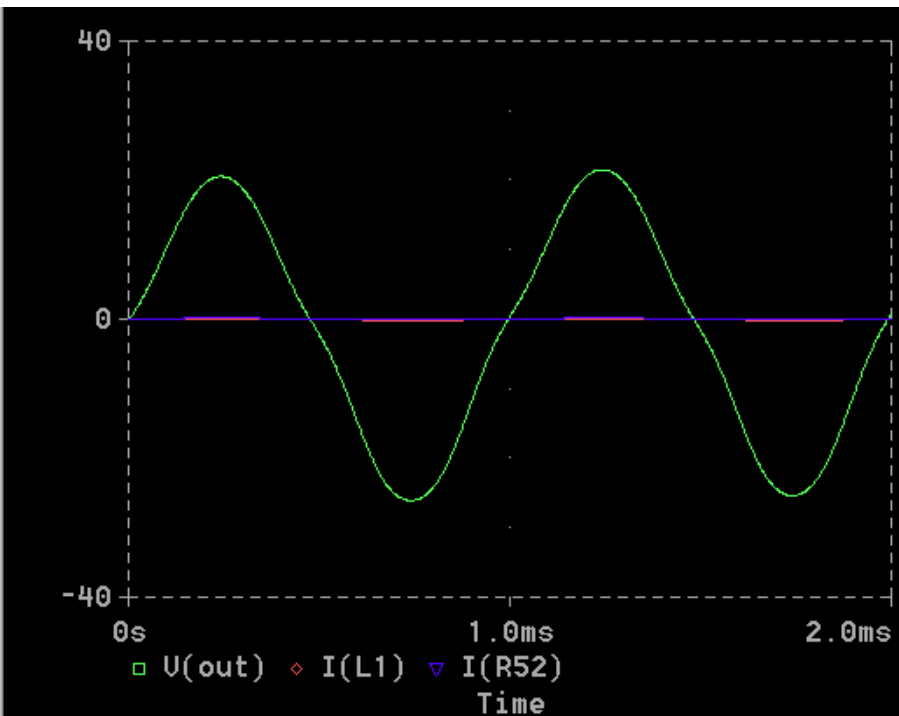

Class AB1 biasing →

Used in audio and RF linear power amps

Why not also in low-power amps??

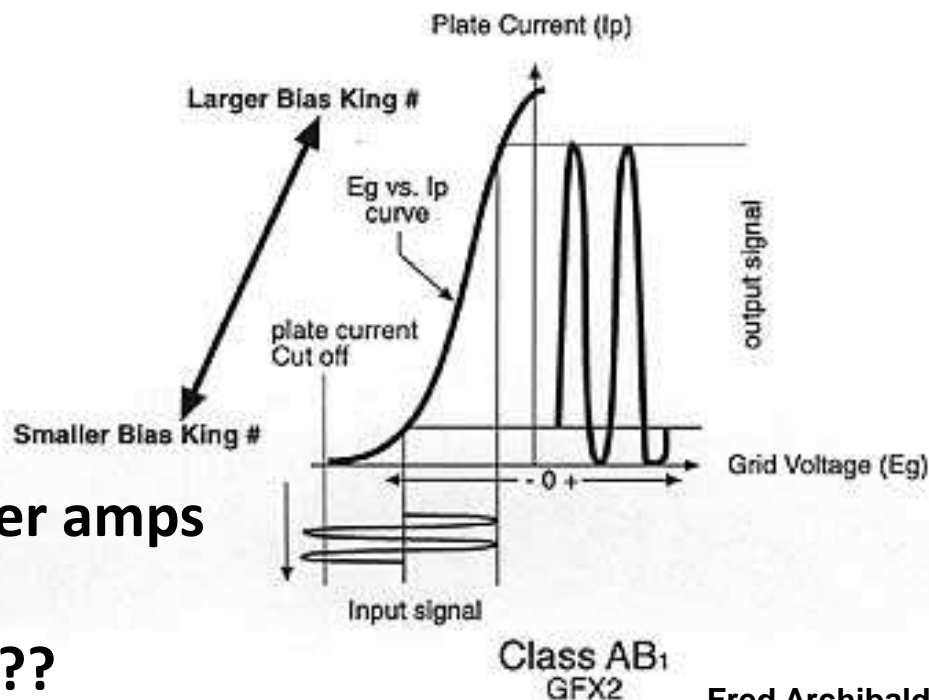

Newer modulation classes

Class D: -non-linear switching amp
-fast switching power MOSFETS
-up to 90% efficient

Class E + F: -power supply PWM (pulse width modulation)
-highly efficient (Nautel)
- RF applications

Class G + H: “Rail switching” class AB amps
-highly efficient


Purposes of RE, CIN, COUT

RE emitter resistor:


- makes bias more negative
- reduces chance of thermal runaway
- reduces gain of transistor, increases fidelity (degeneration)
- RE usually 10-15% of RL value

CIN + COUT

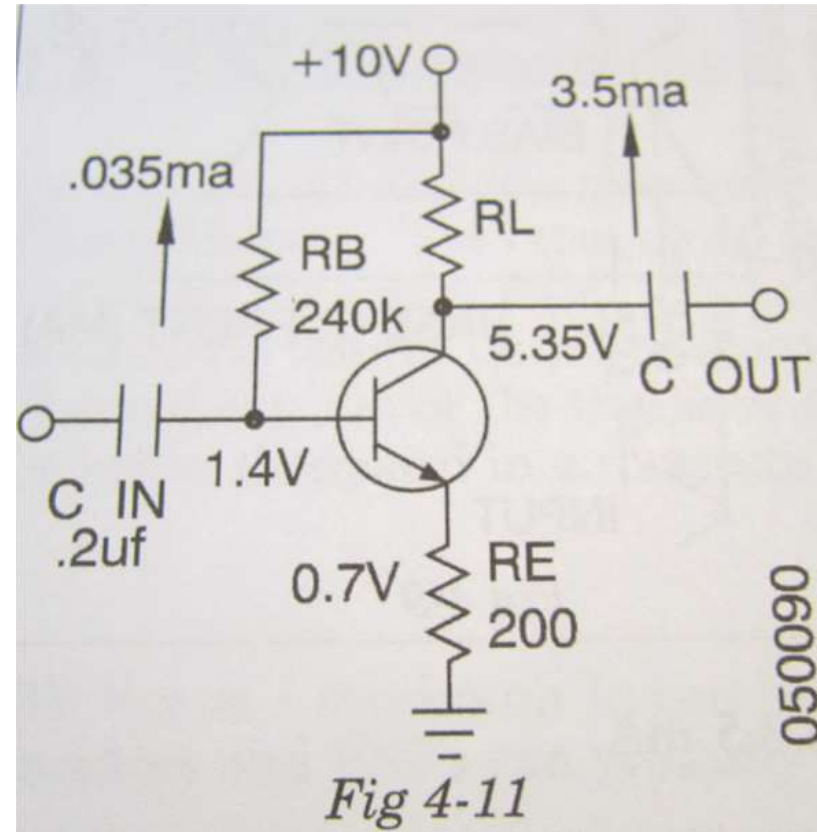- isolates DC operating power to just this stage
- passes AF and/or RF signals, depending on capacitor values




What does each component do?

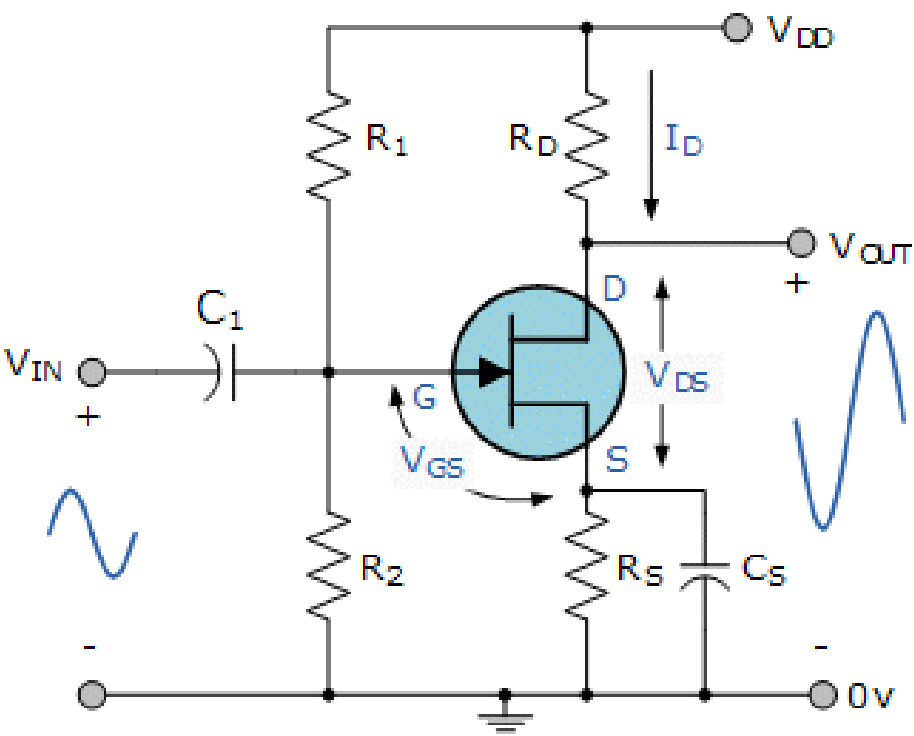

MOSFET small signal amplifier

JFET small signal amplifier

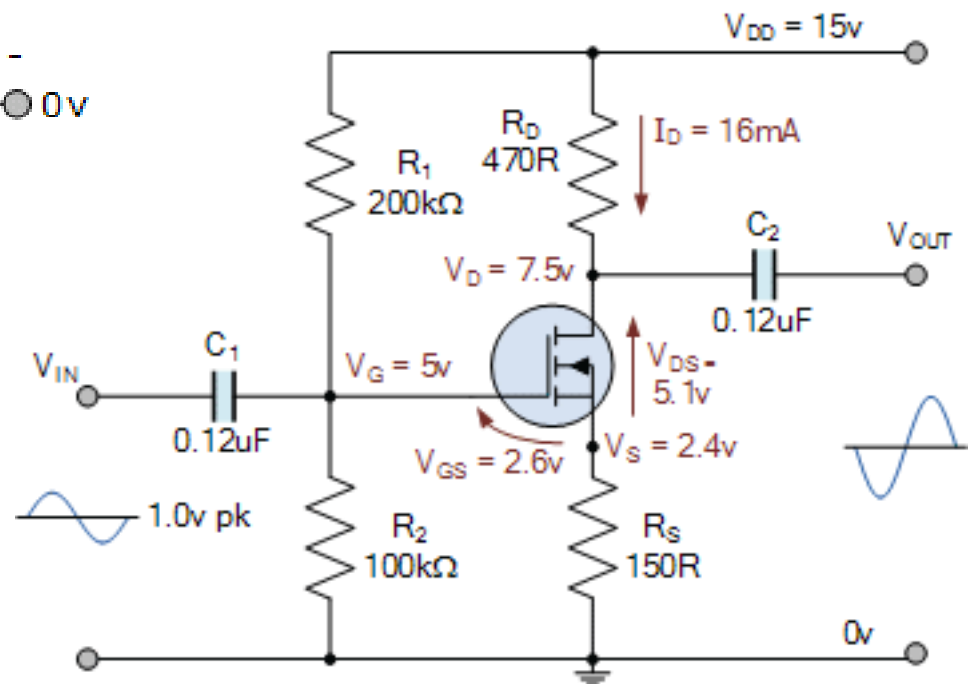

Basic tube (triode) small signal amplifier


R_b - plate load

R_c - grid reference
to ground

R_K - cathode resistor

R_{cf} - output load

C_o - DC blocking
output capacitor

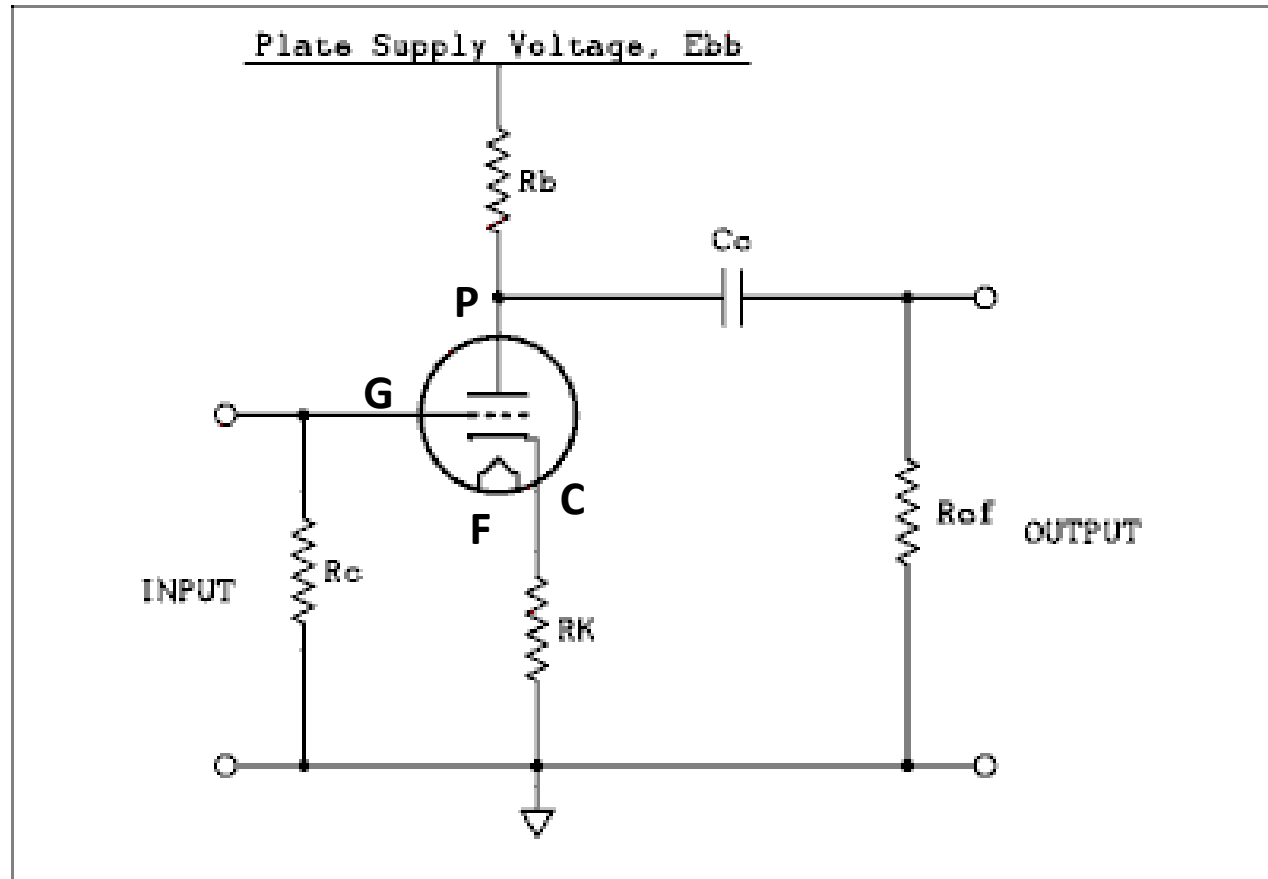

Common emitter amplifier

Transistor as a switch (on/off device)


-max (saturation) or zero amplification/current flow

$$PD = VCE \times IC$$

Alternative/adjunct to a mechanical relay

“Darlington pair”, often in one case

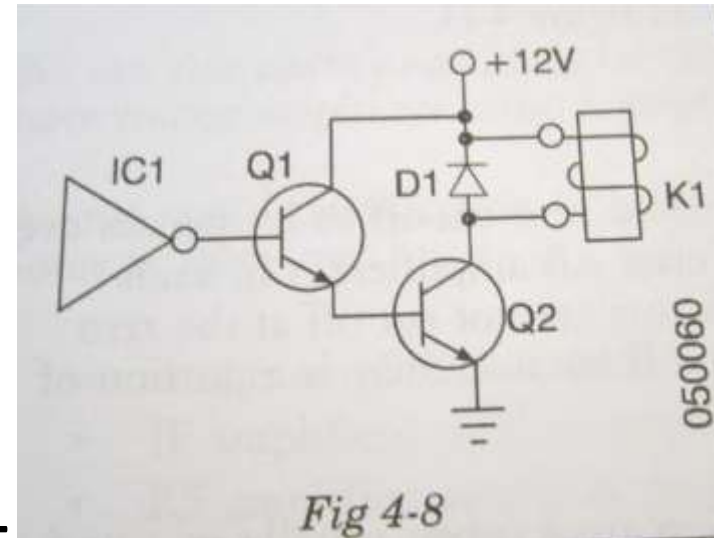Activating Q1+Q2 grounds/activates relay K1




High current transistor can replace relay

Very low power can switch high power


Power MOSFETs have near 0 resistance

when “on” →

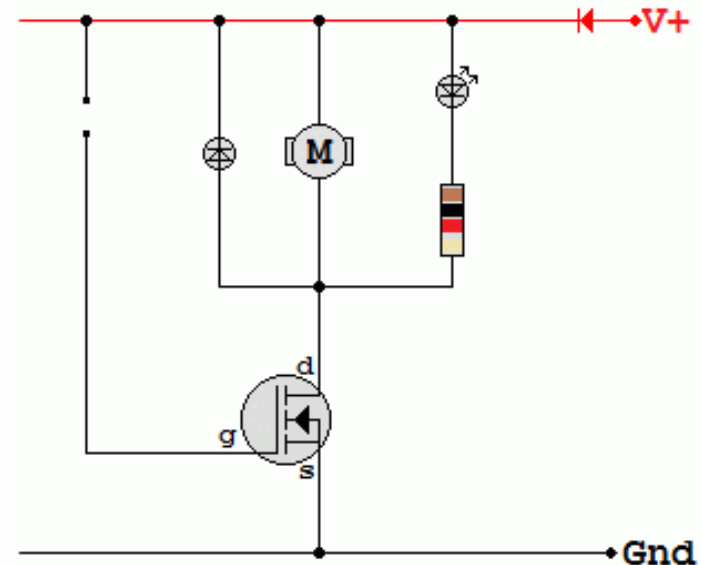

Class B biasing (one method)

Driver stage →

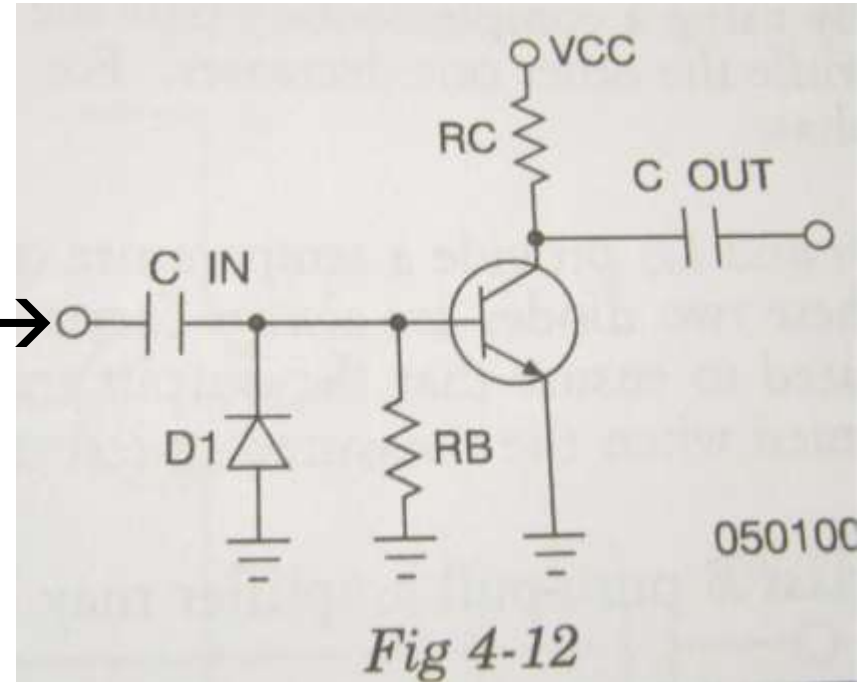

D1 is oriented opposite to the EB junction diode


This produces symmetrical load to driver stage
(if both diodes are Si or Ge,
and have similar properties)

RB sets base I at cutoff

The push-pull amp: when the final tubes/transistors are operated out of phase

-“totem-pole” style push-pull (PNP + NPN complimentary pair)

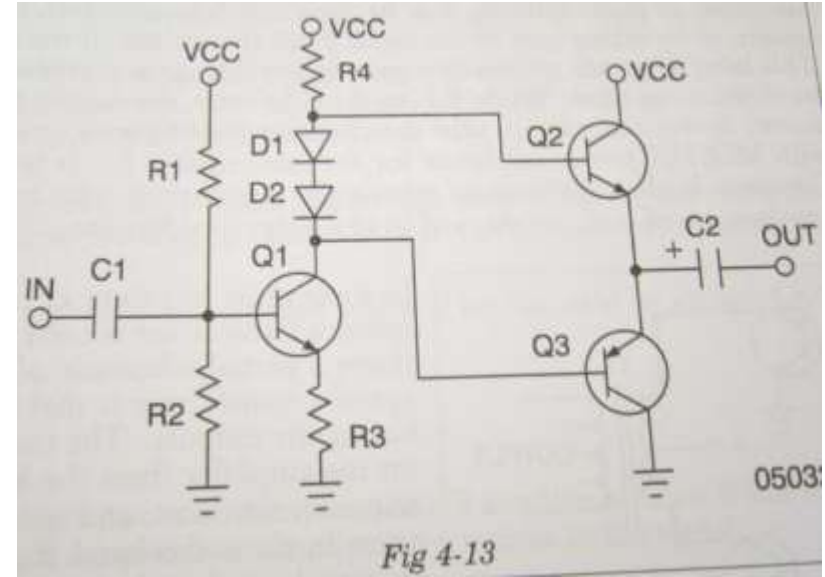-in complimentary pair, device characteristics match, but polarity is opposite



Transformer-type push pull amp


-common transceiver RF output stage

-common hi-fi audio output stage


- B1 provides correct Vcc (usually power supply, not battery)

-two devices (Q1 + Q2) share the output power

-bias: R1 + R2

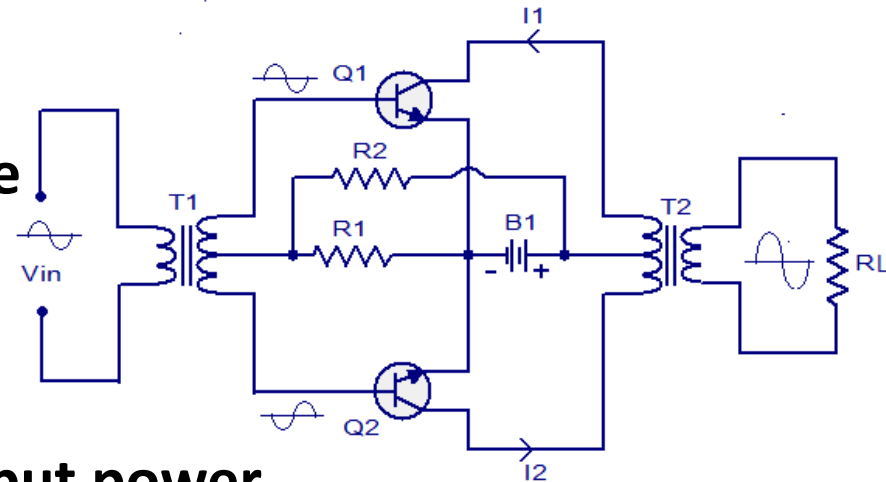

5W audio **push/pull amp**

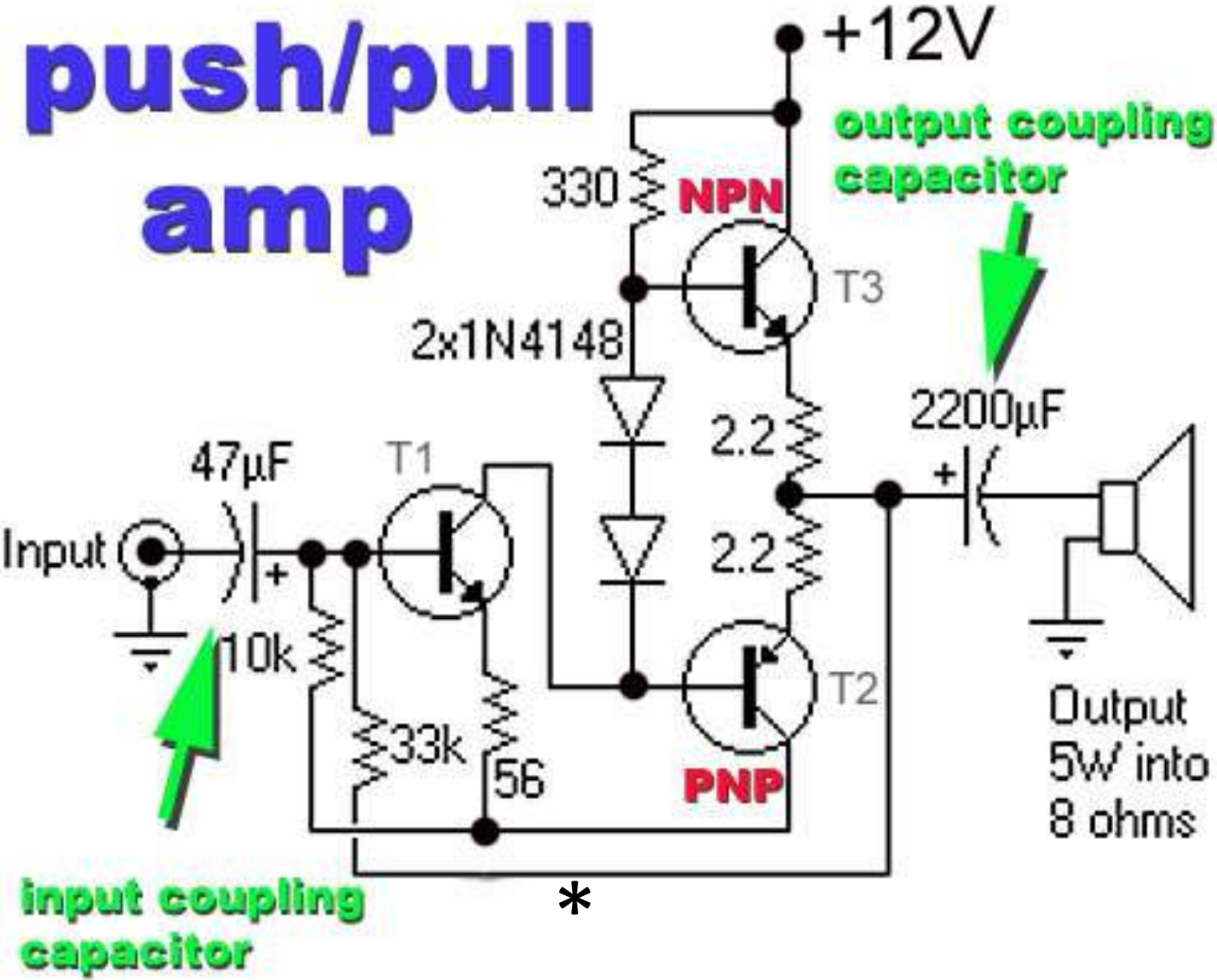

***Note negative feedback!**


Quasi-complimentary push-pull circuit

Similar to totem pole push-pull circuit, but power from matched NPN transistors

- extra stage = higher power out, if power transistors used
- C3: large value allows strong bass notes

-C2 isolates DC on Q1 from rest of amp

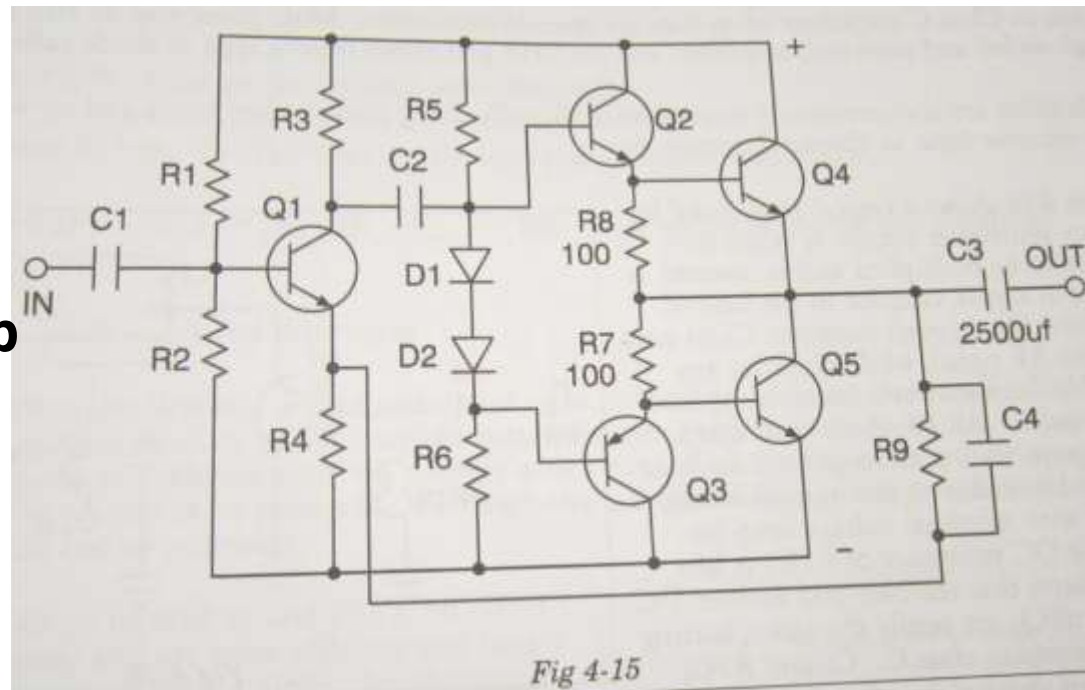- C4+R9: negative feedback loop
- 180° out-of-phase signal re-inserted at Q1.



Negative feedback: -reduces gain

-reduces distortion and noise

-increases stability and linearity

RF frequency multiplier amplifier


Can select a multiple of f_1 and amplify it

- uses class C bias to produce high distortion of f_1
- resonant circuit L_1+C_2 is tuned to a desired multiple of f_1
- eg: if f_1 =1.000 MHz, then output could be 2, 3, 4, 5, 6....etc. MHz
- the higher the harmonic (multiple), the less output is obtained at nf_1

- L_1+C_2 is load of Q_1

- C_3 references output to ground

- C_1 , C_4 isolate DC in multiplier.

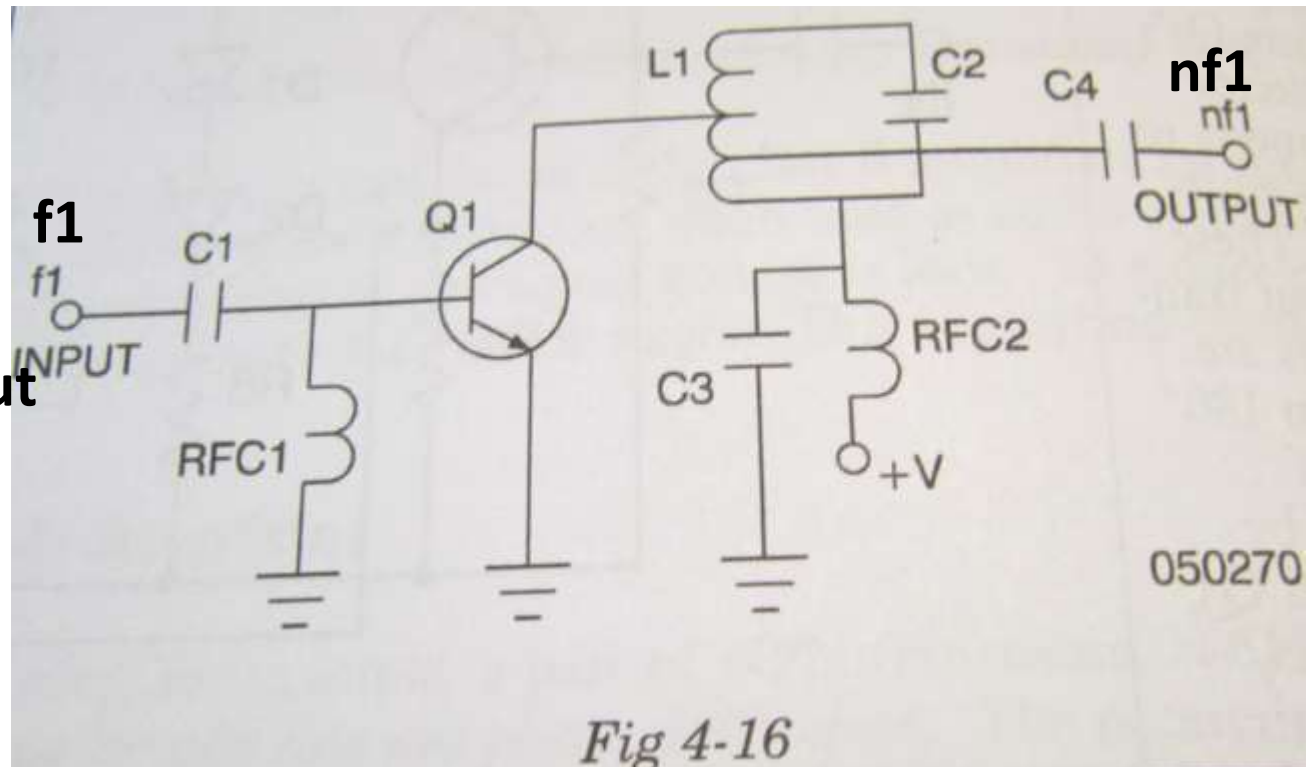

RF mixers

-RF mixer + local oscillator = “converter”

-non-linear circuit allowing 2 or more frequencies to mix and form products (sums and differences)

-key in all direct conversion and superhet RXs


-diode = basic mixer

Sums + differences produced: first order, second, third, higher order

Unbal. Mix: puts out both LO and input signal

Balanced Mix. : puts out either LO or Input signal

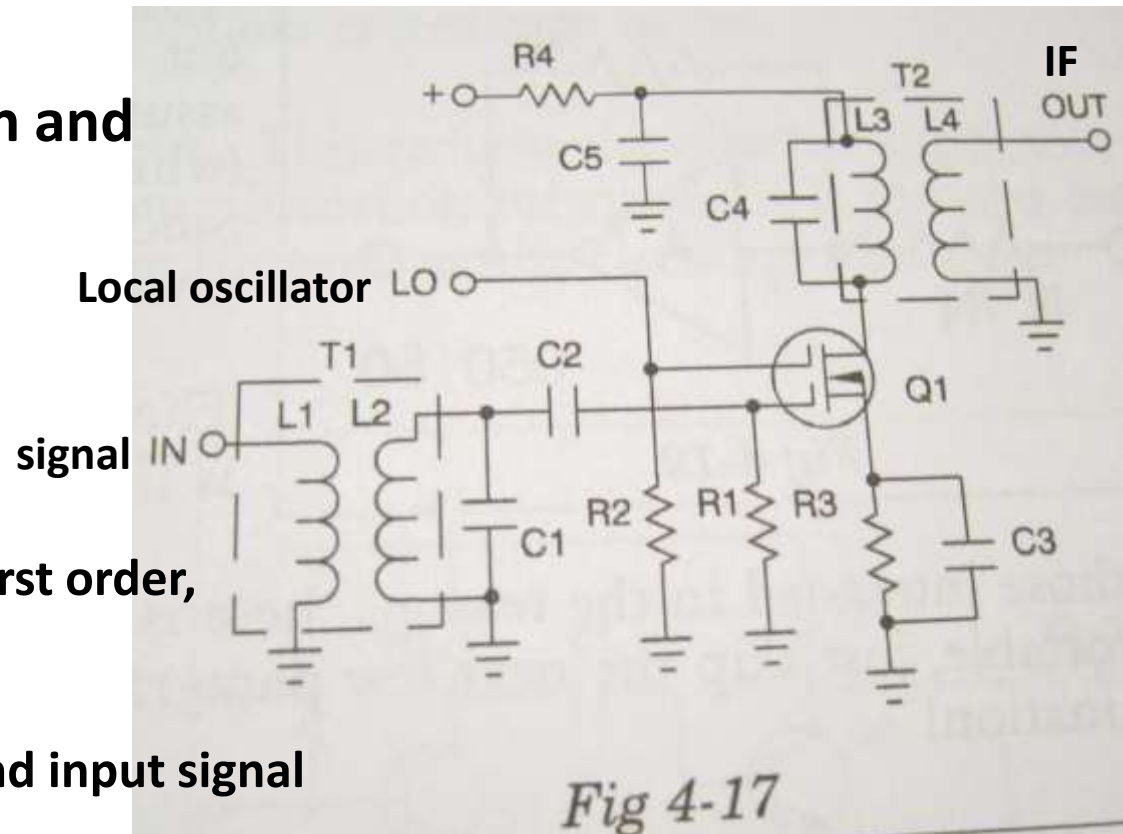Double Bal. Mix.: puts out neither LO or Input signal



“Unbalanced Mixer”

Single ended (unbalanced) vacuum tube mixer

Mixer products

f_s = received signal

f_o = local oscillator input

-many products, most unwanted (spurious)

-inputs still strong in output (no cancellation due to 180° phase shift)

-high order products are much weaker


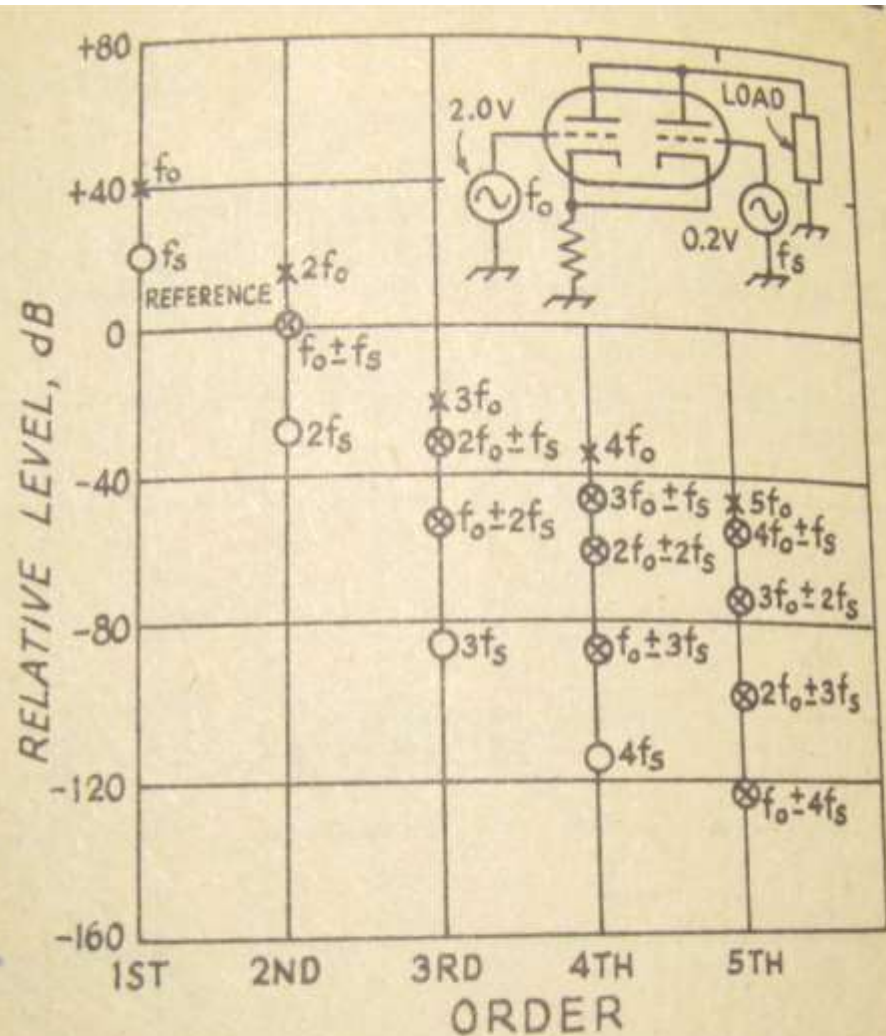


Fig. 8-14 — Chart showing the relative levels of spurious signals generated by a 12AU7A mixer.


Single-ended (unbalanced) tube mixer

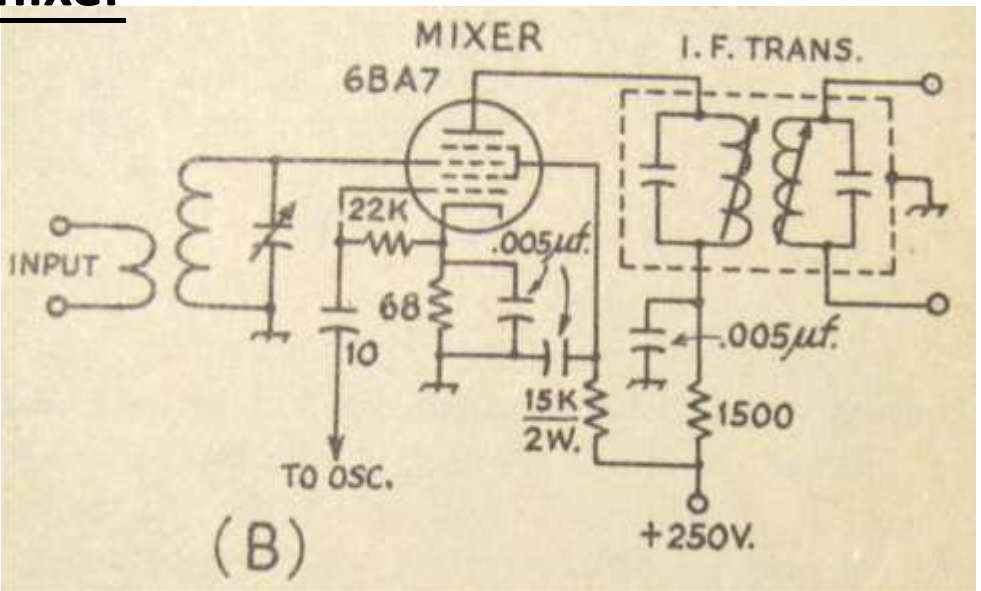- good mixer gain
- LO and signal are lightly loaded and not coupled to each other
- unbalanced
- poor dynamic range
- gainmultigrid tube = high noise



Diode ring mixer

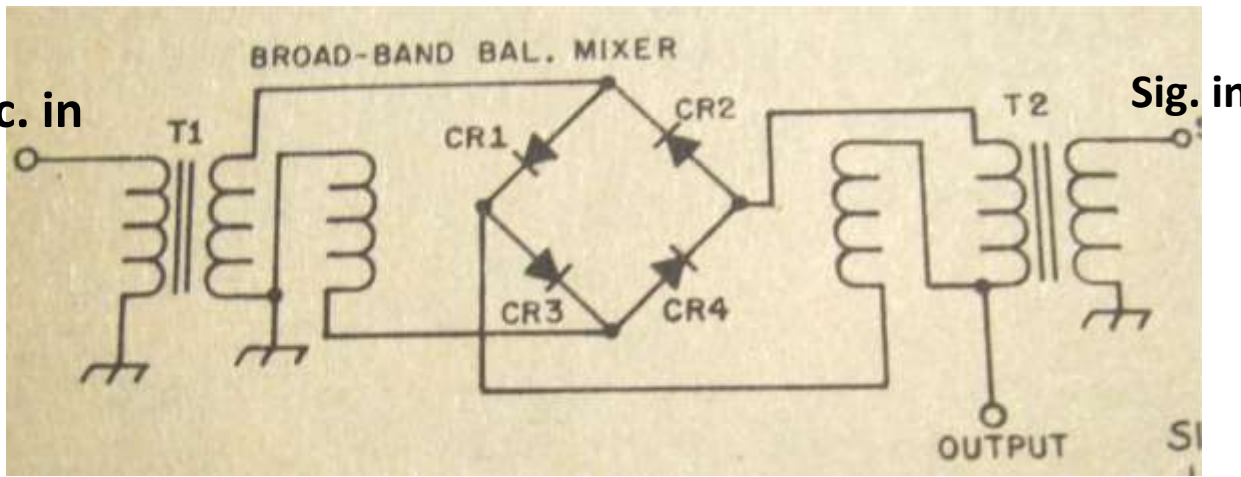- quiet (low noise)
- good dynamic range
- double balanced
- negative gain



Modern HF high performance RX mixer circuit (Kenwood TS-590SG, 2014)

Double-balanced "quad" mixer


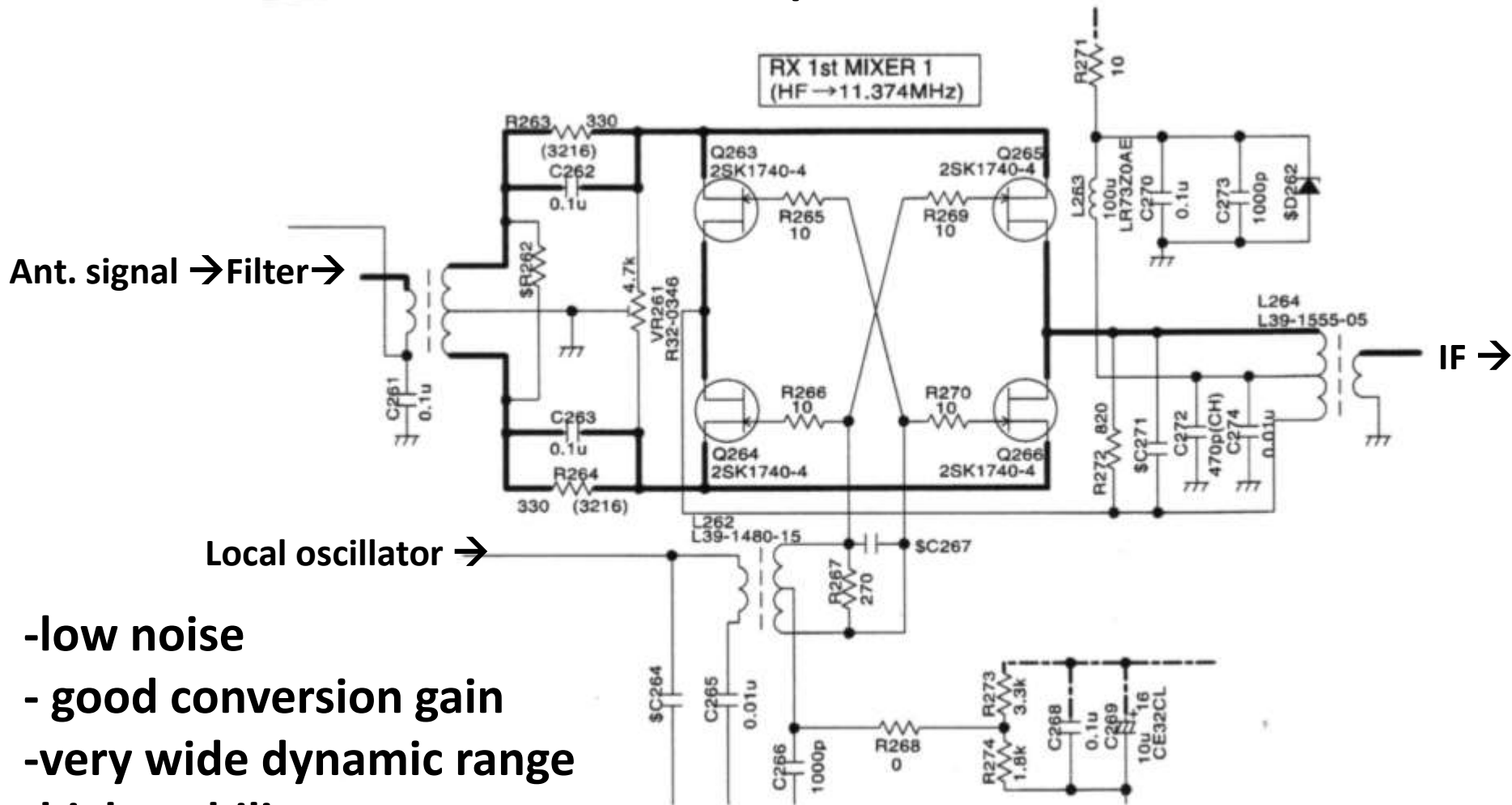


Figure 1-3 Receiver Mixer Circuit

Feedback: returning part of the output power of an amplifier to its input


Negative feedback

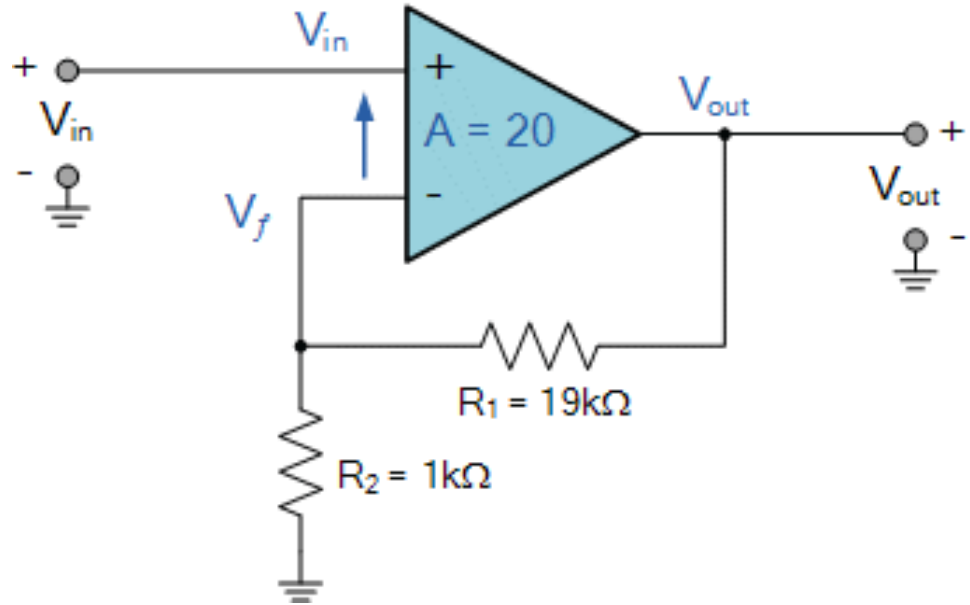- less gain + distortion
- increased stability
- less thermal drift



Positive feedback

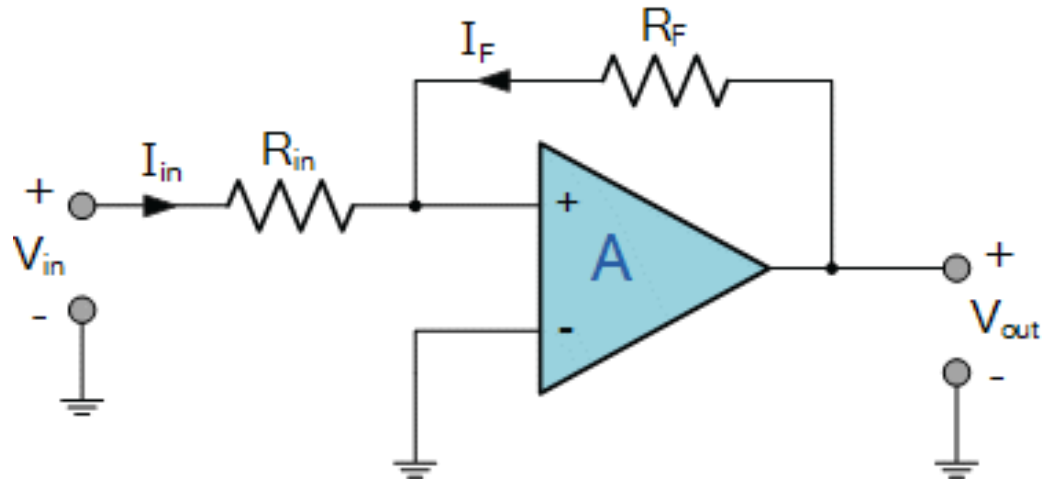- increased gain
- increased noise + distortion
- oscillator!



Feedback


Effective (closed loop) gain (ACL) = AOL – feedback (F)

AOL = open loop gain

ACL = AOL / (1 + AOL x F)

F = R_{IN} / (R_{IN} + R_F)

ACL = R_F / R_{IN}

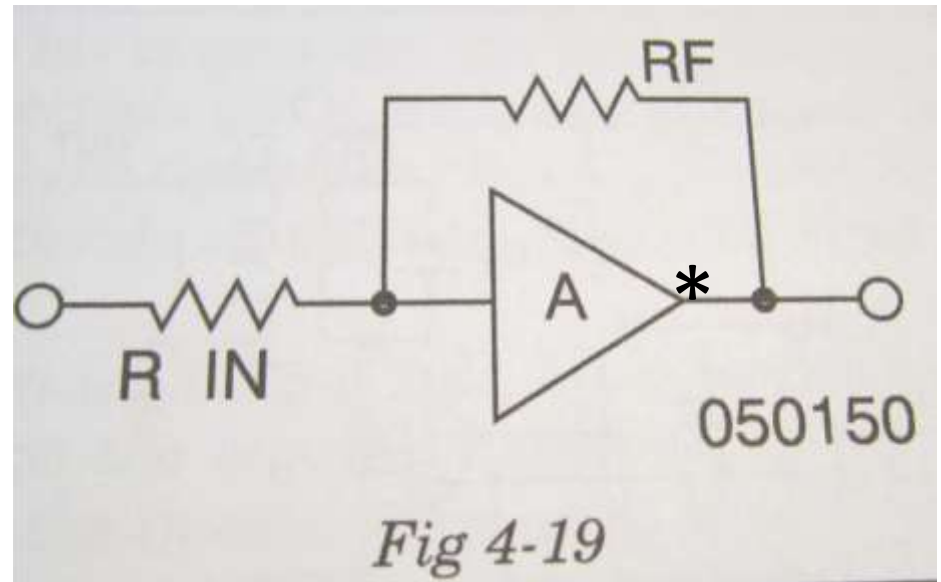


* Output is 180° out of phase with input

Amplifier Gain: can be expressed in I, V, P, or dB

Negative feedback over 2 stages

Feedback factor: $F = R2/R2 + R7$

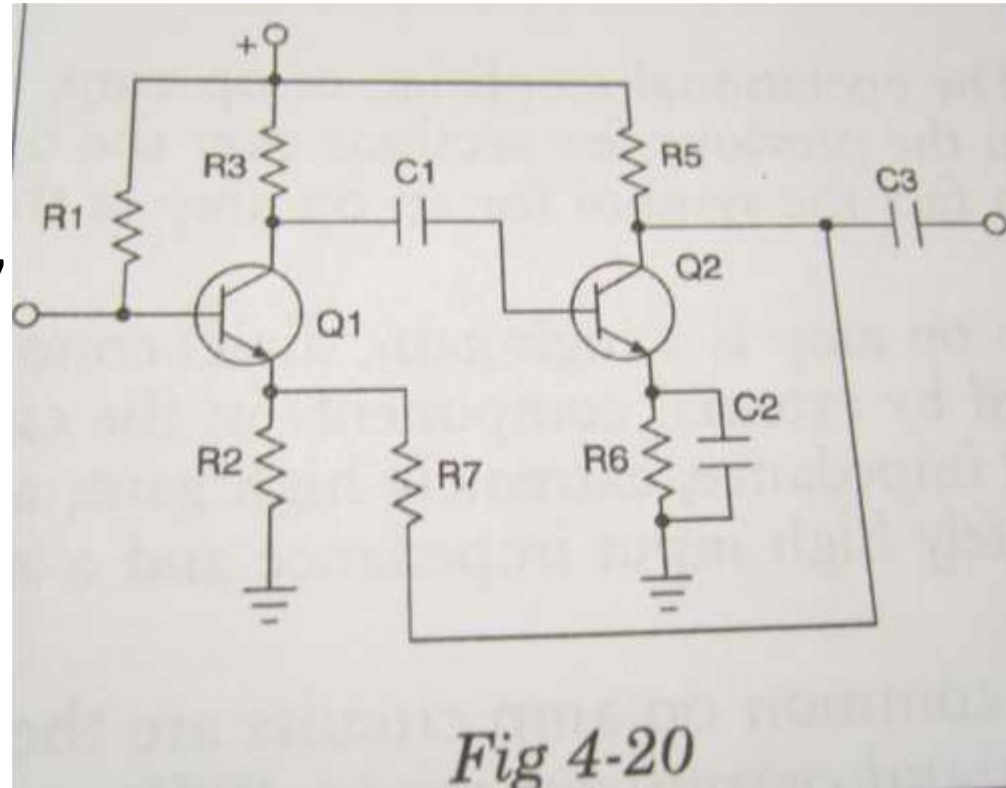

The “op-amp” analog integrated circuit

Output may swing either side of 0 if + and – DC supplies are used

Non-inverting (+) input: output is in phase with input

Inverting (-) input: output is 180° out-of-phase with the input


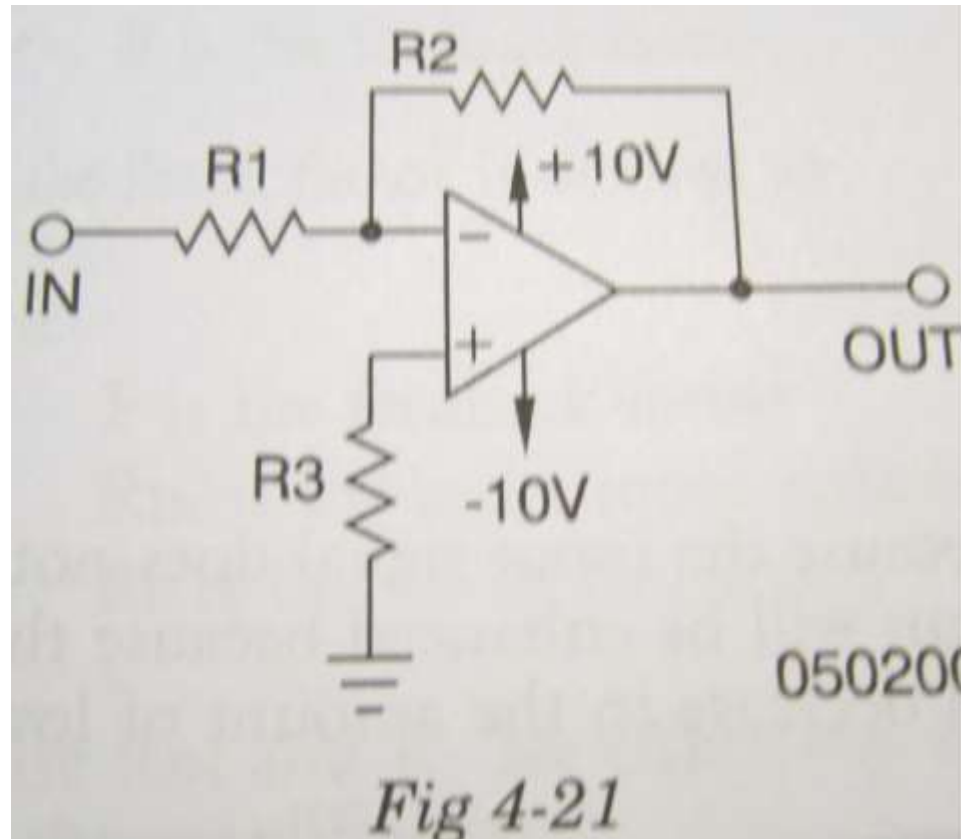


Fig 4-21

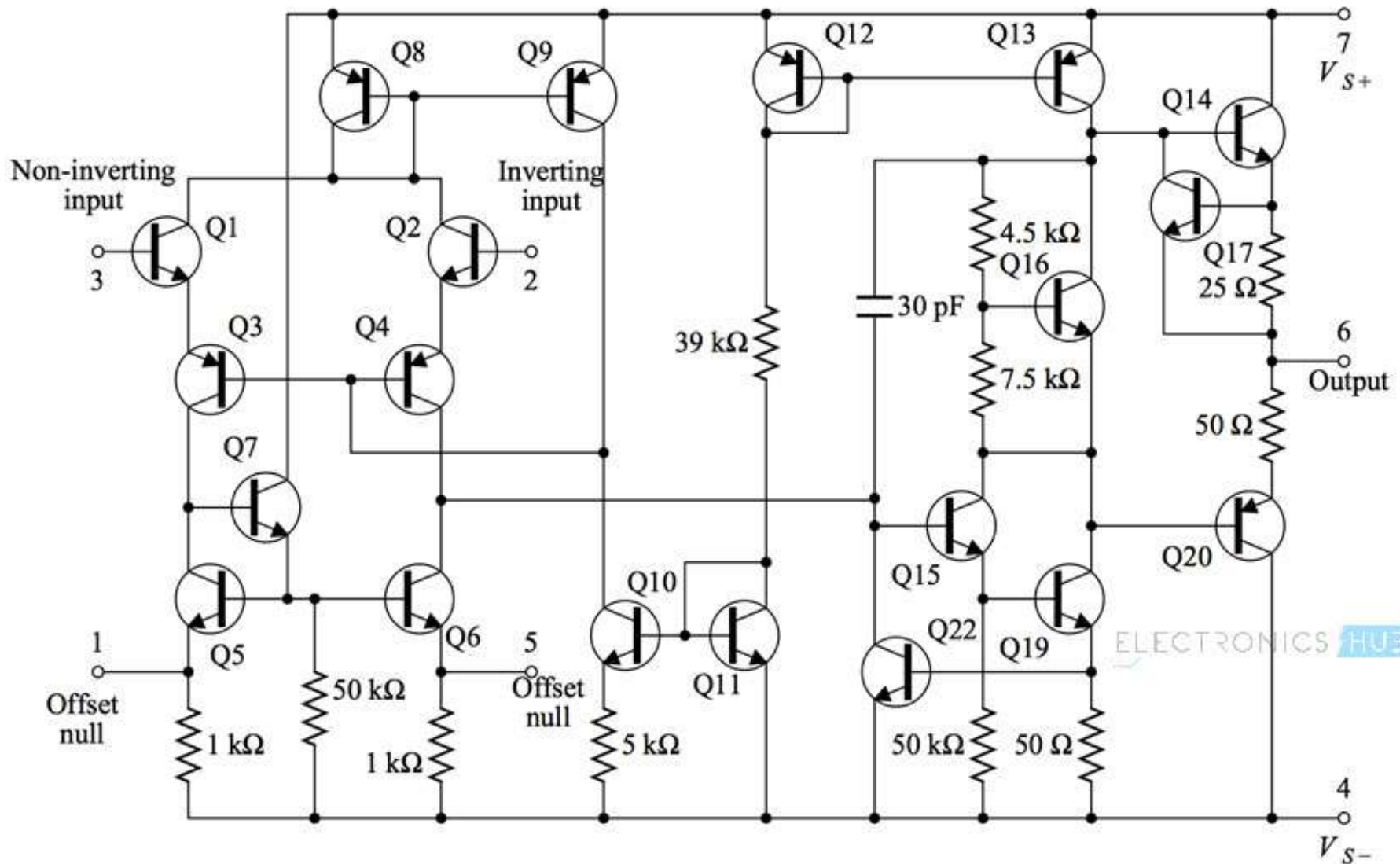
LM741 Linear Monolithic DC to 1.5 MHz integrated circuit (IC) operational amplifier, or “Op Amp”




22 NPN transistors, 11 resistors, 1 capacitor

741IC PIN CONFIGURATION


8-PIN MINI DIP

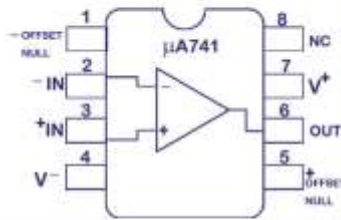


10-PIN FLATPAK

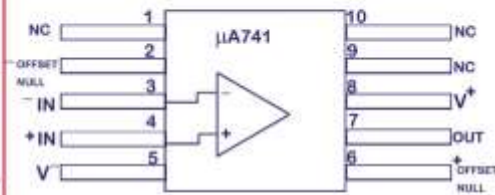



8-PIN METAL CAN

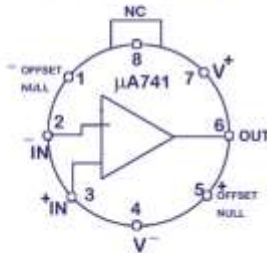

14-PIN DIP

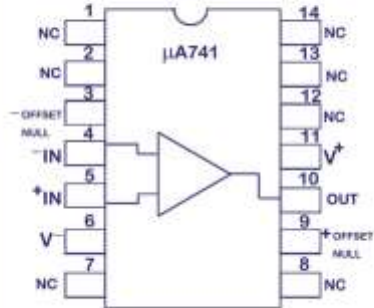


www.CircuitsToday.com

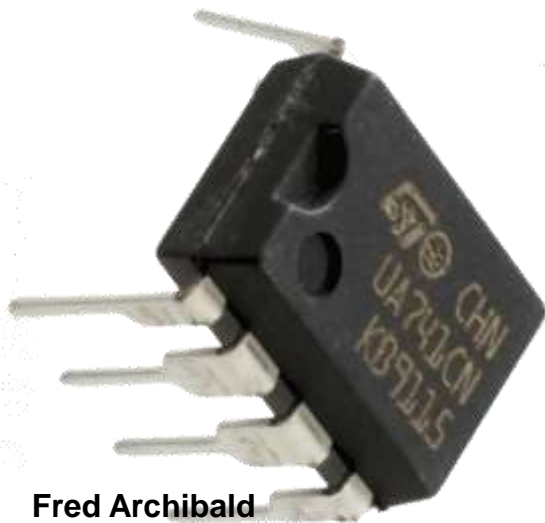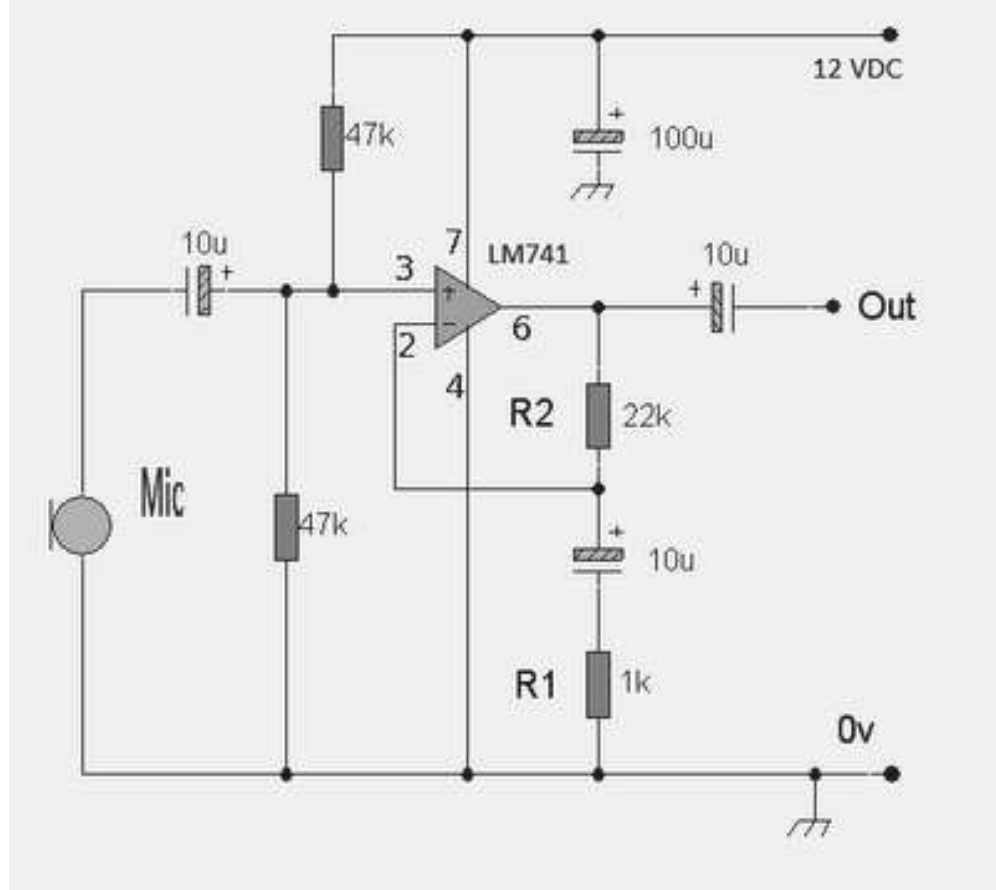

Fred Archibald
VE1FA


LM741 Pinout Diagram

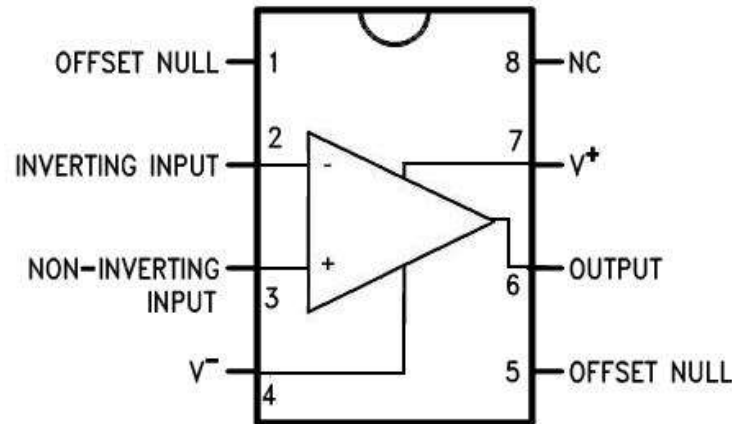


Operational Amplifiers (analog integrated circuits)

- older designs only good (low noise) to about 20 kHz and have slower slew rates
- typical “open loop power gain” = 200,000-400,000
- gain often reduced by (-) feedback to 1, 5, 10, or 50

Frequency-independent negative feedback

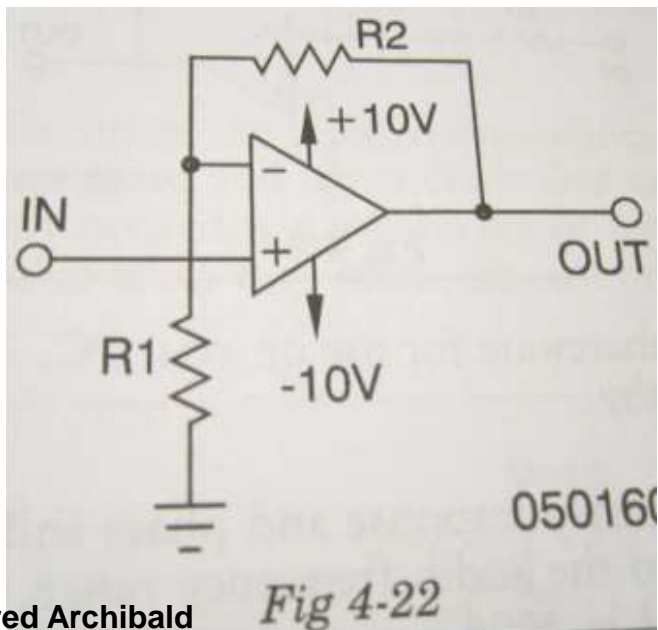


Frequency-dependent negative feedback

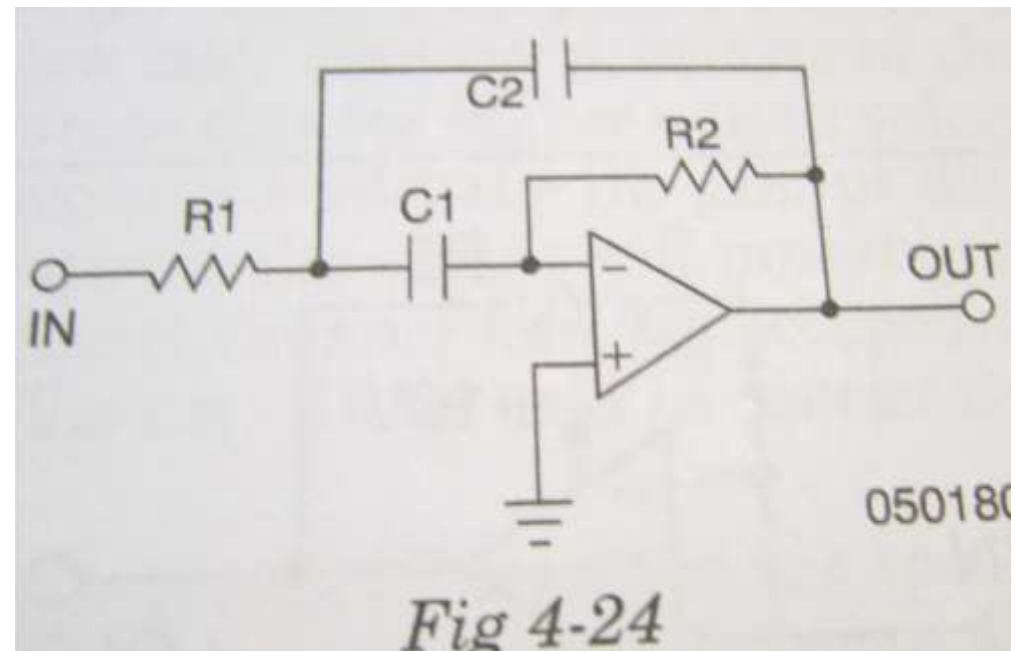

Calculating GNI (non-inverting voltage gain)


$$\text{GNI} = R2/R1 + 1$$

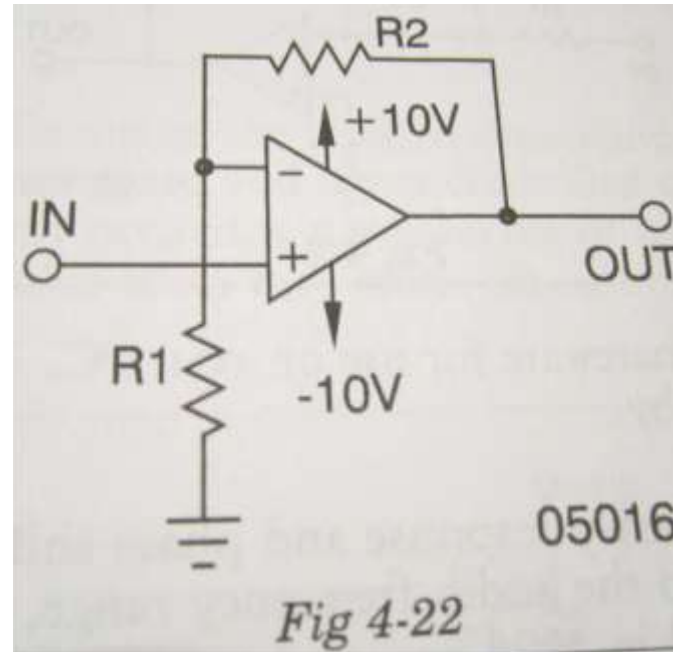

$$\text{GNI} = 1 \text{ (unity)}$$

Analogous to cathode, source,
or emitter follower

-converts high Z to lower Z

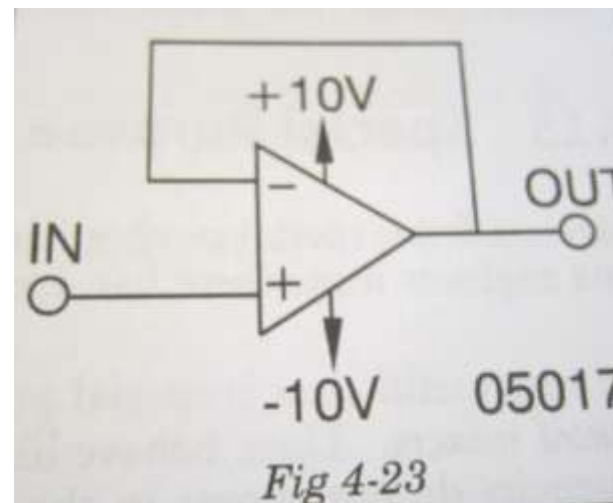


Frequency-multiplying RF JFET amplifier (with neutralization)

JFET internal capacitance causes roll-off, tendency to oscillate


Oscillation: a problem in many amplifiers

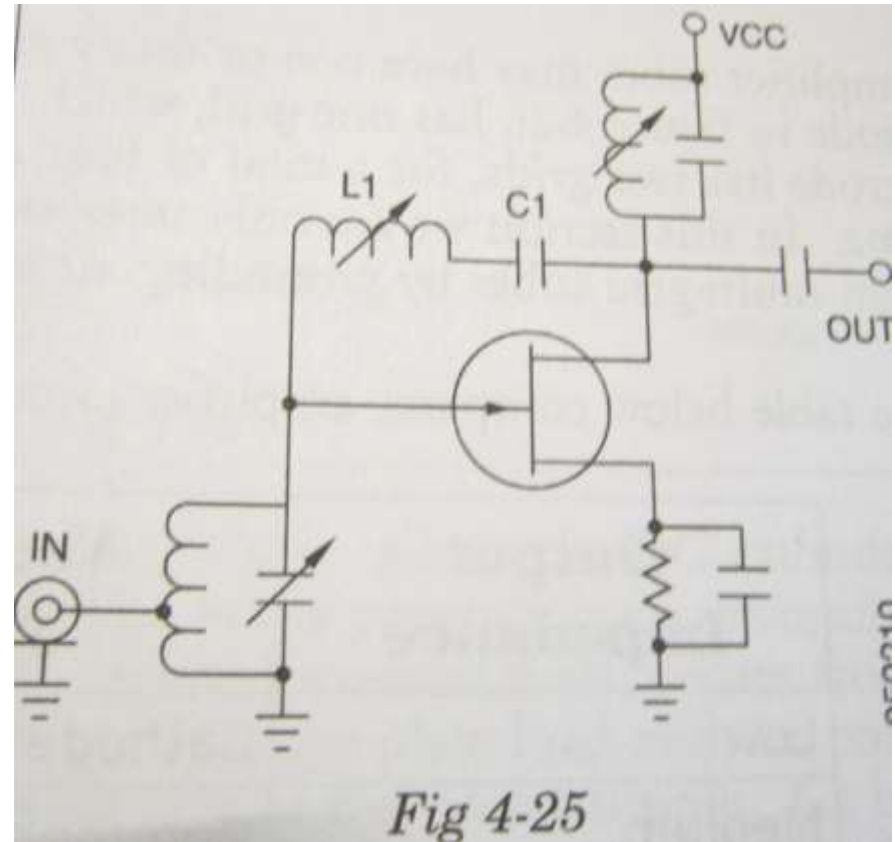L1+C1 are a neutralizing circuit
- negative feedback at a certain frequency



Neutralization needed mostly when input + output circuits are tuned to the same frequency

35W High Fidelity Audio Amplifier

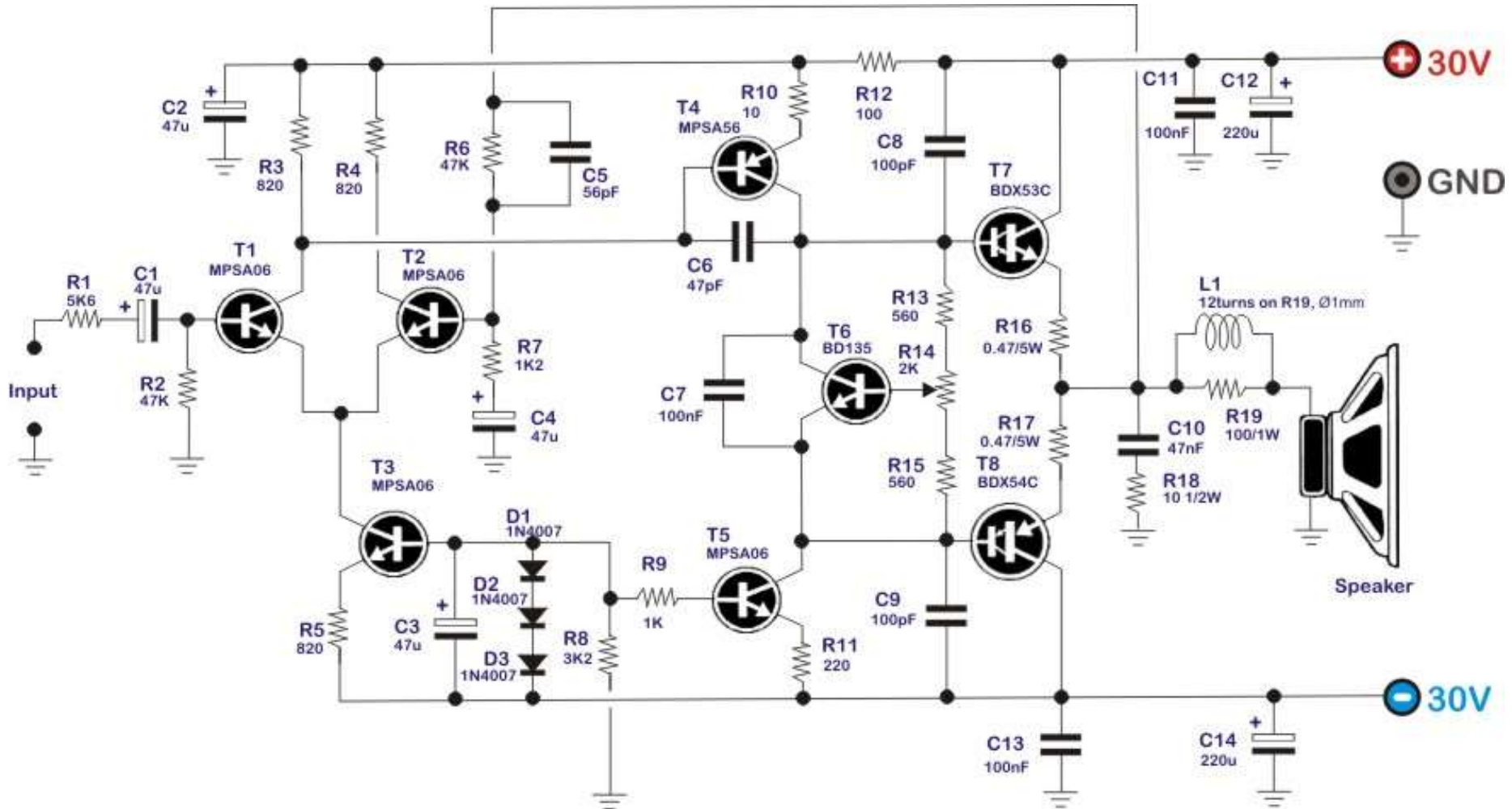

Another 30 W Audio Amp: What's Different?


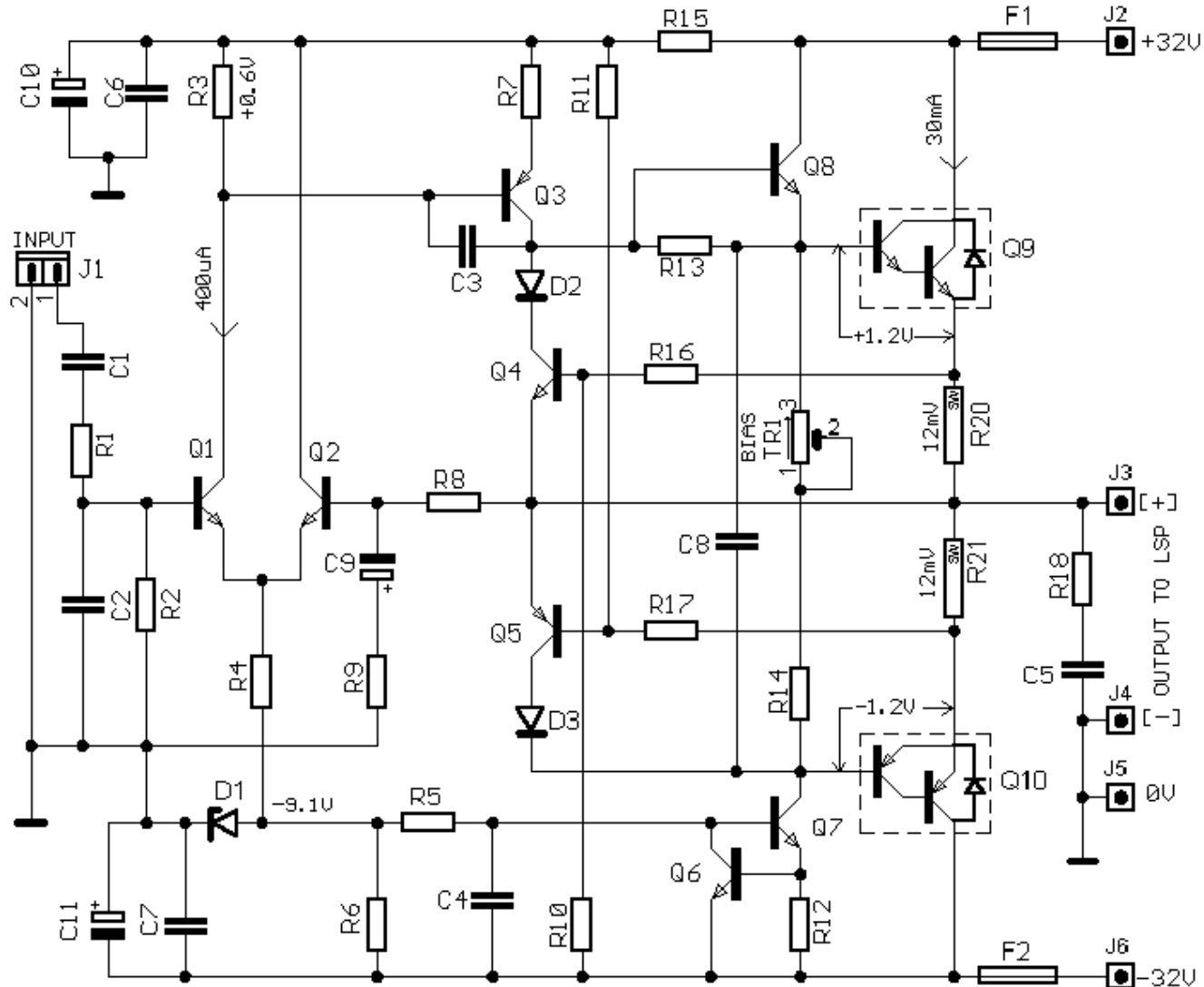


Fig.1--POWER AMPLIFIER 30W

Sam 8/02

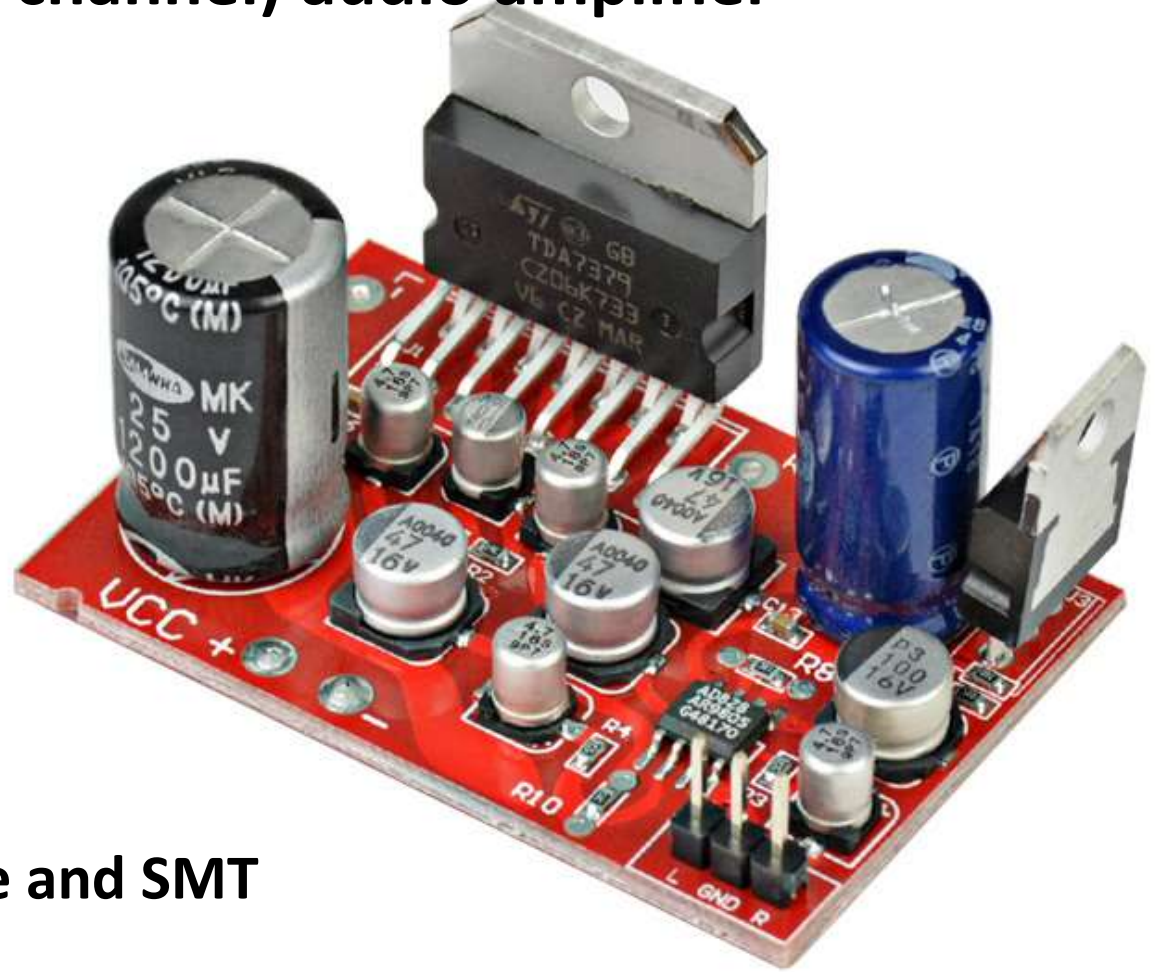-2 X 36 W stereo (2-channel) audio amplifier
-runs on +13.8 VDC



Note:

- double-sided PCB**
- uses both through-hole and SMT**
- heat-sinks needed**
- SMT vs. through-hole components**
- big reduction in cost and parts count with ICs**

Modern “grounded grid” HF linear amplifier output tube

Input is from transmitter/exciter

Will amplify 60-70 W to 700-800 W


Examples: 3CX800A7, 4 x 811A, 3-500Z

C1-L1-C2 tuned + Z-match input

C6-L2-C7-L3 tuned output circuit

EP is about 3400 VDC, IP about 500 mA

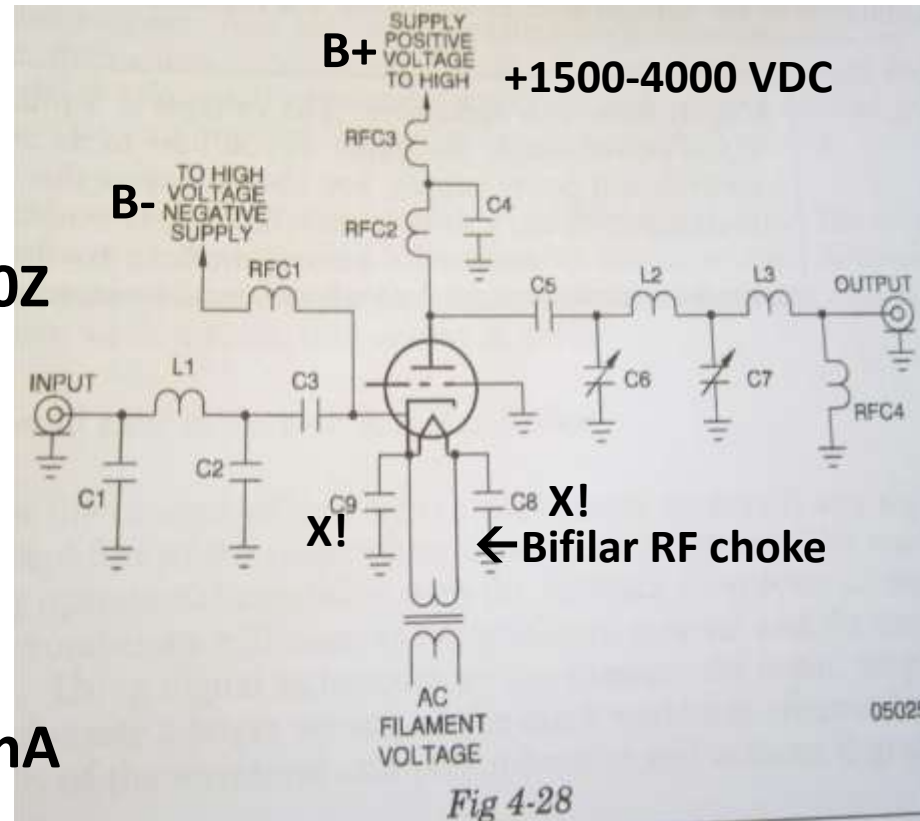An appropriate resistor from the cathode to B- will allow effective self bias. Bias is usually AB1.



Modern ceramic triode tube →



Comparing 2 popular linear amplifiers

Elecraft KPA-500 (MOSFETs)

500W PEP, SSB + CW

No-tune, lots of

Automation + protection

\$2700 CAD 26 lbs, 50V Vcc



Ameritron AL-80B (3-500Z tube)

1kW PEP SSB, 800W CW

Manual, \$2000 CAD

48 lbs

3200 VDC



**3-500Z
Triode tube**

An inside look at AMERITRON'S AL-80B

Dual illuminated cross-needle meters give you four separate indicators that monitor your operating conditions -- PEP forward power, PEP reflected power, SWR, Grid Current, Plate Current, Plate Voltage and ALC.

Heavy Duty Bandswitch.


Tank coils spaced away from chassis for optimum "Q".

Pi-Network gives smooth tuning and full band coverage, even on 160 and 80 Meters.

Heavy duty power supply: 26 lb. high silicone steel transformer and computer grade capacitors.

Rear panel adjustable input Pi-Network.

Genuine classic 3-500 Tube.

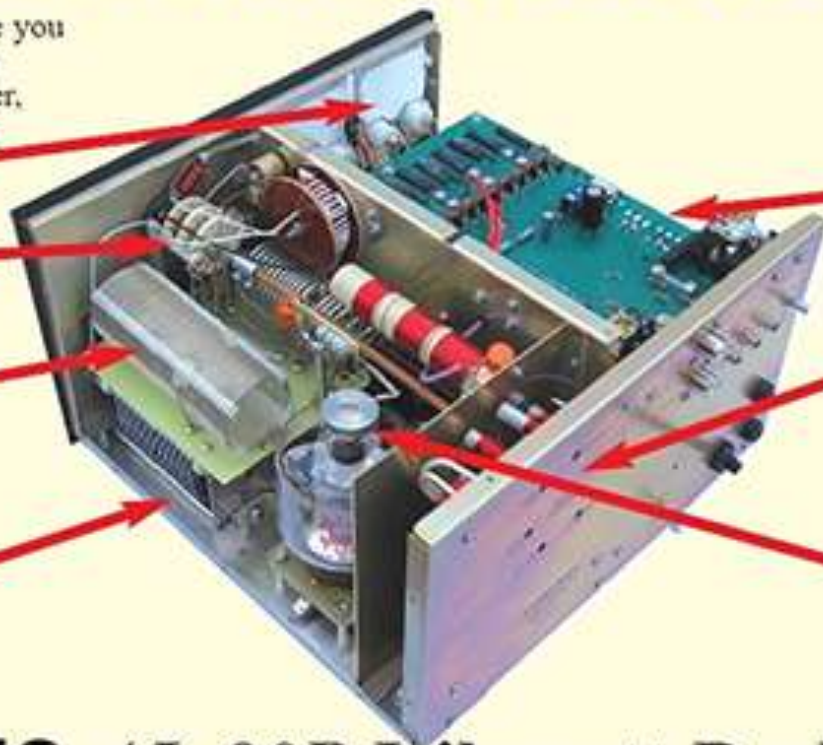

AMERITRON'S AL-80B Kilowatt Desktop Linear

SPECIFICATIONS:

Frequency Coverage: 1.8, 3.5, 7, 14, 21 MHz and WARC bands.

Export/User modified models include 10/12 Meters.

Input Circuit: Adjustable Pi-Network, VSWR 1.3:1 or less at resonance.

Output Circuit: Pi-L/Pi-Network.

Input Bandwidth: 20% for 2:1 VSWR or better.

Drive Requirement: 85 Watts for 800 Watt CW output.
10 dB gain.

Shipping Weight: Amplifier, 54 lbs.; tube, 3 lb.

Operating Weight: 48 pounds.

Efficiency: CW/SSB better than 66%.

Dimensions: 15 1/4" Dx 14" W x 8 1/2" H inches.

END of Amplifiers!

