

# Ohm's Law and Power

Al Penney  
VO1NO


Chapter 3

# Objective


---

- Define Ohm's law;
- Make simple calculations using Ohm's law;  
and
- Understand the concept of power and the formula for its calculation.


Al Penney  
VO1NO

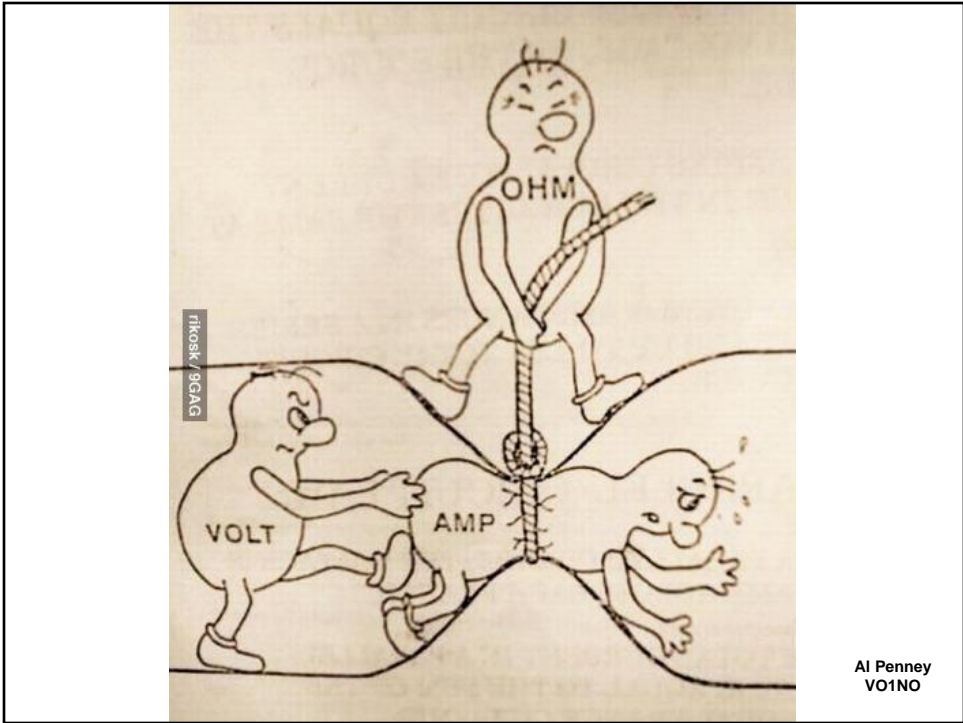

# Voltage and Current

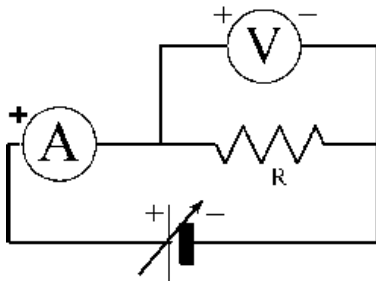

Current  
In Amps

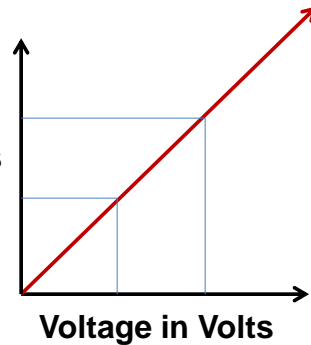

**As Voltage is increased, Current also increases.**

Al Penney  
VO1NO

**Ohm's law** states that the current through a conductor between two points is directly proportional to the potential difference across the two points. Introducing the constant of proportionality, the resistance, one arrives at the usual mathematical equation that describes this relationship:

$$E = I \times R$$

where  $I$  is the current through the conductor in units of amperes,  $V$  is the potential difference measured *across* the conductor in units of volts, and  $R$  is the resistance of the conductor in units of ohms. More specifically, Ohm's law states that the  $R$  in this relation is constant, independent of the current.

The law was named after the German physicist Georg Ohm, who, in a treatise published in 1827, described measurements of applied voltage and current through simple electrical circuits containing various lengths of wire. He presented a slightly more complex equation than the one above to explain his experimental results. The above equation is the modern form of Ohm's law.

**Georg Simon Ohm** (16 March 1789 – 6 July 1854) was a [German physicist](#) and [mathematician](#). As a school teacher, Ohm began his research with the new [electrochemical cell](#), invented by Italian scientist [Alessandro Volta](#). Using equipment of his own creation, Ohm found that there is a direct proportionality between the potential difference ([voltage](#)) applied across a conductor and the resultant [electric current](#). This relationship is known as [Ohm's law](#), and the [ohm](#), the standard unit of [electrical resistance](#), is named after him.

Ohm's law, that electric current is proportional to a potential difference, was first discovered by [Henry Cavendish](#), but Cavendish did not publish his electrical discoveries in his lifetime and they did not become known until 1879, long after Ohm had independently made the discovery and published himself. Thus the law came to bear the name of Ohm.

# Ohm's Law

---

- Relationship between Voltage, Current and Resistance can be expressed mathematically as:

$$E = I \times R$$

Where

E is measured in Volts;

I is measured in Amps; and

R is measured in Ohms.

Al Penney  
VO1NO

# Ohm's Law

---

The equation can be re-written to determine any of the 3 variables if the other two are known:

$$I = E / R$$


And

$$R = E / I$$

Al Penney  
VO1NO

# Ohm's Law Triangle

---

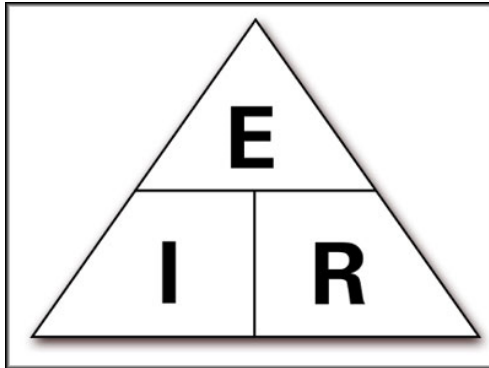

Remember the Units:

- E is measured in **VOLTS**
- I is measured in **AMPS**
- R is measured in **OHMS**

Al Penney  
VO1NO


To help remember the formula it is possible to use a triangle with one side horizontal and the peak at the top like a pyramid. This is sometimes known as the Ohm's law triangle.

In the top corner of the Ohms law triangle is the letter E, in the left hand corner, the letter I, and in the right hand bottom corner, R.


To use the triangle cover up the unknown quantity and then and then calculate it from the other two. If they are in line they are multiplied, but if one is on top of the other then they should be divided. In other words if current has to be calculated the voltage is divided by the resistance i.e.  $E/R$  and so forth.

# Ohm's Law Triangle


(Okay – Circle!)

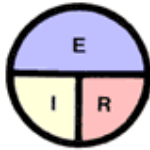

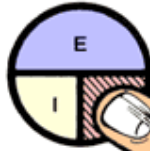
I = AMPERES (CURRENT)  
R = OHMS (RESITANCE)  
E = VOLTS (ELECTROMOTIVE FORCE)



$$R = \frac{E}{I}$$

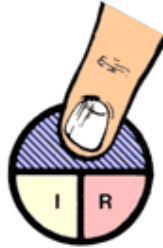

$$E = I \times R$$

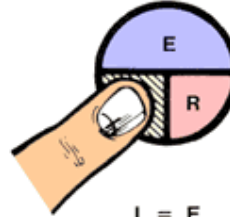

$$I = \frac{E}{R}$$


Al Penney  
VO1NO



# Ohm's Law Problem #1

---


What is the current?

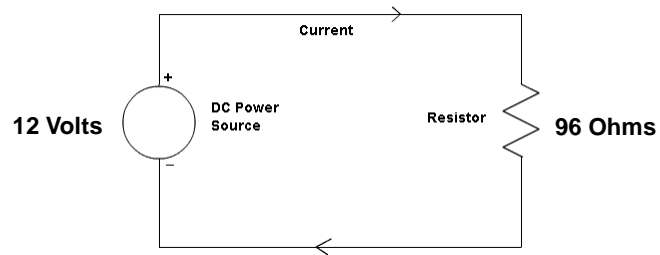


Al Penney  
VO1NO

# Ohm's Law Problem #1

What is the current?

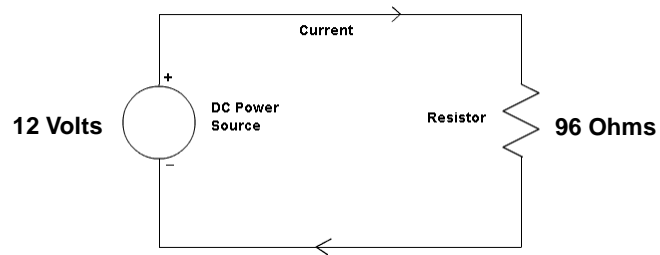


Consult the Ohms Law Triangle:

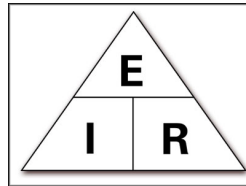


Al Penney  
VO1NO

# Ohm's Law Problem #1

What is the current?

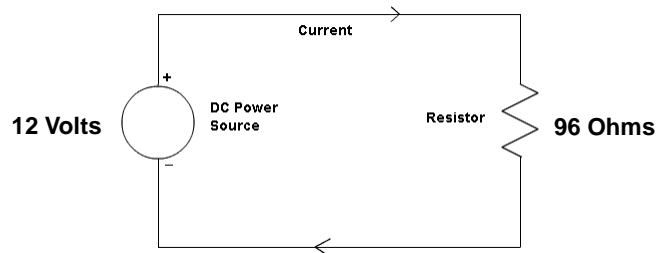

Consult the Ohms Law Triangle:

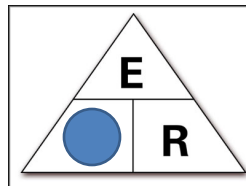


$$I = E / R$$

Al Penney  
VO1NO

# Ohm's Law Problem #1

---

What is the current?

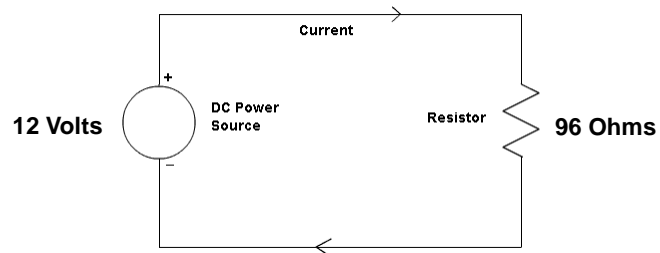

$$I = E / R$$

$$I = 12 \text{ Volts} / 96 \text{ Ohms}$$


$$I =$$

Al Penney  
VO1NO

# Ohm's Law Problem #1

---

What is the current?

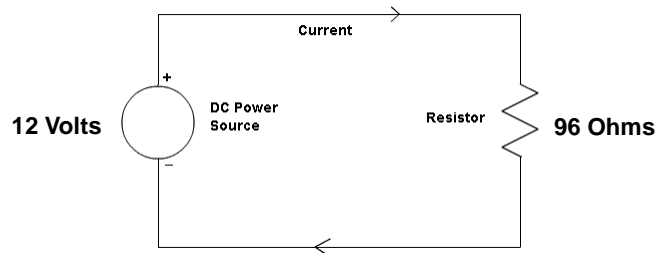

$$I = E / R$$

$$I = 12 \text{ Volts} / 96 \text{ Ohms}$$


$$I = 0.125 \text{ Amps}$$

Al Penney  
VO1NO

# Ohm's Law Problem #2

---


What is the voltage?

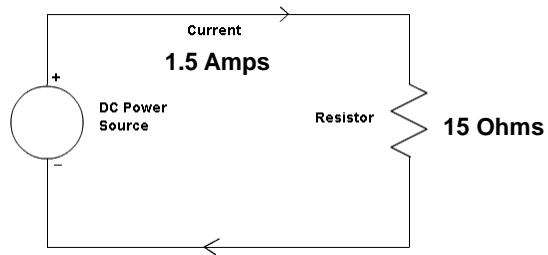


Al Penney  
VO1NO

# Ohm's Law Problem #2

What is the voltage?

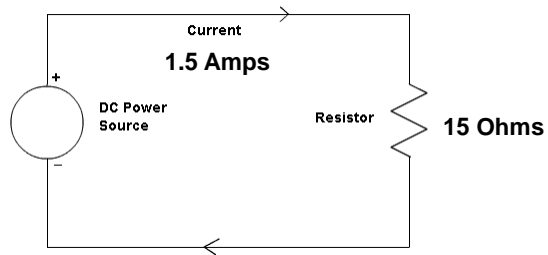


Consult the Ohms Law Triangle:

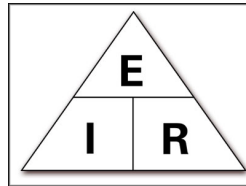


Al Penney  
VO1NO

# Ohm's Law Problem #2

What is the voltage?

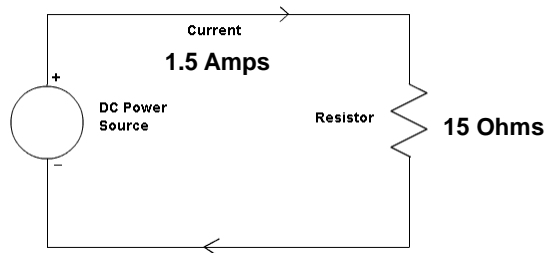

Consult the Ohms Law Triangle:

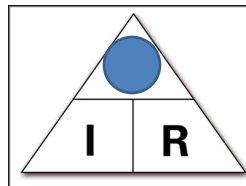

$$E = I \times R$$


Al Penney  
VO1NO



# Ohm's Law Problem #2

---

What is the voltage?

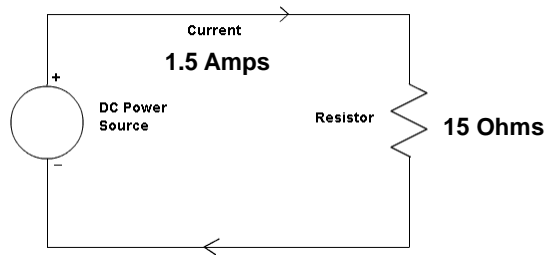


$$\begin{aligned} E &= I \times R \\ &= 1.5 \text{ Amps} \times 15 \text{ Ohms} \end{aligned}$$

Al Penney  
VO1NO

# Ohm's Law Problem #2

---

What is the voltage?

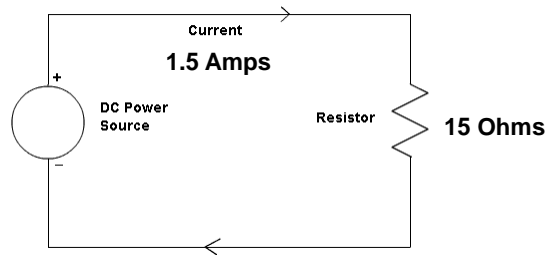


$$\begin{aligned} E &= I \times R \\ &= 1.5 \text{ Amps} \times 15 \text{ Ohms} \\ &= 22.5 \text{ Volts} \end{aligned}$$

Al Penney  
VO1NO

# Ohm's Law Problem #3

---


What is the resistance?

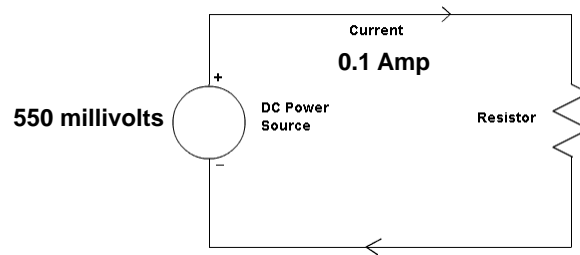


Al Penney  
VO1NO

# Ohm's Law Problem #3

What is the resistance?

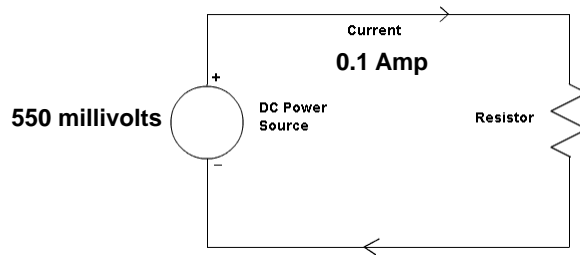


Consult the Ohms Law Triangle:

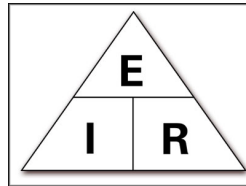


Al Penney  
VO1NO

# Ohm's Law Problem #3

What is the resistance?

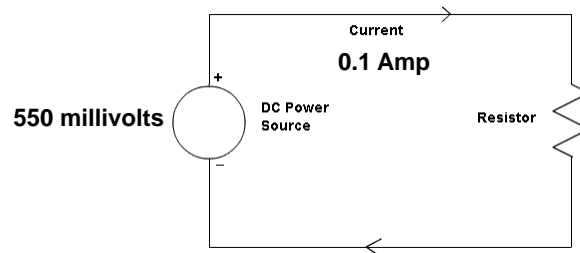

Consult the Ohms Law Triangle:

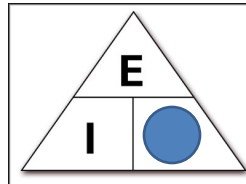


$$R = E / I$$

Al Penney  
VO1NO

# Ohm's Law Problem #3

---

What is the resistance?

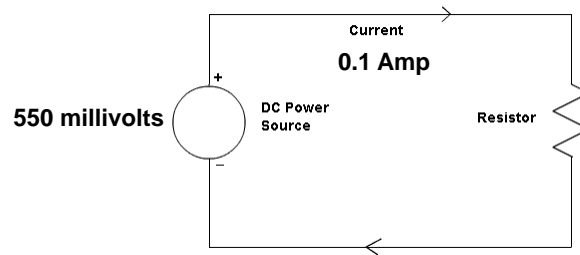

$$R = E / I$$
$$= 550 \text{ millivolts} / 0.1 \text{ Amp}$$

Al Penney  
VO1NO

# Ohm's Law Problem #3

---


- **REMEMBER the UNITS!**
  - 550 millivolts =  $550 / 1000$  volts = 0.55 volts

Al Penney  
VO1NO

# Ohm's Law Problem #3

---

What is the resistance?

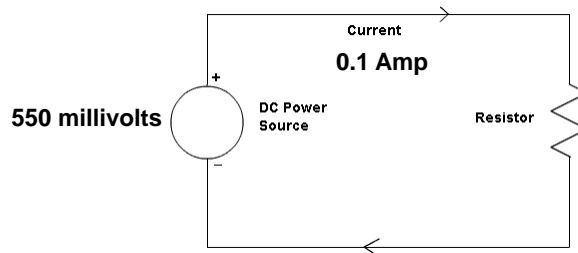

$$\begin{aligned} R &= E / I \\ &= 550 \text{ millivolts} / 0.1 \text{ Amp} \\ &= 0.55 \text{ Volts} / 0.1 \text{ Amp} \end{aligned}$$


Al Penney  
VO1NO



# Ohm's Law Problem #3

---

What is the resistance?

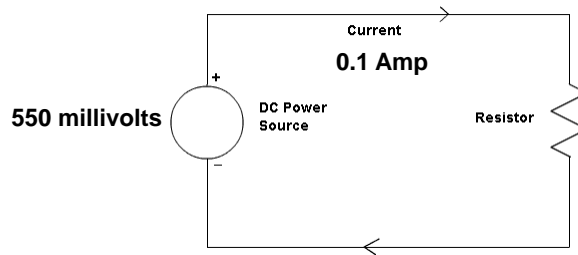


$$\begin{aligned} R &= E / I \\ &= 550 \text{ millivolts} / 0.1 \text{ Amp} \\ &= 0.55 \text{ Volts} / 0.1 \text{ Amp} \\ &= 5.5 \text{ Ohms} \end{aligned}$$

Al Penney  
VO1NO

# Ohm's Law Problem #4

---


What is the voltage?

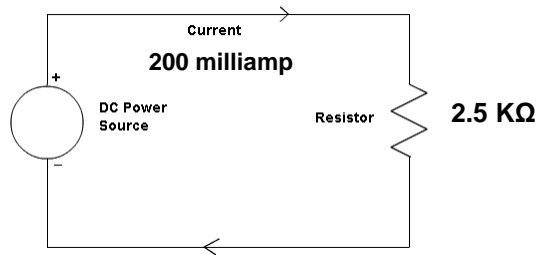


Al Penney  
VO1NO

# Ohm's Law Problem #4

What is the voltage?

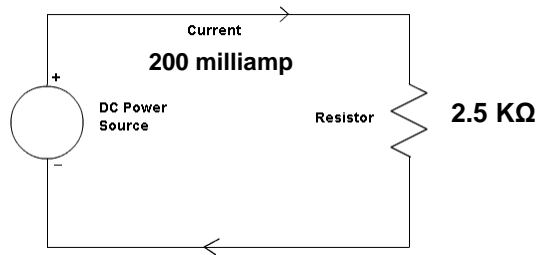


Consult the Ohms Law Triangle:

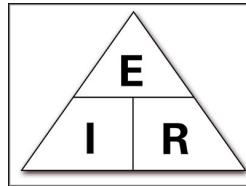


Al Penney  
VO1NO

# Ohm's Law Problem #4

What is the voltage?

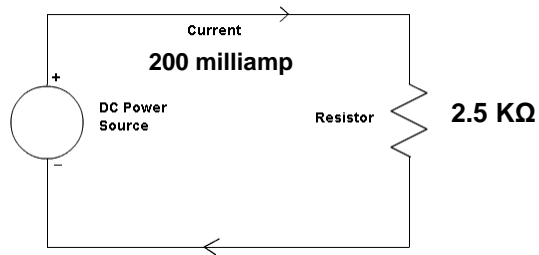

Consult the Ohms Law Triangle:

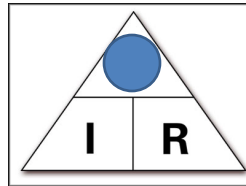


$$E = I \times R$$

Al Penney  
VO1NO

# Ohm's Law Problem #4

---

What is the voltage?

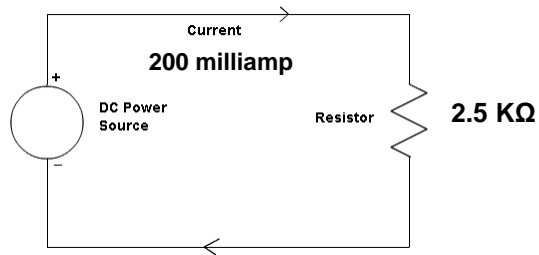

$$\begin{aligned} E &= I \times R \\ &= 200 \text{ milliamps} \times 2.5 \text{ Kilo Ohms} \end{aligned}$$

Al Penney  
VO1NO

# Ohm's Law Problem #3

---


- **REMEMBER the UNITS!**
  - 200 **milliamps** =  $200 / 1000$  Amps = 0.2 Amps
  - 2.5 **Kilo Ohms** =  $2.5 \times 1000$  Ohms = 2500 Ohms

Al Penney  
VO1NO

# Ohm's Law Problem #4

---

What is the voltage?

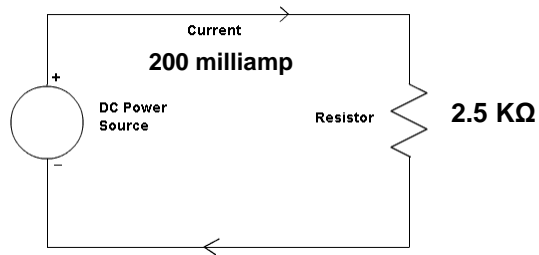


$$\begin{aligned} E &= I \times R \\ &= 200 \text{ milliamps} \times 2.5 \text{ Kilo Ohms} \\ &= 0.2 \text{ Amps} \times 2500 \text{ Ohms} \end{aligned}$$

Al Penney  
VO1NO

# Ohm's Law Problem #4

---

What is the voltage?

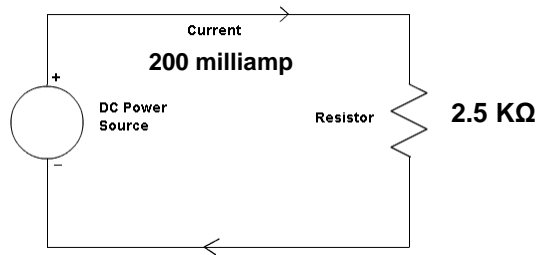

$$\begin{aligned} E &= I \times R \\ &= 200 \text{ milliamps} \times 2.5 \text{ Kilo Ohms} \\ &= 0.2 \text{ Amps} \times 2500 \text{ Ohms} \\ &= 500 \text{ Volts} \end{aligned}$$


Al Penney  
VO1NO


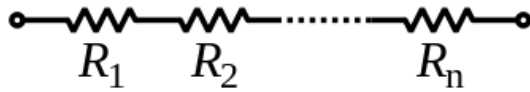
# Resistors in Series

---

- When resistors are in **SERIES**, the total resistance is the **SUM** of the individual resistances.




$$R_{\text{Total}} = R_1 + R_2 + R_3 + \dots + R_N$$

Al Penney  
VO1NO

# Resistors in Series


---

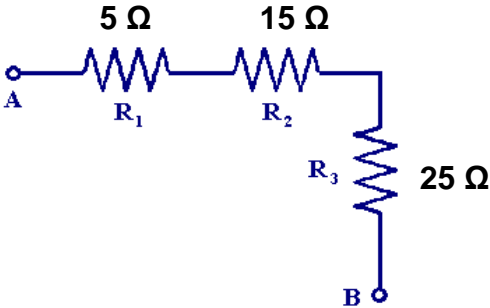

Al Penney  
VO1NO

# Resistors in Series


---

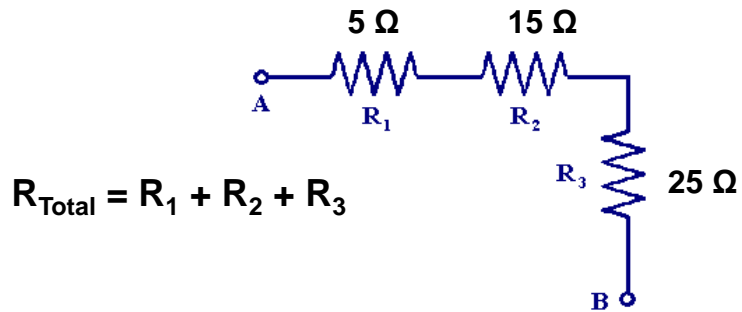

Al Penney  
VO1NO

# Resistors in Series

---

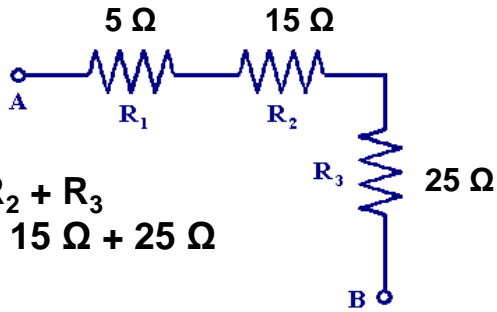


$$R_{\text{Total}} = R_1 + R_2 + R_3$$

$$R_{\text{Total}} = 5 \Omega + 15 \Omega + 25 \Omega$$

Al Penney  
VO1NO

# Resistors in Series

---

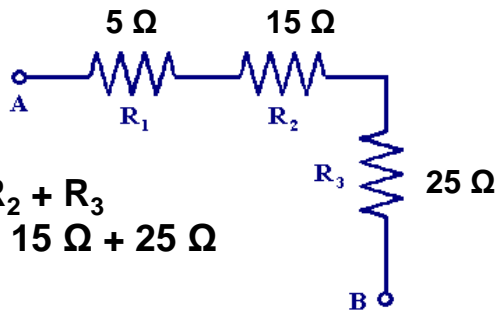

$$R_{\text{Total}} = R_1 + R_2 + R_3$$

$$R_{\text{Total}} = 5 \Omega + 15 \Omega + 25 \Omega$$

$$R_{\text{Total}} = 45 \Omega$$


Al Penney  
VO1NO

# Resistors in Parallel

---

- When resistors are in Parallel, the total resistance is given by the following equation:

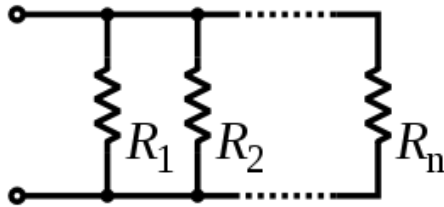
$$1/R_{\text{Total}} = 1/R_1 + 1/R_2 + 1/R_3 + \dots + 1/R_N$$



Al Penney  
VO1NO

# Resistors in Parallel


---

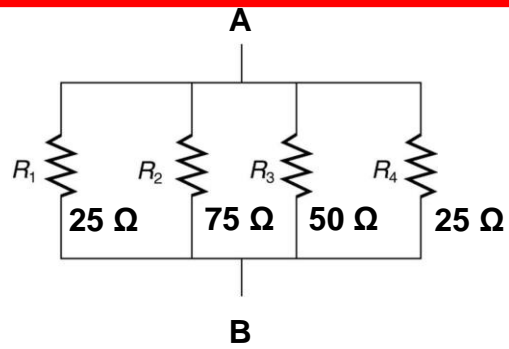

Al Penney  
VO1NO

# Resistors in Parallel

---

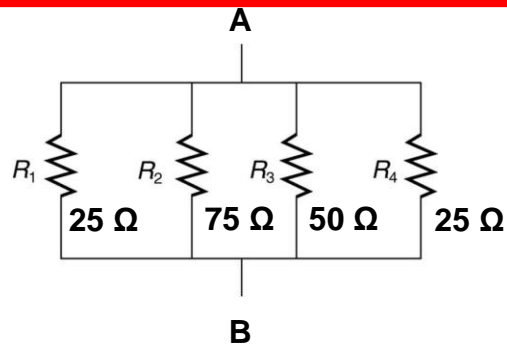


$$1/R_{\text{Total}} = 1/R_1 + 1/R_2 + 1/R_3 + 1/R_4$$

Al Penney  
VO1NO



# Resistors in Parallel

---

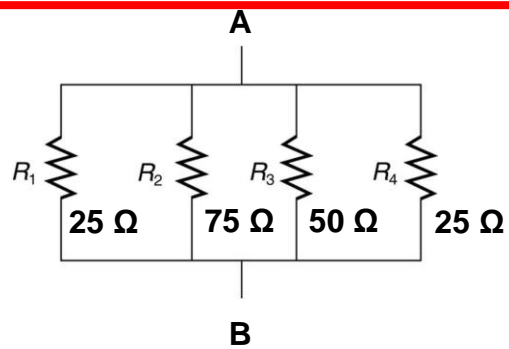


$$\frac{1}{R_{\text{Total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$
$$\frac{1}{R_{\text{Total}}} = \frac{1}{25} + \frac{1}{75} + \frac{1}{50} + \frac{1}{25}$$

Al Penney  
VO1NO

# Resistors in Parallel

---

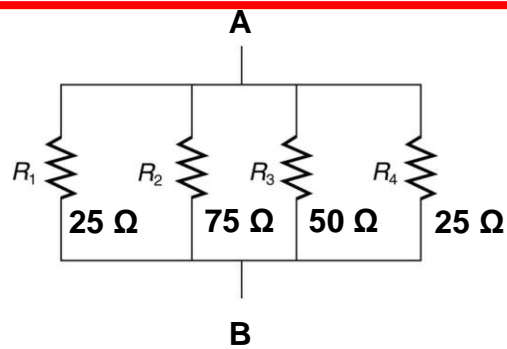


$$1/R_{\text{Total}} = 1/R_1 + 1/R_2 + 1/R_3 + 1/R_4$$

$$1/R_{\text{Total}} = 1/25 + 1/75 + 1/50 + 1/25 = 6/150 + 2/150 + 3/150 + 6/150$$

Al Penney  
VO1NO

# Resistors in Parallel

---

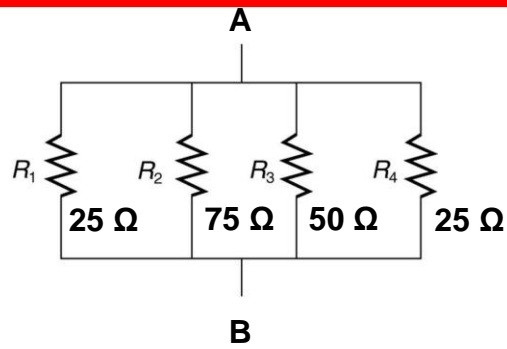

$$1/R_{\text{Total}} = 1/R_1 + 1/R_2 + 1/R_3 + 1/R_4$$


$$1/R_{\text{Total}} = 1/25 + 1/75 + 1/50 + 1/25 = 6/150 + 2/150 + 3/150 + 6/150$$

$$1/R_{\text{Total}} = 17/150 \Omega$$

Al Penney  
VO1NO

# Resistors in Parallel

---

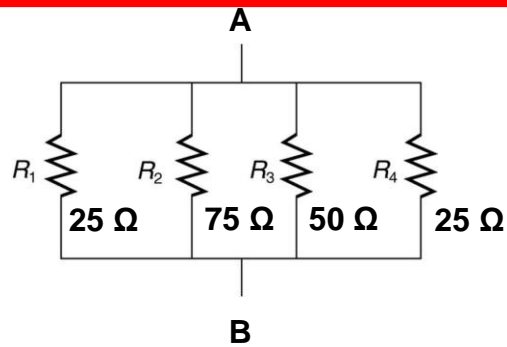

$$1/R_{\text{Total}} = 1/R_1 + 1/R_2 + 1/R_3 + 1/R_4$$


$$1/R_{\text{Total}} = 1/25 + 1/75 + 1/50 + 1/25 = 6/150 + 2/150 + 3/150 + 6/150$$

$$1/R_{\text{Total}} = 17/150 \Omega$$


$$R_{\text{Total}} = 150/17 \Omega = 8.82 \Omega$$

Al Penney  
VO1NO

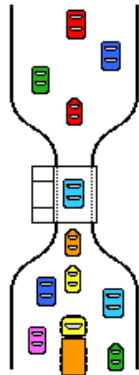
### Influencing the Flow Rate on a Tollway



**A Single Resistor**

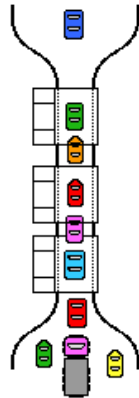

**Three Resistors  
Placed in Series**

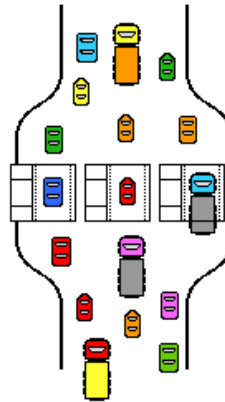


**Three Resistors  
Placed in Parallel**

Al Penney  
VO1NO
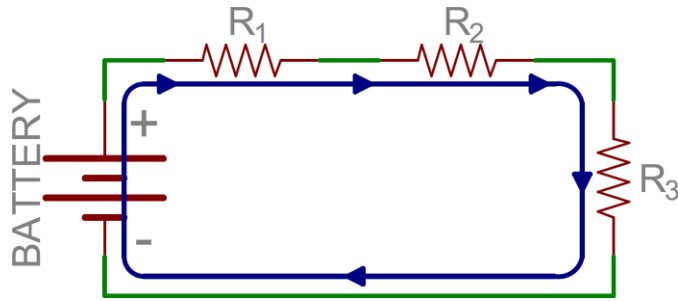
# Current in a Series Circuit

- The current through each resistor in a Series Circuit is identical.




$$I_{\text{Total}} = I_{R1} = I_{R2} = I_{R3}$$

Al Penney  
VO1NO
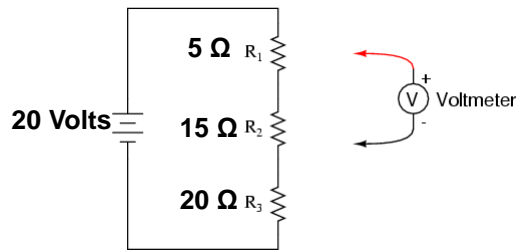
# Voltage in Series Circuits

- The sum of all the voltages across each resistor in a Series Circuit will equal the source voltage.




$$E_{\text{source}} = E_{R1} + E_{R2} + E_{R3}$$

Al Penney  
VO1NO

**Voltage drop** is the decrease of electrical potential along the path of a current flowing in an electrical **circuit**. Voltage drops in the **internal resistance** of the source, across **conductors**, across **contacts**, and across **connectors** are undesirable because some of the energy supplied is dissipated. The voltage drop across the **electrical load** is proportional to the power available to be converted in that load to some other useful form of energy.

Voltage drop is the loss of voltage caused by the flow of current flow through a resistance. The greater the resistance the greater the VD. To check the VD, use a voltmeter connected between the point where the VD is to be measured. In DC circuits and AC resistive circuits the total of all the voltage drops across series-connected loads should add up to the voltage applied to the circuit


# To Calculate Voltage Drop...

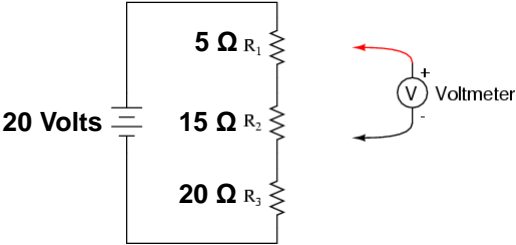

Al Penney  
VO1NO



# 1. Determine Total Resistance

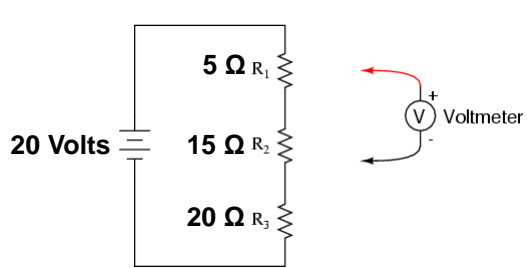


$$R_{\text{Total}} = R_1 + R_2 + R_3$$

$$R_{\text{Total}} =$$

Al Penney  
VO1NO



# 1. Determine Total Resistance

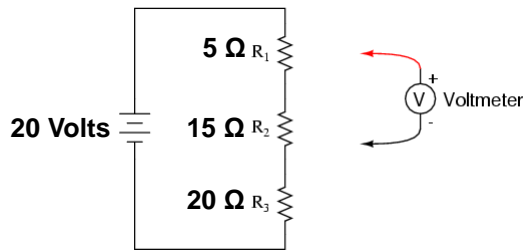

$$R_{\text{Total}} = R_1 + R_2 + R_3$$
$$R_{\text{Total}} = 5 \Omega + 15 \Omega + 20 \Omega$$
$$R_{\text{Total}} = 40 \Omega$$

Al Penney  
VO1NO

## 2. Determine Current

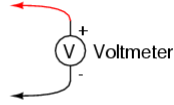
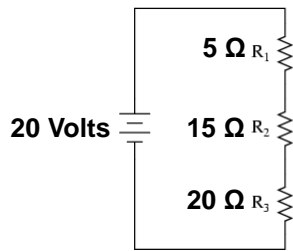


$$R_{\text{Total}} = R_1 + R_2 + R_3$$
$$R_{\text{Total}} = 5 \Omega + 15 \Omega + 20 \Omega$$
$$R_{\text{Total}} = 40 \Omega$$

$$I = E / R$$
$$I =$$

Al Penney  
VO1NO

## 2. Determine Current

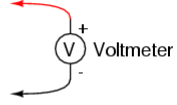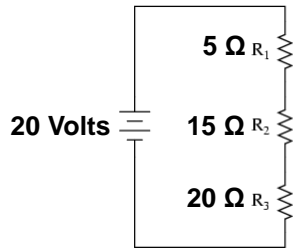


$$R_{\text{Total}} = R_1 + R_2 + R_3$$
$$R_{\text{Total}} = 5\ \Omega + 15\ \Omega + 20\ \Omega$$
$$R_{\text{Total}} = 40\ \Omega$$

$$I = E / R$$
$$I = 20\ \text{Volts} / 40\ \text{Ohms}$$
$$I = 0.5\ \text{Amps}$$

Al Penney  
VO1NO

### 3. Determine Voltage Drops

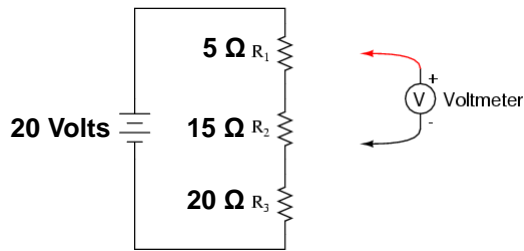

$$R_{\text{Total}} = R_1 + R_2 + R_3$$
$$R_{\text{Total}} = 5 \Omega + 15 \Omega + 20 \Omega$$
$$R_{\text{Total}} = 40 \Omega$$

$$I = E / R$$
$$I = 20 \text{ Volts} / 40 \text{ Ohms}$$
$$I = 0.5 \text{ Amps}$$


$$E_{R1} = I \times R_1$$
$$E_{R1} =$$

$$E_{R2} = I \times R_2$$
$$E_{R2} =$$

$$E_{R3} = I \times R_3$$
$$E_{R3} =$$

Al Penney  
VO1NO

### 3. Determine Voltage Drops

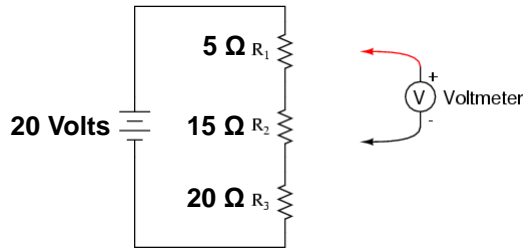

$$R_{\text{Total}} = R_1 + R_2 + R_3$$
$$R_{\text{Total}} = 5 \Omega + 15 \Omega + 20 \Omega$$
$$R_{\text{Total}} = 40 \Omega$$

$$I = E / R$$
$$I = 20 \text{ Volts} / 40 \text{ Ohms}$$
$$I = 0.5 \text{ Amps}$$


$$E_{R1} = I \times R_1$$
$$E_{R1} = 0.5 \text{ Amps} \times 5 \Omega$$
$$E_{R1} = 2.5 \text{ Volts}$$

$$E_{R2} = I \times R_2$$
$$E_{R2} = 0.5 \text{ Amps} \times 15 \Omega$$
$$E_{R2} = 7.5 \text{ Volts}$$

$$E_{R3} = I \times R_3$$
$$E_{R3} = 0.5 \text{ Amps} \times 20 \Omega$$
$$E_{R3} = 10 \text{ Volts}$$

Al Penney  
VO1NO

## 4. Check Your Results!

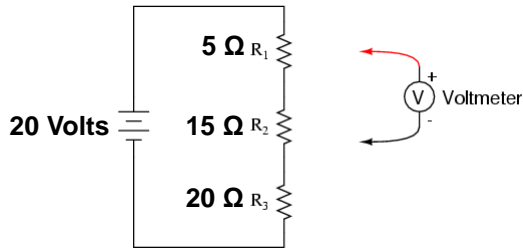

$$\begin{aligned}R_{\text{Total}} &= R_1 + R_2 + R_3 \\R_{\text{Total}} &= 5 \Omega + 15 \Omega + 20 \Omega \\R_{\text{Total}} &= 40 \Omega\end{aligned}$$

$$\begin{aligned}I &= E / R \\I &= 20 \text{ Volts} / 40 \text{ Ohms} \\I &= 0.5 \text{ Amps}\end{aligned}$$

$$E_{R1} = I \times R_1$$

$$E_{R1} = 0.5 \text{ Amps} \times 5 \Omega$$

$$E_{R1} = 2.5 \text{ Volts}$$

$$E_{R2} = I \times R_2$$

$$E_{R2} = 0.5 \text{ Amps} \times 15 \Omega$$

$$E_{R2} = 7.5 \text{ Volts}$$

$$E_{R3} = I \times R_3$$

$$E_{R3} = 0.5 \text{ Amps} \times 20 \Omega$$

$$E_{R3} = 10 \text{ Volts}$$


$$E_{\text{source}} = E_{R1} + E_{R2} + E_{R3}$$

$$E_{\text{source}} = 2.5\text{V} + 7.5\text{V} + 10\text{V} = 20\text{V}$$

Al Penney  
VO1NO
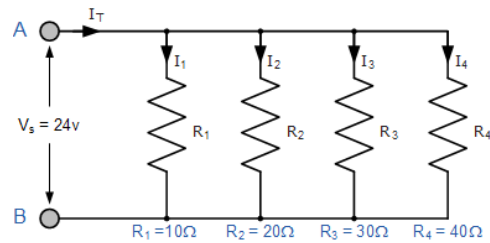
# Voltage in Parallel Circuits

- The voltage applied to each resistor in a Parallel Circuit is the same as the source voltage.




$$E_{\text{source}} = E_{R1} = E_{R2} = E_{R3} = E_{R4}$$

Al Penney  
VO1NO


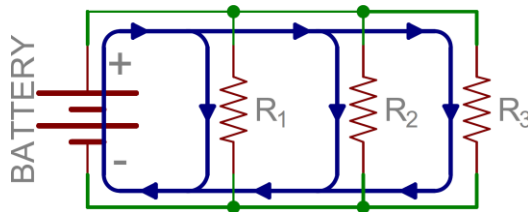
# Current in a Parallel Circuit

- The total current in a Parallel Circuit is divided among the resistors.
- The sum of the currents through each resistor equals the total current.




$$I_{\text{Total}} = I_{R1} + I_{R2} + I_{R3}$$

Al Penney  
VO1NO


# To Calculate Currents...

---

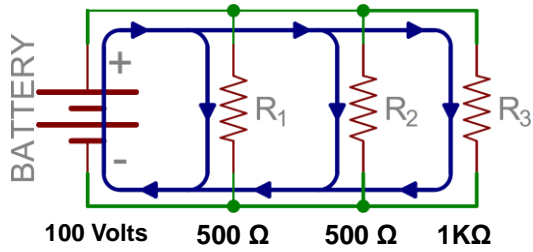


Al Penney  
VO1NO

# Determine Equivalent Resistance

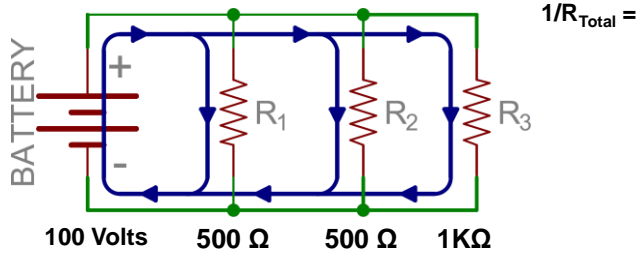

Al Penney  
VO1NO


# Determine Equivalent Resistance

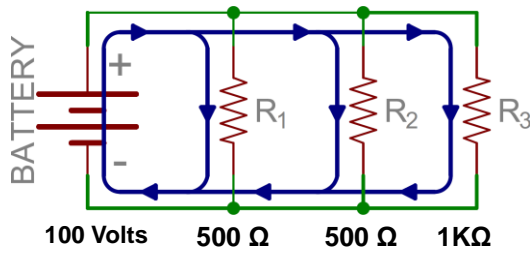

$$\frac{1}{R_{\text{Total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$
$$\frac{1}{R_{\text{Total}}} = \frac{1}{500} + \frac{1}{500} + \frac{1}{1K}$$

Al Penney  
VO1NO


# Determine Equivalent Resistance

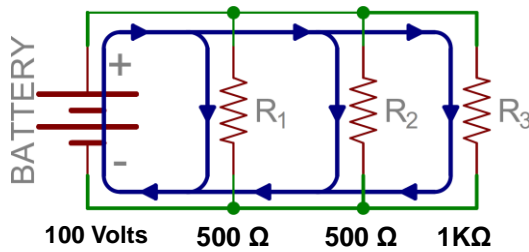

$$\begin{aligned} 1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\ 1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1K \\ 1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\ 1/R_{\text{Total}} &= 5/1000 \end{aligned}$$

Al Penney  
VO1NO


# Determine Equivalent Resistance

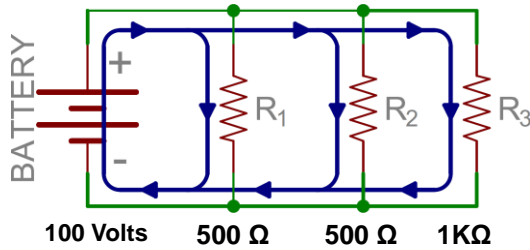

$$\begin{aligned} 1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\ 1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1K \\ 1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\ 1/R_{\text{Total}} &= 5/1000 \\ R_{\text{Total}} &= 1000/5 = 200 \Omega \end{aligned}$$

Al Penney  
VO1NO

# Determine Overall Current

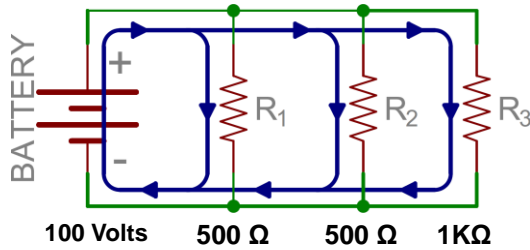


$$\begin{aligned} 1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\ 1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1K \\ 1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\ 1/R_{\text{Total}} &= 5/1000 \\ R_{\text{Total}} &= 1000/5 = 200 \Omega \end{aligned}$$

I =

Al Penney  
VO1NO

# Determine Overall Current

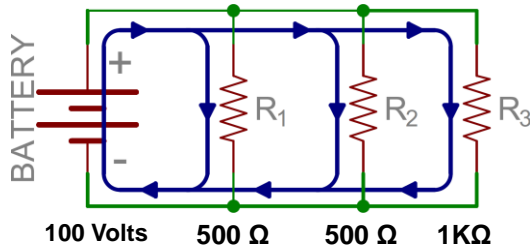


$$\begin{aligned} 1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\ 1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1K \\ 1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\ 1/R_{\text{Total}} &= 5/1000 \\ R_{\text{Total}} &= 1000/5 = 200 \Omega \end{aligned}$$

$$I = E / R$$

Al Penney  
VO1NO



# Determine Overall Current

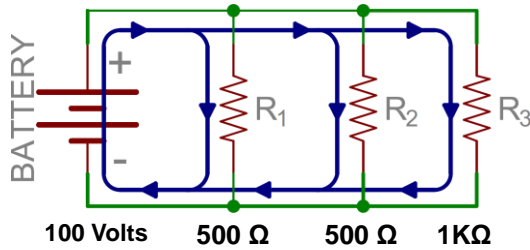


$$\begin{aligned}1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1K \\1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\1/R_{\text{Total}} &= 5/1000 \\R_{\text{Total}} &= 1000/5 = 200 \Omega\end{aligned}$$

$$\begin{aligned}I &= E / R \\I &= 100 \text{ V} / 200 \Omega \\I &= 0.5 \text{ Amps}\end{aligned}$$

Al Penney  
VO1NO

# Determine Individual Currents

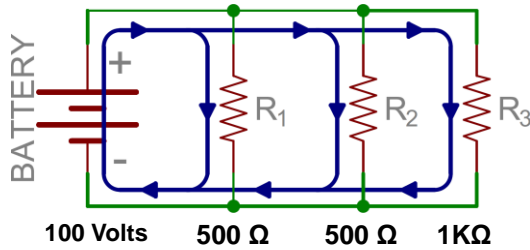

$$\begin{aligned}1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1K \\1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\1/R_{\text{Total}} &= 5/1000 \\R_{\text{Total}} &= 1000/5 = 200 \Omega\end{aligned}$$

$$\begin{aligned}I &= E / R \\I &= 100 \text{ V} / 200 \Omega \\I &= 0.5 \text{ Amps}\end{aligned}$$


$$I_{R1} =$$

$$I_{R2} =$$

$$I_{R3} =$$

Al Penney  
VO1NO

# Determine Individual Currents

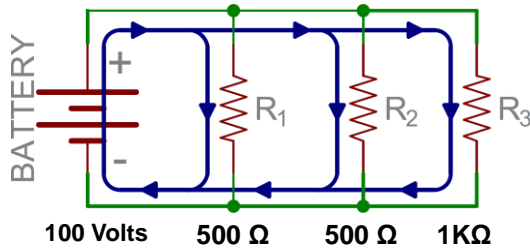

$$\begin{aligned}1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1K \\1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\1/R_{\text{Total}} &= 5/1000 \\R_{\text{Total}} &= 1000/5 = 200 \Omega\end{aligned}$$

$$\begin{aligned}I &= E / R \\I &= 100 \text{ V} / 200 \Omega \\I &= 0.5 \text{ Amps}\end{aligned}$$


$$I_{R1} = E / R_1$$

$$I_{R2} = E / R_2$$

$$I_{R3} = E / R_3$$

Al Penney  
VO1NO

# Determine Individual Currents

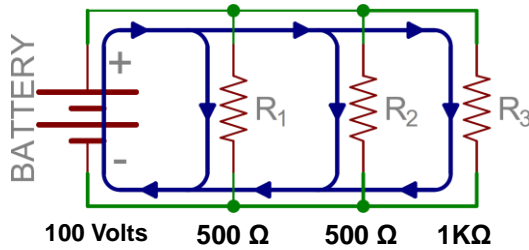

$$\begin{aligned} 1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\ 1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1K \\ 1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\ 1/R_{\text{Total}} &= 5/1000 \\ R_{\text{Total}} &= 1000/5 = 200 \Omega \end{aligned}$$

$$\begin{aligned} I &= E / R \\ I &= 100 \text{ V} / 200 \Omega \\ I &= 0.5 \text{ Amps} \end{aligned}$$


$$\begin{aligned} I_{R1} &= E / R_1 \\ I_{R1} &= 100 \text{ V} / 500 \Omega \\ I_{R1} &= \end{aligned}$$

$$\begin{aligned} I_{R2} &= E / R_2 \\ I_{R2} &= 100 \text{ V} / 500 \Omega \\ I_{R2} &= \end{aligned}$$

$$\begin{aligned} I_{R3} &= E / R_3 \\ I_{R3} &= 100 \text{ V} / 1000 \Omega \\ I_{R3} &= \end{aligned}$$

Al Penney  
VO1NO

# Determine Individual Currents

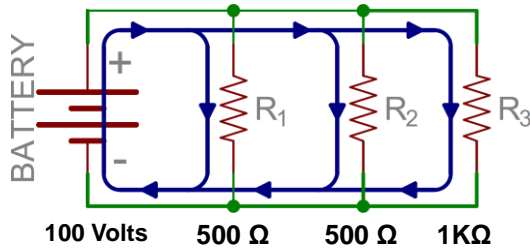

$$\begin{aligned}1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1K \\1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\1/R_{\text{Total}} &= 5/1000 \\R_{\text{Total}} &= 1000/5 = 200 \Omega\end{aligned}$$

$$\begin{aligned}I &= E / R \\I &= 100 \text{ V} / 200 \Omega \\I &= 0.5 \text{ Amps}\end{aligned}$$


$$\begin{aligned}I_{R1} &= E / R_1 \\I_{R1} &= 100 \text{ V} / 500 \Omega \\I_{R1} &= 0.2 \text{ Amps}\end{aligned}$$

$$\begin{aligned}I_{R2} &= E / R_2 \\I_{R2} &= 100 \text{ V} / 500 \Omega \\I_{R2} &= 0.2 \text{ Amps}\end{aligned}$$

$$\begin{aligned}I_{R3} &= E / R_3 \\I_{R3} &= 100 \text{ V} / 1000 \Omega \\I_{R3} &= 0.1 \text{ Amps}\end{aligned}$$

Al Penney  
VO1NO

# Check your Answer!

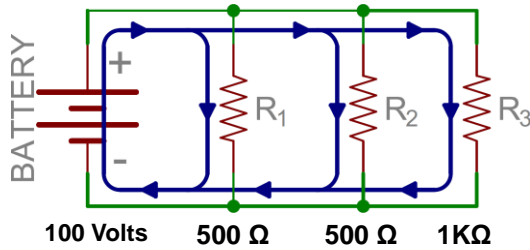

$$1/R_{\text{Total}} = 1/R_1 + 1/R_2 + 1/R_3$$

$$1/R_{\text{Total}} = 1/500 + 1/500 + 1/1K$$

$$1/R_{\text{Total}} = 2/1000 + 2/1000 + 1/1000$$

$$1/R_{\text{Total}} = 5/1000$$

$$R_{\text{Total}} = 1000/5 = 200 \Omega$$

$$I = E / R$$

$$I = 100 \text{ V} / 200 \Omega$$

$$I = 0.5 \text{ Amps}$$

$$I_{R1} = E / R_1$$

$$I_{R1} = 100 \text{ V} / 500 \Omega$$

$$I_{R1} = 0.2 \text{ Amps}$$

$$I_{R2} = E / R_2$$

$$I_{R2} = 100 \text{ V} / 500 \Omega$$

$$I_{R2} = 0.2 \text{ Amps}$$

$$I_{R3} = E / R_3$$


$$I_{R3} = 100 \text{ V} / 1000 \Omega$$

$$I_{R3} = 0.1 \text{ Amps}$$

**I<sub>Total</sub> =**

Al Penney  
VO1NO

# Check your Answer!

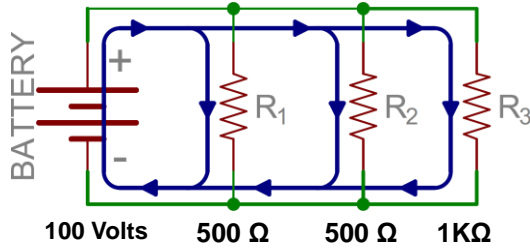

$$\begin{aligned}1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1K \\1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\1/R_{\text{Total}} &= 5/1000 \\R_{\text{Total}} &= 1000/5 = 200 \Omega\end{aligned}$$

$$\begin{aligned}I &= E / R \\I &= 100 \text{ V} / 200 \Omega \\I &= 0.5 \text{ Amps}\end{aligned}$$

$$\begin{aligned}I_{R1} &= E / R_1 \\I_{R1} &= 100 \text{ V} / 500 \Omega \\I_{R1} &= 0.2 \text{ Amps}\end{aligned}$$


$$\begin{aligned}I_{R2} &= E / R_2 \\I_{R2} &= 100 \text{ V} / 500 \Omega \\I_{R2} &= 0.2 \text{ Amps}\end{aligned}$$

$$\begin{aligned}I_{R3} &= E / R_3 \\I_{R3} &= 100 \text{ V} / 1000 \Omega \\I_{R3} &= 0.1 \text{ Amps}\end{aligned}$$

$$I_{\text{Total}} = I_{R1} + I_{R2} + I_{R3} =$$

Al Penney  
VO1NO

# Check your Answer!

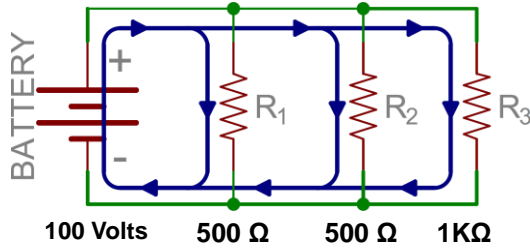

$$\begin{aligned}1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1K \\1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\1/R_{\text{Total}} &= 5/1000 \\R_{\text{Total}} &= 1000/5 = 200 \Omega\end{aligned}$$

$$\begin{aligned}I &= E / R \\I &= 100 \text{ V} / 200 \Omega \\I &= 0.5 \text{ Amps}\end{aligned}$$

$I_{R1} = E / R_1$	$I_{R2} = E / R_2$	$I_{R3} = E / R_3$
$I_{R1} = 100 \text{ V} / 500 \Omega$	$I_{R2} = 100 \text{ V} / 500 \Omega$	$I_{R3} = 100 \text{ V} / 1000 \Omega$
$I_{R1} = 0.2 \text{ Amps}$	$I_{R2} = 0.2 \text{ Amps}$	$I_{R3} = 0.1 \text{ Amps}$


$$I_{\text{Total}} = I_{R1} + I_{R2} + I_{R3} = 0.2 + 0.2 + 0.1 = 0.5 \text{ Amp}$$

Al Penney  
VO1NO



# Series Parallel Combinations


---

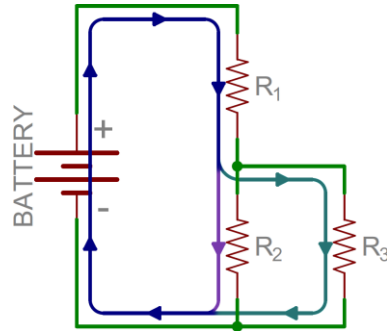

Al Penney  
VO1NO


# Series Parallel Combinations

---

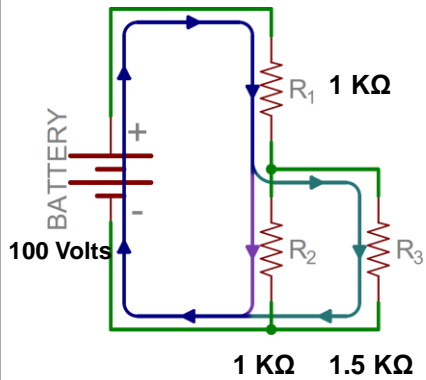


Al Penney  
VO1NO

# Series Parallel Combinations

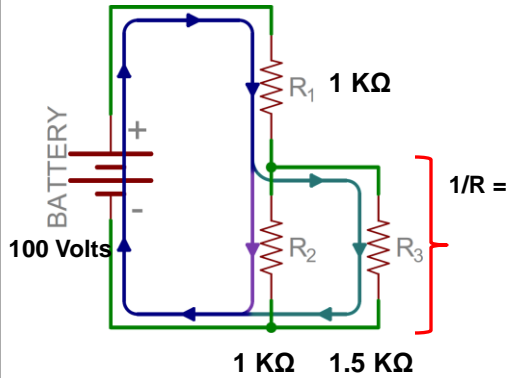


Al Penney  
VO1NO

# Series Parallel Combinations

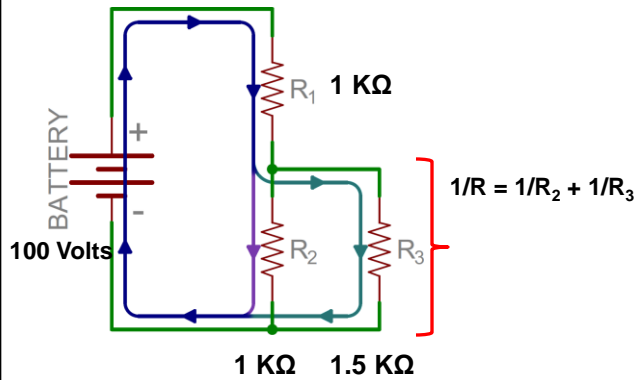


Al Penney  
VO1NO

# Series Parallel Combinations

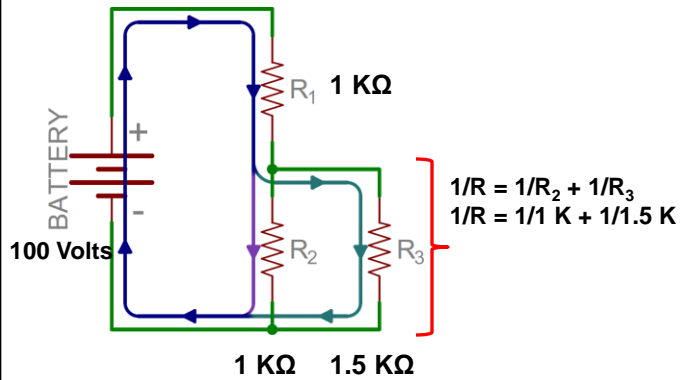


Al Penney  
VO1NO

# Series Parallel Combinations

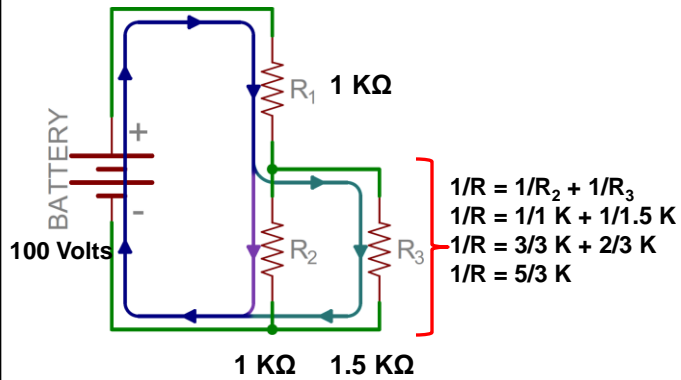


Al Penney  
VO1NO

# Series Parallel Combinations

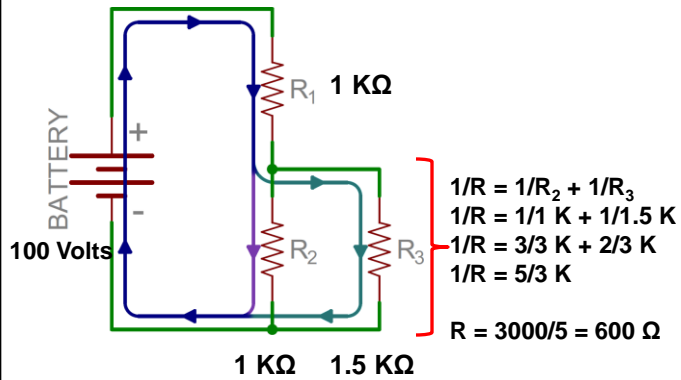

Al Penney  
VO1NO


# Series Parallel Combinations

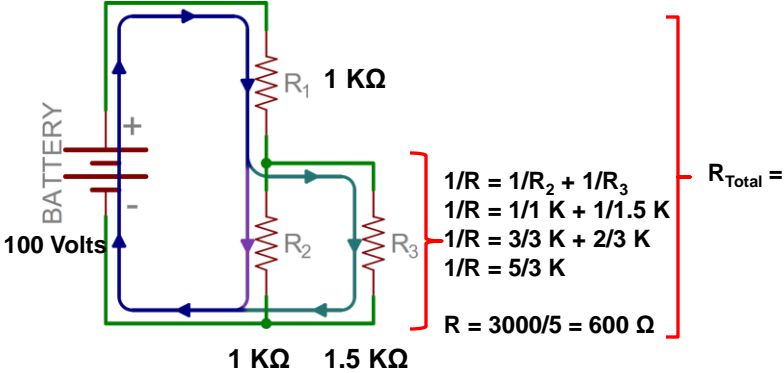

Al Penney  
VO1NO




# Series Parallel Combinations

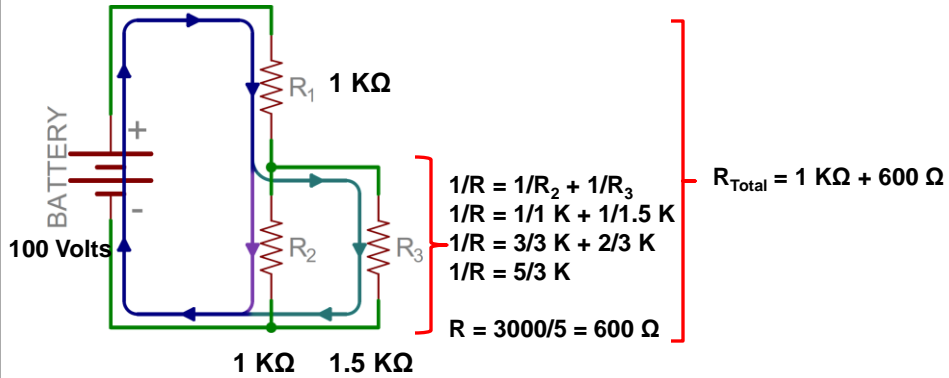


Al Penney  
VO1NO

# Series Parallel Combinations

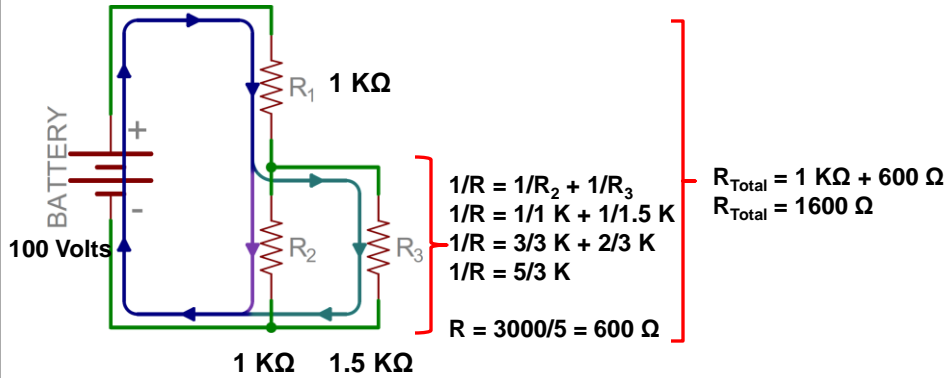

Al Penney  
VO1NO

# Series Parallel Combinations

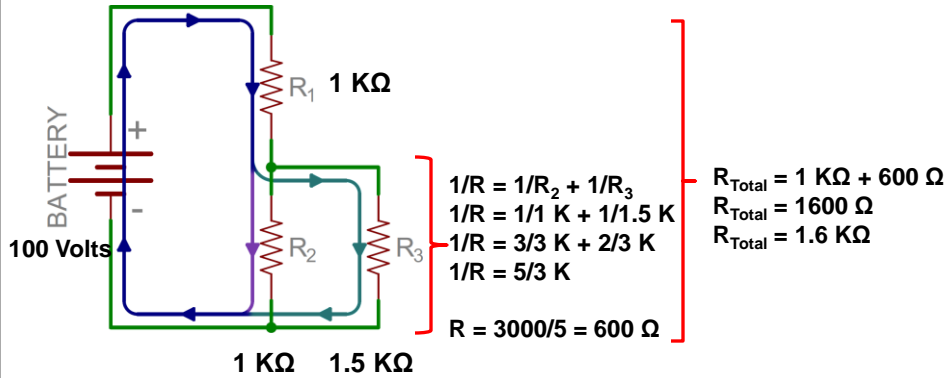

Al Penney  
VO1NO

# Energy and Power

---

- Energy is the ability to do work.
- Some common types include **Kinetic** and **Potential**.
- A cell has Potential Energy – it stores chemical energy that can be released to do work.
- When electrons move against a resistance, work is done.
- The **rate** at which work is done is called **Power**.

Al Penney  
VO1NO

An important aspect of any electrical or electronic circuit is the power associated with it. It is found that when a current flows through a resistor, electrical energy is converted into heat. This fact is used by electrical heaters which consist of a resistor through which current flows. Light bulbs use the same principle, heating the element up so that it glows white hot and produces light. At other times much smaller resistors and very much smaller currents are used. Here the amount of heat generated may be very small. However if some current flows then some heat is generated. In this instance the heat generated represents the amount of electrical power being dissipated.

## Definition of power

Whether power is used in a mechanical environment or an electrical environment, the definition of power is still the same. The way in which it may be discussed may be slightly different, but nevertheless the definition and actuality of it is exactly the same.

## Electric power definition:

Electric power is the rate, per unit time, at which electrical energy is transferred by an electric circuit. It is the rate of doing work.

In [physics](#), **energy** is the [quantitative property](#) that must be [transferred](#) to an [object](#) in order to perform [work](#) on, or to [heat](#), the object. Energy is a [conserved quantity](#); the law of [conservation of energy](#) states that energy can be [converted](#) in form, but not created or destroyed. The SI [unit](#) of energy is the [joule](#), which is the energy transferred to an object by the [work](#) of moving it a distance of 1 [metre](#) against a [force](#) of 1 [newton](#).

**Common forms of energy include the kinetic energy of a moving object, the potential energy stored by an object's position in a force field (gravitational, electric or magnetic), the elastic energy stored by stretching solid objects, the chemical energy released when a fuel burns, the radiant energy carried by light, and the thermal energy due to an object's temperature.**

# Power

- Basic unit of Power is the **Watt**, abbreviated W.
- In electrical systems, we can calculate power if we know any two of
  - Voltage;
  - Current; or
  - Resistance.

$$P = I \times E = E^2 / R = I^2 \times R$$

**(Mnemonic PIE)**

Al Penney  
VO1NO

## Definition of the watt:

The watt is the SI unit of power defining the rate of energy conversion and it is equivalent to one joule per second.


The watt can be defined according to the application:

•**Electrical definition of the watt:** one watt is the rate at which work is done when a current of one ampere, I of current flows through a network which has an electrical potential difference of one volt, V.  $W = V I$

The **joule** (symbol: **J**) is a **derived unit** of **energy** in the **International System of Units**. It is equal to the energy transferred to (or **work** done on) an object when a **force** of one **newton** acts on that object in the direction of the force's motion through a distance of one **metre** (1 newton metre or N·m). It is also the energy dissipated as heat when an electric **current** of one **ampere** passes through a **resistance** of one **ohm** for one second. It is named after the English physicist **James Prescott Joule** (1818–1889)

# Calculating Power #1

---

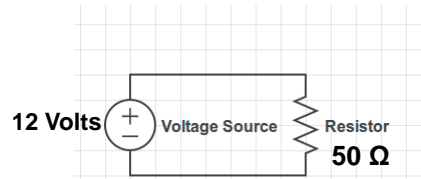


$$P = E \times I = E^2 / R = I^2 \times R$$

Al Penney  
VO1NO

# Calculating Power #1

---

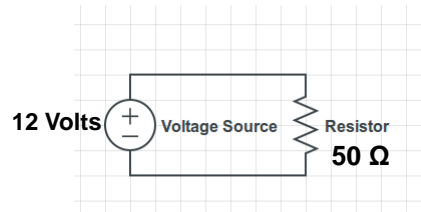


$$P = E \times I = E^2 / R = I^2 \times R$$
$$P = E^2 / R$$

Al Penney  
VO1NO

# Calculating Power #1

---

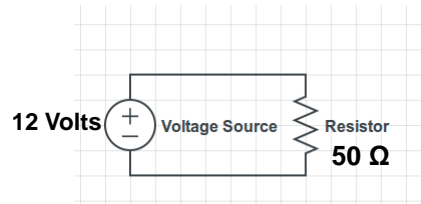

$$P = E \times I = E^2 / R = I^2 \times R$$

$$P = E^2 / R$$

$$P = 12^2 / 50$$

$$P = 144 / 50$$


$$P = 2.88 \text{ Watts}$$

Al Penney  
VO1NO



# Calculating Power #2


---

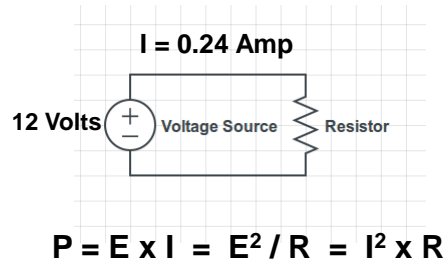

Al Penney  
VO1NO

# Calculating Power #2

---

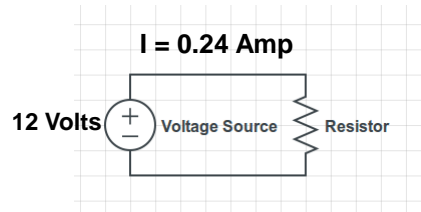


$$P = E \times I = E^2 / R = I^2 \times R$$
$$P = E \times I$$

Al Penney  
VO1NO

# Calculating Power #2

---

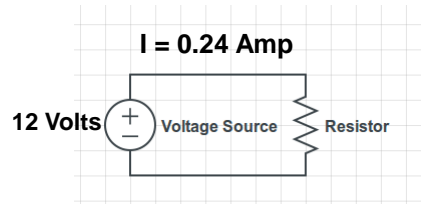

$$P = E \times I = E^2 / R = I^2 \times R$$

$$P = E \times I$$


$$P = 12 \times 0.24$$

$$P = 2.88 \text{ Watts}$$

Al Penney  
VO1NO

# Calculating Power #3

---

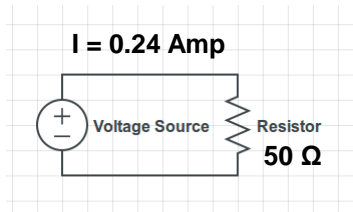


$$P = E \times I = E^2 / R = I^2 \times R$$

Al Penney  
VO1NO

# Calculating Power #3

---

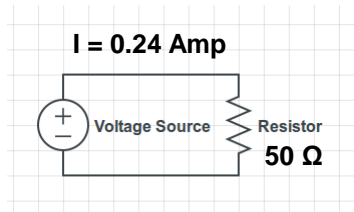


$$P = E \times I = E^2 / R = I^2 \times R$$
$$P = I^2 \times R$$

Al Penney  
VO1NO

# Calculating Power #3

---

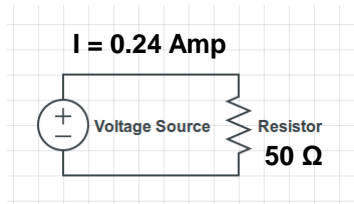

$$P = E \times I = E^2 / R = I^2 \times R$$

$$P = I^2 \times R$$


$$P = 0.24^2 \times 50$$

$$P = 0.0576 \times 50$$

$$P = 2.88 \text{ Watts}$$

Al Penney  
VO1NO

# Circuit Calculator

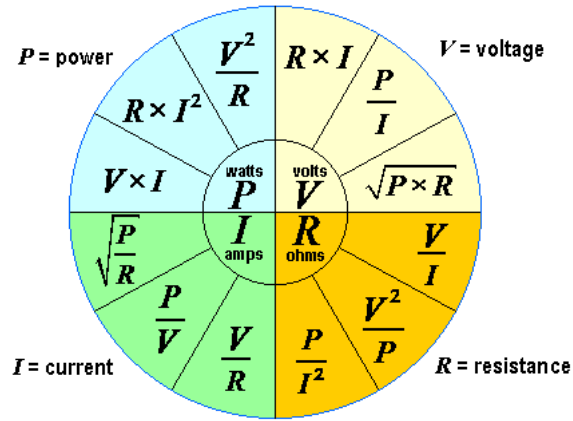

**Remember the Units – Ohms, Volts, Amps, Watts!!**

Al Penney  
VO1NO

# Power and Resistors


---

- Resistors rated not just by resistance, but also **amount of heat (power)** they can **safely dissipate**.
- Measured in **Watts**.
- In general, bigger resistors can dissipate more heat than smaller resistors.
- Use 50% to 100% safety margin in selecting components.

Al Penney  
VO1NO



# Power and Resistors

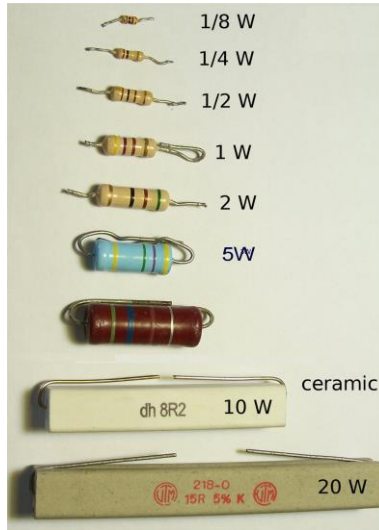

Al Penney  
VO1NO

# Power Ratings in Circuits

---

- **Series Circuits**

- Same current through all resistors.
- Calculate power dissipated by each separately (**Power =  $I^2 \times R$** ).
- Lowest wattage component sets max rating of the overall circuit.

Al Penney  
VO1NO

# Power Ratings in Circuits

---


- **Parallel Circuits**

- Same voltage applied to all resistors.
- Calculate power dissipated by each separately  
**(Power =  $E^2 / R$ ).**
- Do not exceed current and power ratings of any resistor in the group.
- For greater heat dissipation, replace a single resistor with two resistors of twice the resistance (assuming same wattage).

Al Penney  
VO1NO

# Heat – Parallel Resistors

---

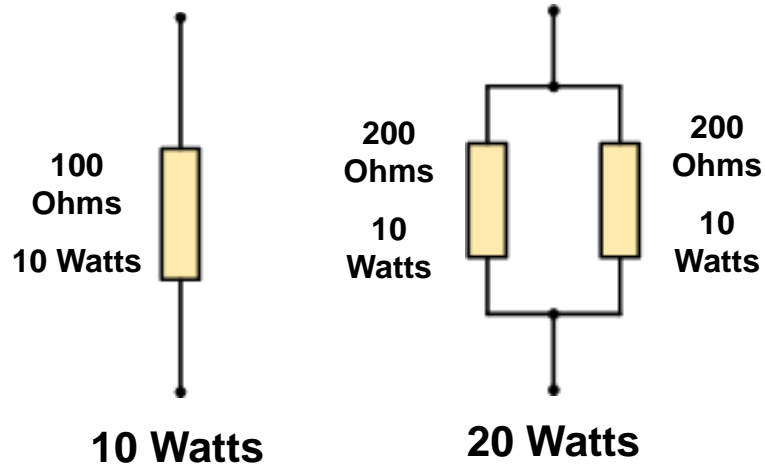

Al Penney  
VO1NO

# Questions?

Al Penney  
VO1NO

# Review Question 1

If you have light bulbs marked 40 watts, 60 watts and 100 watts, which one will use electrical energy the fastest?

- The 40 watt bulb
- The 60 watt bulb
- The 100 watt bulb
- They will all be the same

Al Penney  
VO1NO

# Review Question 1

If you have light bulbs marked 40 watts, 60 watts and 100 watts, which one will use electrical energy the fastest?

- The 40 watt bulb
- The 60 watt bulb
- The 100 watt bulb
- They will all be the same

< **The 100 watt bulb** >

Al Penney  
VO1NO

## Review Question 2

Which electrical circuit will have no current?

- A short circuit
- A complete circuit
- A closed circuit
- An open circuit

Al Penney  
VO1NO



## Review Question 2

Which electrical circuit will have no current?

- A short circuit
  - A complete circuit
  - A closed circuit
  - An open circuit
- < **An open circuit** >

Al Penney  
VO1NO

## Review Question 3

Which two electrical units multiplied together give the unit “watts”?

- Amperes and henrys
- Volts and amperes
- Volts and farads
- Farads and henrys

Al Penney  
VO1NO

## Review Question 3

Which two electrical units multiplied together give the unit “watts”?

- Amperes and henrys
  - Volts and amperes
  - Volts and farads
  - Farads and henrys
- < **Volts and amperes** >

Al Penney  
VO1NO

## Review Question 4

How is the resistance in a DC circuit calculated when the voltage and current are known?

- Resistance equals current multiplied by voltage
- Resistance equals voltage divided by current
- Resistance equals power divided by voltage
- Resistance equals current divided by voltage

Al Penney  
VO1NO

## Review Question 4

How is the resistance in a DC circuit calculated when the voltage and current are known?

- Resistance equals current multiplied by voltage
  - Resistance equals voltage divided by current
  - Resistance equals power divided by voltage
  - Resistance equals current divided by voltage
- < **Resistance equals voltage divided by current** >

Al Penney  
VO1NO

## Review Question 5

The voltage required to force a current of 4.4 amperes through a resistance of 50 ohms is:

- 220 volts
- 2220 volts
- 22.0 volts
- 0.220 volt

Al Penney  
VO1NO

## Review Question 5

The voltage required to force a current of 4.4 amperes through a resistance of 50 ohms is:

- 220 volts
- 2220 volts
- 22.0 volts
- 0.220 volt
- < **220 volts** >

Al Penney  
VO1NO

## Review Question 6

What voltage would be needed to supply a current of 200 milliamperes, to operate an electric lamp which has a resistance of 25 ohms?

- 5 volts
- 8 volts
- 175 volts
- 225 volts

Al Penney  
VO1NO



## Review Question 6

What voltage would be needed to supply a current of 200 milliamperes, to operate an electric lamp which has a resistance of 25 ohms?

- 5 volts
- 8 volts
- 175 volts
- 225 volts
- < 5 volts >**

Al Penney  
VO1NO

## Review Question 7

Total resistance in a parallel circuit:

- is always less than the smallest resistance
- depends upon the voltage drop across each branch
- could be equal to the resistance of one branch
- depends upon the applied voltage

Al Penney  
VO1NO

## Review Question 7

Total resistance in a parallel circuit:

- is always less than the smallest resistance
  - depends upon the voltage drop across each branch
  - could be equal to the resistance of one branch
  - depends upon the applied voltage
- < is always less than the smallest resistance >**

Al Penney  
VO1NO

## Review Question 8

One advantage of replacing a 50 ohm resistor with a parallel combination of two similarly rated 100 ohm resistors is that the parallel combination will have:

- lesser resistance and similar power rating
- the same resistance but greater power rating
- the same resistance but lesser power rating
- greater resistance and similar power rating

Al Penney  
VO1NO

## Review Question 8

One advantage of replacing a 50 ohm resistor with a parallel combination of two similarly rated 100 ohm resistors is that the parallel combination will have:

- lesser resistance and similar power rating
  - the same resistance but greater power rating
  - the same resistance but lesser power rating
  - greater resistance and similar power rating
- < the same resistance but greater power rating >**

Al Penney  
VO1NO

## For Next Class:

- Review Chapter 3 of Basic Study Guide;
- Read Chapter 4 of Basic Study Guide; and
- Read RBR-4:
  - <https://www.ic.gc.ca/eic/site/smt-gst.nsf/eng/sf10650.html>

Al Penney  
VO1NO


# Questions?

Al Penney  
VO1NO







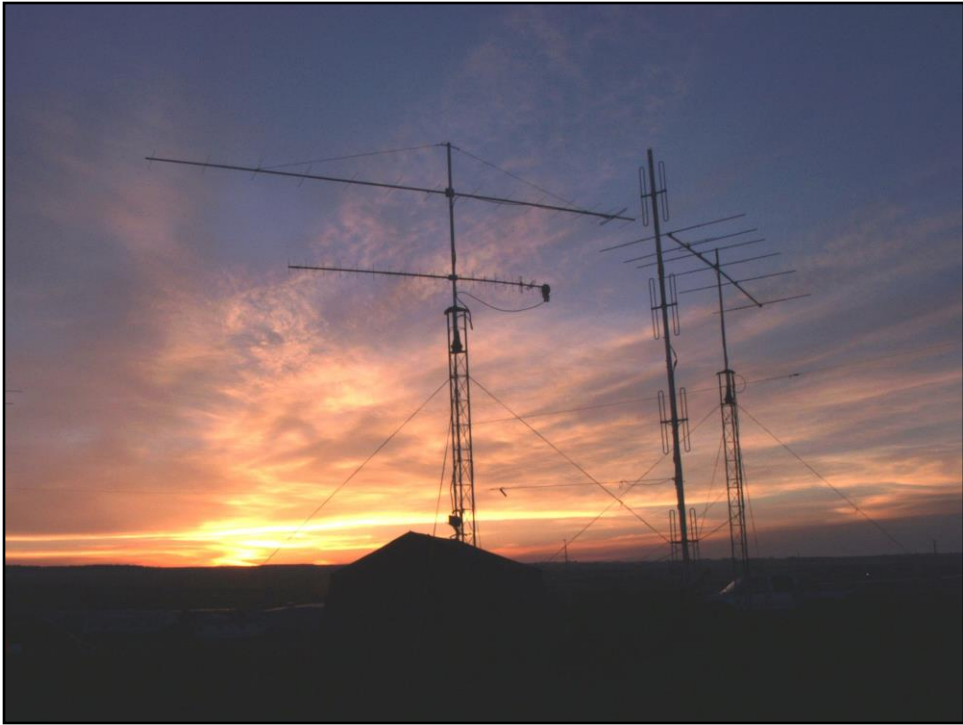











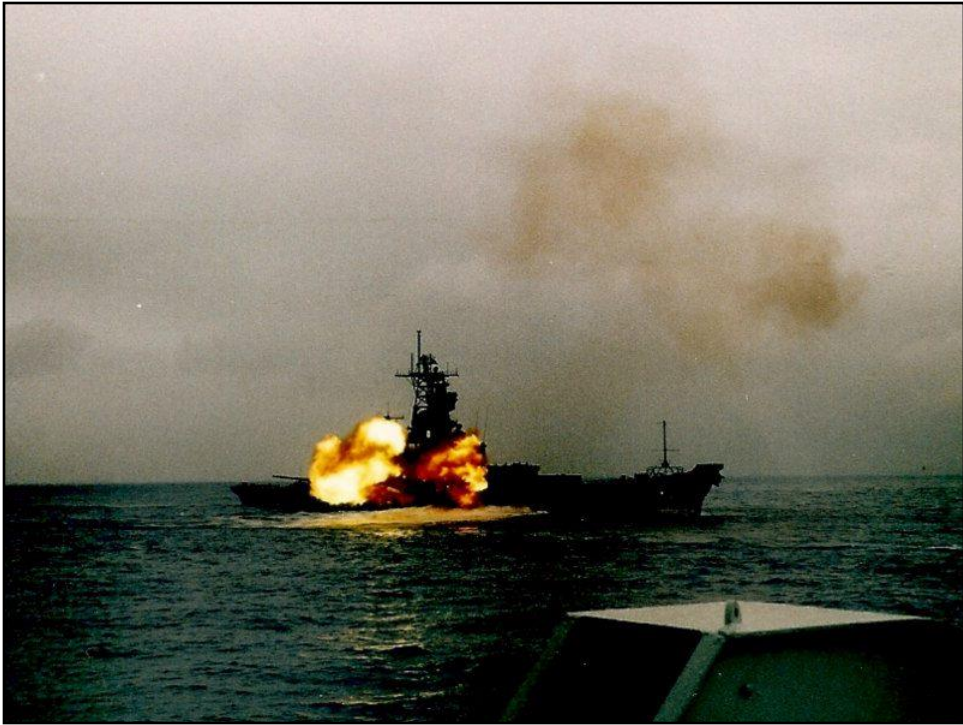



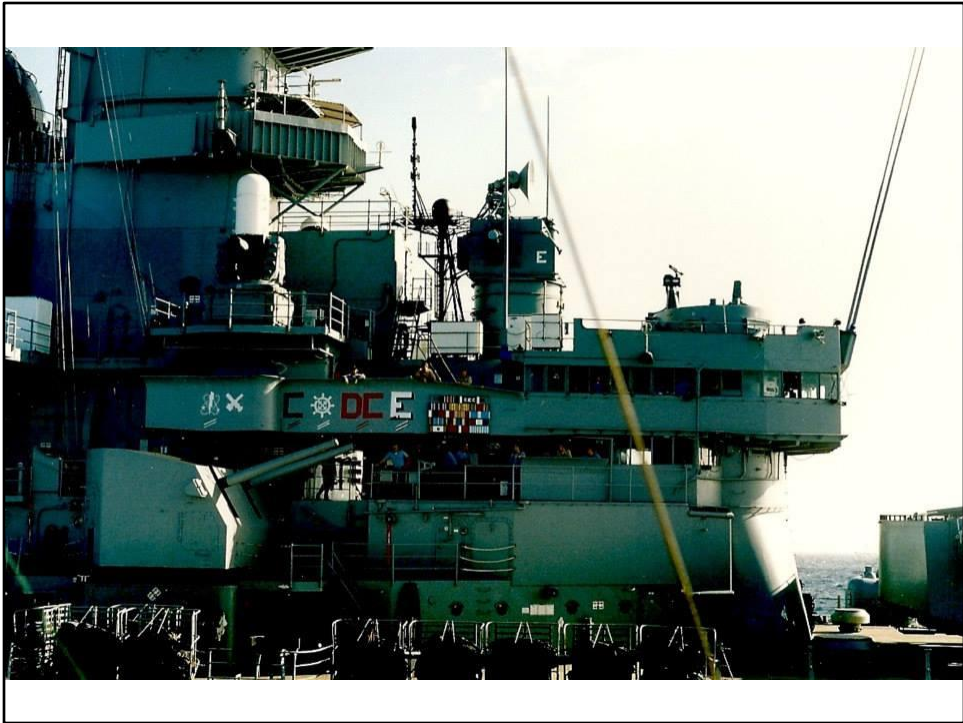



# Questions?

Al Penney  
VO1NO